

ECE 6130: LECTURE 1 REVIEW TRANSMISSION LINES


Text Section 2.1, Handout

Portfolio:

- 1) Describe the lumped element transmission line model.
- 2) Describe how to calculate the lumped element values for known lines such as coaxial and microstripline (See Chapter 2 Problems 1,2)

"Transmission Line" -- Any structure or media which *guides* EM waves from one location to another.

Two-port circuit diagram:

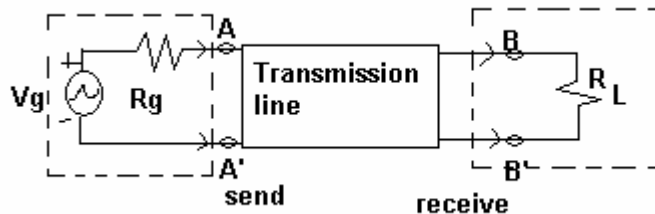

Effect of Transmission line (function of frequency and speed of wave):

$$V_{AA'} = V_g(t) = V_o \cos(\omega t) \text{ volts}$$

$$V_{BB'} = V_{AA'}(t + t_{\text{delay}}) = V_o \cos(\omega(t + \text{length}/\text{speed})) \text{ volts}$$

$$\text{Speed} = v_o = 2.996e8 \text{ m/s}$$

Example 1: $f = 60 \text{ Hz}$, $\text{length} = 1 \text{ meter}$, $\omega * t_{\text{delay}} = .0000012$, $V_{BB'} = V_{AA'}$

Example 2: $f = 1\text{GHz}$, $\text{length} = 1\text{meter}$, $\omega * t_{\text{delay}} = 20.94 \text{ radians}$! 6.67 cycles, $V_{BB'} = -0.49 * V_{AA'}$

Example 3: $f = 10 \text{ GHz}$, $\text{length} = 1 \text{ cm}$, $\omega * t_{\text{delay}} = 2.094 \text{ radians}$, $V_{BB'} = -.49 * V_{AA'}$

Reflections:

With 6.67 cycles, there has been a lot of time for bounces (reflections) to get back to source.

- Reflections add (you think your computer line = 0.0, but it actually = .5, which is enough to give a digital "1")
- Reflections subtract (you think your power is 1 W, but it is actually .5 W)

Power Loss

- Reflections through lossy material
- Multiple bounces through semi-lossy material

Dispersive effects:

- Many materials have different properties at different frequencies. All water-based materials, many semi-conductors, etc.


Propagation Modes

- TEM : Transverse Electromagnetic (** we are going to study these)
 Transverse = perpendicular
E and **H** fields are both entirely perpendicular to the direction of propagation.
 Made up of two parallel conducting surfaces:
 Coaxial Line: See transparency Figure 2-5
- Higher - order transmission lines:
E and **H** fields have at least one significant component in direction of propagation. Combination of TE and TM.

Lumped –Element Model:

TEM transmission lines (remember, no fields in the direction of propagation) can be represented by a lumped element model ...

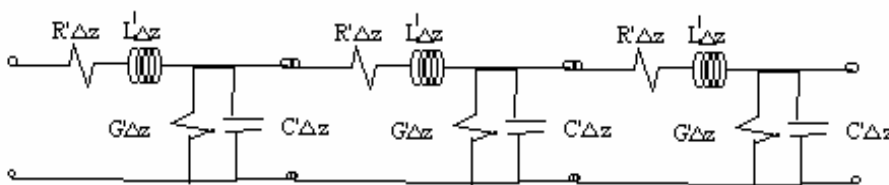- Parallel-wire equivalent
- Represents motion of fields down the transmission line
- Transverse field effects (all fields ARE transverse in TEM) are modeled by equivalent circuit elements ... RLC
- Accuracy of method depends on:
 - True TEM nature (non-transverse fields not properly modeled)
 - Correct calculation of circuit parameters (RLC) of line (done analytically, as we will do in a minute)



“Lumped” Elements:

R' : Combined resistance of both conductors / unit length (ohm/meter)

L' : Combined inductance of both conductors / unit length (H/m)

G' : Combined conductance of both conductors / unit length (S/m = 1/ (ohm-meter))

C' : Combined capacitance of both conductors / unit length (F/m)

How do you get them? From derivations See in a minute → Tabulated for standard transmission lines

What effects do we see?

R' : Waves move down the transmission lines, but if the material has a resistance (anything except a perfect conductor), $R' \neq 0$. Resistance would be continuous, rather than discrete as shown ... it is exact in the limit as $\Delta z \rightarrow 0$. Thus a “lumped” element, is generally an approximation.

L' : Inductance represents magnetic flux generated by the current on the transmission line. Again, it would be continuous, but is represented by a small lumped element.

G' : Conductance (1/R) . This represents coupling currents between the line. If the internal material has some conductivity, it can draw current from one line to the other.

C' : Capacitance between the lines. Charges induced on the lines produce a voltage . Capacitance is charge/voltage.

For all TEM lines (properties are of insulating material):

$$L'C' = \mu \epsilon$$

$$G'/C' = \sigma / \epsilon$$

Characteristic Impedance

$$Z_0 = V_{o+} / I_{o+} = V_{o-} / I_{o-} = \sqrt{(R+j\omega L)/(G+j\omega C)}$$