





ECE 6130 LUMPED ELEMENT IMPEDANCE MATCHING

Reference: Bowick, RF Circuits, pp. 66-75 (Handout)

Also: Handout sources for SMT caps, inductors

The L-Network:

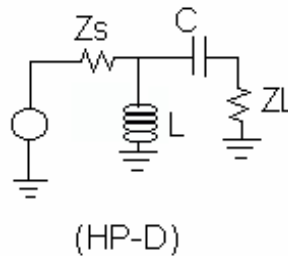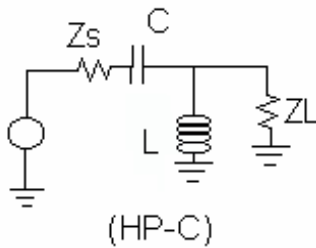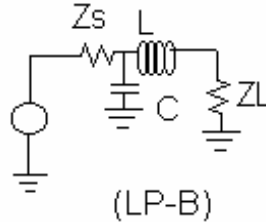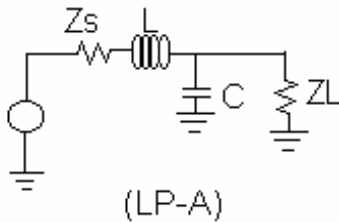Four different forms of the L-Shaped Network. LowPass (A,B) and High Pass (C,D):



Purpose of the Elements:

SHUNT Element : Transform large Z_L to smaller value with real part equal to the real part of Z_s .

SERIES Element: Resonate with (cancel) the imaginary part of the impedance.

Design steps:

$$Q_s = Q_p = \sqrt{\frac{R_p}{R_s}} - 1$$

$$Q_s = X_s / R_s$$

$$Q_p = R_p / X_p$$

Q_s = Q of series leg

Q_p = Q of parallel leg

R_p = Real part of parallel leg

R_s = Real part of series leg

X_s = Imaginary part of series leg

X_p = Imaginary part of parallel leg

X_s and X_p can be either capacitive or inductive, but must be of opposite type.

Example:

Match a 100-ohm load (R_p) to a 50-ohm line (R_s) at 1 GHz. Do not allow DC power to reach the load.


$$Q_s = Q_p = \sqrt{\frac{100}{50} - 1} = 1$$

$$X_s = Q_s R_s = (1)(50)$$

$$X_p = R_p / Q_p = 100 / 1$$

$$\omega = 2\pi(1\text{GHz})$$

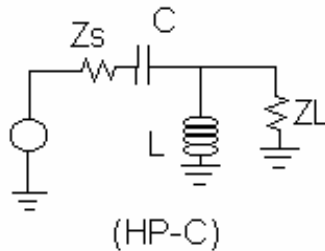Since we do not want DC power to reach the circuit, we need one of the high pass configurations such as (C) above. High Pass configuration (D) would work equally well.



Calculate values of L and C:

$$X_s = \frac{1}{\omega C} \rightarrow C = \frac{1}{\omega X_s} = 3.18 \text{ pF}$$

$$X_p = \omega L \rightarrow L = X_p / \omega = 15.9 \text{ nH}$$

PROBLEMS/LIMITATIONS with this method:

- 1) Component values can be limited (problem with all discrete element matches)
- 2) This is either HP or LP, not both (other methods will take care of this)
- 3) Cannot match impedances less than the line impedance (Q becomes imaginary)
- 4) Stray capacitances, inductances of the packaging of the elements, solder methods, line lengths (albeit small) may all become significant.

MATCHING COMPLEX IMPEDANCES

Two methods can be used to remove the load reactance:

- 1) Absorption (using the load reactance as part of the desired matching circuit)
- 2) Resonance (using an L to cancel a C or a C to cancel an L)

Example:

Same example as above, but let the load have a reactive component:



$$Z_L = 100 - j 25 \text{ ohms}$$

Design the matching network ignoring the reactive component, EXACTLY like it was done above.

The $X_L = -25 \text{ ohms}$ is equivalent to a capacitor in series with the load resistance R_L . The value of $C_L =$

$$1/(\omega X_L) = 6.4 \text{ pF}$$

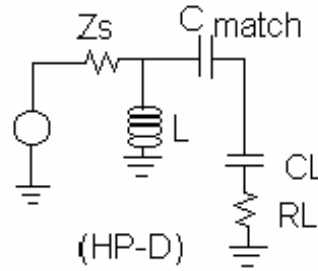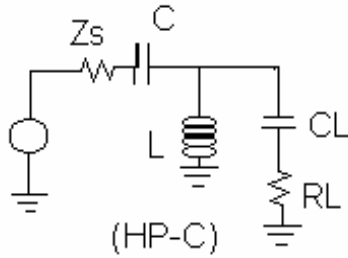This gives either of the two circuits shown below:



ABSORPTION OF CL:

CL can now be "absorbed" in the HP-D configuration.

The combination of Cmatch and CL should equal C from the original matching network design.

That is :

$$C = C_{total} = 3.18\text{pF} = C_{match} \text{ in series with } CL = \frac{C_{match} CL}{CL + C_{match}}$$

OR:


$$C_{match} = \frac{C CL}{CL - C} = \frac{(3.18\text{pF})(6.4\text{pF})}{(6.4-3.18\text{pF})} = 6.32 \text{ pF}$$

LIMITATION:

This only works if CL is greater than Ctotal.

Your book has a similar example where the load is modeled with a parallel C,R configuration.

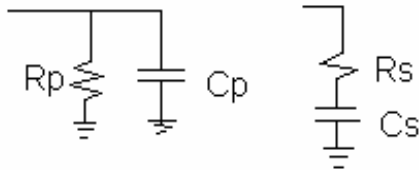TO CONVERT FROM SERIES TO PARALLEL LOAD ADMITTANCE:



Write the impedance of the above configurations:

$$Z_p = (R_p) (1/j\omega C_p) / (R_p + 1/j\omega C_p) = R_p / (1 + j\omega C_p R_p)$$

$$Z_s = R_s + 1/j\omega C_s$$

Equate: $Z_s = Z_p$

This gives two equations and two unknowns.

The unknowns are either R_s, C_s (if you have R_p, C_p) OR R_p, C_p (if you have R_s, C_s)

Solving gives

$$R_s = \frac{X_p^2 R_p}{(X_p^2 + R_p^2)}$$

$$X_s = \frac{R_p R_s}{X_p}$$

where

$$X = \frac{-1}{\omega C} \text{ OR } \omega L$$

OR

$$R_p = (R_s^2 + X_s^2) / R_s$$

$$X_p = R_p R_s / X_s$$

For our case where $R_s=100$ and $X_s = -25$ ohms, we get $R_p=106.25$ ohms and $X_p = -425$ ohms.

This is a shunt capacitance $X_p = -1/(\omega C)$ where $C = 0.374$ pF

RESONANCE of CL:

If you cannot absorb CL, you may be able to resonate its effect away. This is done by canceling it out with an inductance. This is easier when the C and L are in parallel.

Then $L_p = 1/(\omega^2 C_p)=67.72$ H

The input impedance that needs to be matched is now $Z_L = R_p$ (which is different than the original RL).

Proceed with normal matching as in the first example. See also EXAMPLE 4.3 in the handout.

