

ECE 6130 Quadrature Coupler

Text Section 7.5

What is a quadrature coupler and how does it work?

Quadrature Coupler

90 degree phase shift between output ports.


Power Evenly divided (-3dB) between output ports.

All ports matched.

No coupling to port 4 (complete isolation).


$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

Branch Line Coupler:

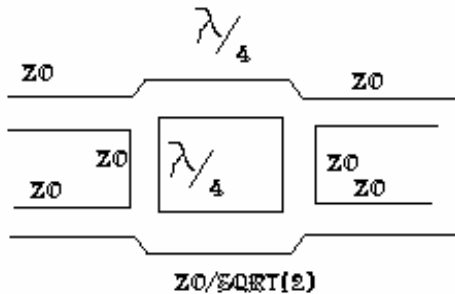


Even-Odd Mode Analysis:

Normalized Impedance Circuit Model:

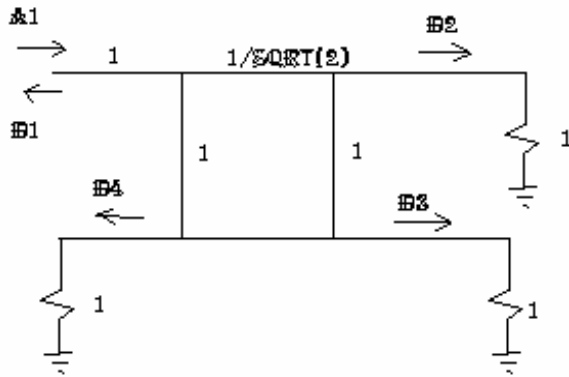

EVEN MODE:

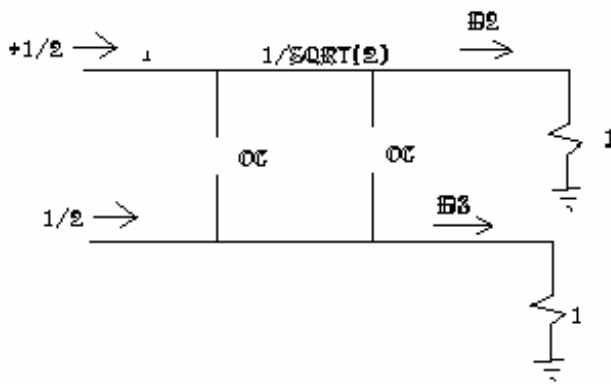


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = [\lambda/8 \text{ Stub}] [\lambda/4 \text{ TL}] [\lambda/8 \text{ Stub}]$$

$$= \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} \cos \beta l & jZ_0 \sin \beta l \\ jZ_0 \sin \beta l & \cos \beta l \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} \begin{bmatrix} 0 & j/\sqrt{2} \\ j\sqrt{2} & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} -1 & j \\ j & -1 \end{bmatrix}$$

$$S_{11} = \Gamma_e = \frac{A+B-C-D}{A+B+C+D} = \frac{(-1+j-j+1)/\sqrt{2}}{(-1+j+j-1)/\sqrt{2}} = 0$$
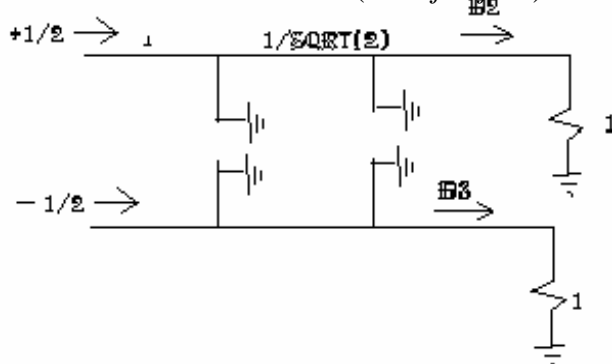
$$S_{21} = T_e = \frac{2}{A+B+C+D} = \frac{2}{(-1+j+j-1)/\sqrt{2}} = \frac{-1}{\sqrt{2}}(1+j)$$



$$\begin{aligned}
\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e &= [\lambda / 8 \text{ Stub}] [\lambda / 4 \text{ TL}] [\lambda / 8 \text{ Stub}] \\
&= \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} \cos \beta \ell & jZ_0 \sin \beta \ell \\ jZ_0 \sin \beta \ell & \cos \beta \ell \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \\
&= \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} \begin{bmatrix} 0 & j/\sqrt{2} \\ j\sqrt{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & j \\ j & 1 \end{bmatrix} \\
S_{11} = \Gamma_e &= \frac{A + B - C - D}{A + B + C + D} = \frac{(1 + j - j - 1) / \sqrt{2}}{(1 + j + j + 1) / \sqrt{2}} = 0 \\
S_{21} = T_e &= \frac{2}{A + B + C + D} = \frac{2}{(1 + j + j + 1) / \sqrt{2}} = \frac{1}{\sqrt{2}} (1 - j)
\end{aligned}$$

COMBINE EVEN and ODD MODES:

Incident voltage at node 1: $V_{1e} = V_{1o} = 1/2$

Incident voltage at node 4: $V_{4e} = -V_{4o} = -1/2$

Amplitudes of waves exiting each node:

$B_1 = V_{1e} \Gamma_e + V_{1o} \Gamma_o = \Gamma_e / 2 + \Gamma_o / 2 = 0$ (Port 1 is matched)

$B_2 = V_{1e} T_e + V_{1o} T_o = T_e / 2 + T_o / 2 = -j / \sqrt{2}$ (Half power, -90 degree phase shift from port 1 to 2)

$B_3 = V_{4e} T_e + V_{4o} T_o = T_e / 2 - T_o / 2 = -1/\sqrt{2}$ (Half power, 180 degree phase shift from port 1 to 3)

$B_4 = V_{4e} \Gamma_e + V_{4o} \Gamma_o = \Gamma_e / 2 - \Gamma_o / 2 = 0$ (Port 4 is isolated)

This is the first row of the S matrix:

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

Other rows are found by transposition:

Row 2 for example:

$$1 \rightarrow 2 = 0$$

$$2 \rightarrow 1 = j$$

$$3 \rightarrow 4 = 1$$

$$4 \rightarrow 3 = 0$$