
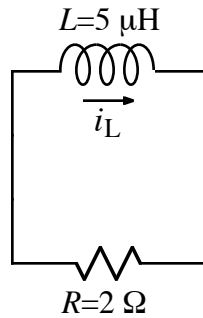


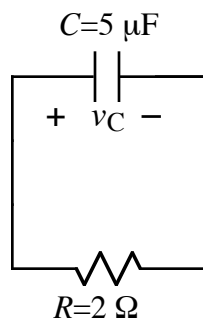
1. Find the current,  $i_L$ , through the inductor in the circuit below for  $t > 0$  if  $i_L(t=0) = 5$  A.



2. Find the voltage,  $v_C$ , across the capacitor in the circuit below for  $t > 0$  if  $v_C(t=0) = 5$  V.




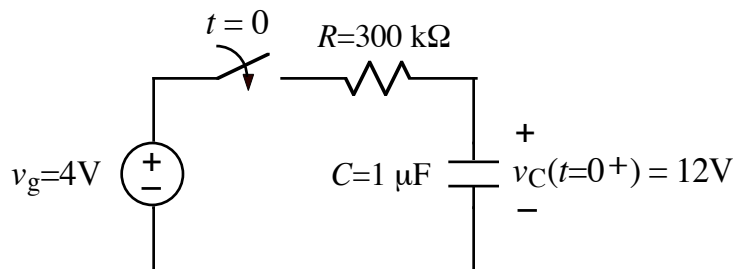3. After being open for a long time, the switch closes at  $t = 0$ .




- a) Find an expression for  $v_C(t)$  for  $t \geq 0$ .
- b) Find the energy stored in the capacitor at time  $t = 10$  ms.

4.

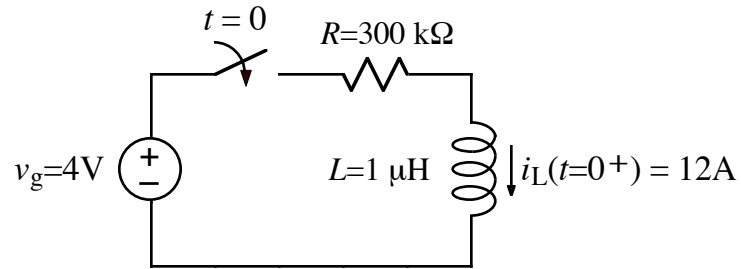

- Find an expression for  $i_L(t)$  for  $t \geq 0$ . Note: Assume the initial current in the  $L$  is created by circuitry not shown in the diagram.
- Find the energy stored in the inductor at time  $t = 10$  ms.

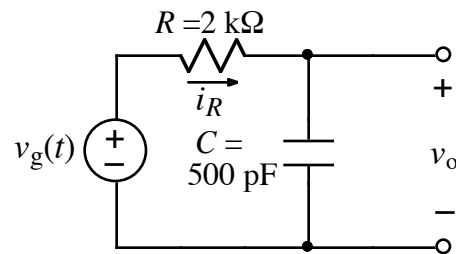5. After being zero for a long time, the value of  $v_g(t)$  changes to 9 V at  $t = 0$  (and remains at 9 V as time increases to infinity).



- Find an expression for  $v_o(t)$  for  $t > 0$ .
- Find the current,  $i_R$ , in  $R$  as a function of time.