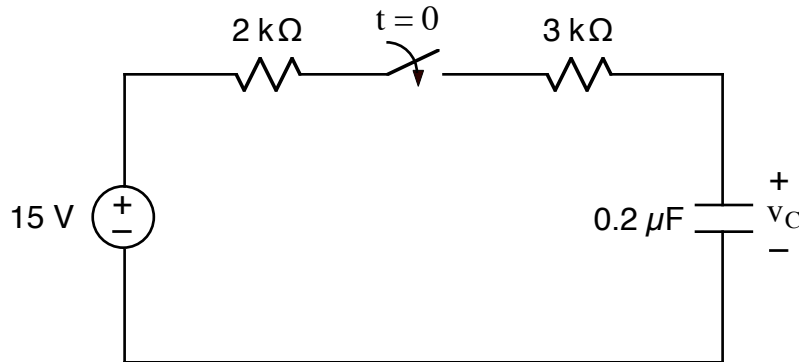


Ex:



After being open for a long time, the switch closes at $t = 0$. $v_C(t = 0^-) = 0V$. Find $v_C(t)$ for $t > 0$.

sol'n: Use the general form of solution for RC problems.

$$v_C(t > 0) = v_C(t \rightarrow \infty) + [v_C(0^+) - v_C(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

We now proceed to find the following values:


$$v_C(0^+), v_C(t \rightarrow \infty), \text{ and } R_{Th}$$

To find $v_C(0^+)$, we consider $t = 0^-$ and find $v_C(0^-)$. Since v_C is an energy variable that cannot change instantly, we have $v_C(0^+) = v_C(0^-)$.

At $t = 0^-$, currents and voltages have stabilized, and all time derivatives of currents and voltages are zero.

Thus, $i_C = C \frac{dv_C}{dt} = C \cdot 0 = 0$. C looks like open.

$t = 0^-$: C = open, switch open

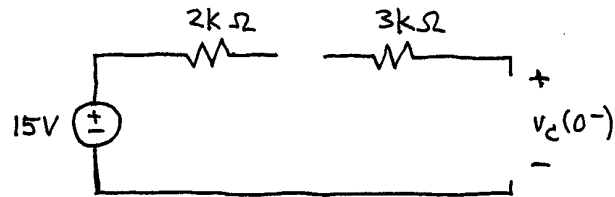


From the circuit diagram, we cannot determine $v_c(0^-)$. The C could be charged to some voltage, and it would remain at that voltage forever.

Fortunately, the problem states that $v_c(0^-) = 0V$.

$t = 0^+$: v_c cannot change instantly, so


$$v_c(0^+) = v_c(0^-) = 0V$$

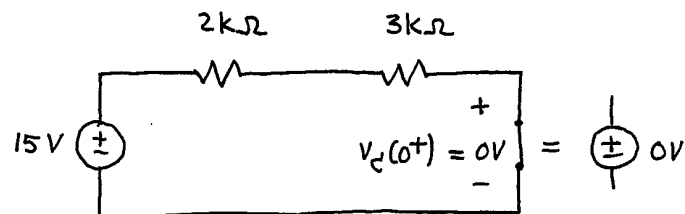If needed a circuit model at $t = 0^+$, we would model the C as a V src with value 0V. In other words, C = wire at $t = 0^+$.



To find $v_c(t \rightarrow \infty)$, we again use the idea that currents and voltages are stable and C = open.

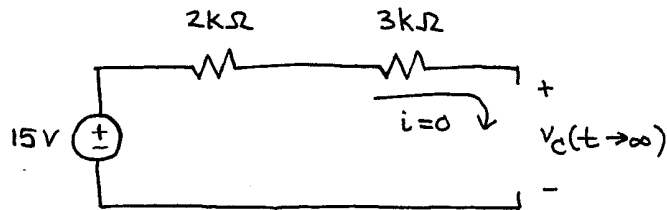$t \rightarrow \infty$: $C = \text{open}$, switch closed




Since no current flows, the voltage drop across the $2\text{k}\Omega$ and $3\text{k}\Omega$ R's is 0V.

Thus, we have 15V across C:

$$v_c(t \rightarrow \infty) = 15\text{V}$$

To find R_{TH} , we remove C and find the Thevenin equivalent resistance seen looking into the terminals where C was connected.

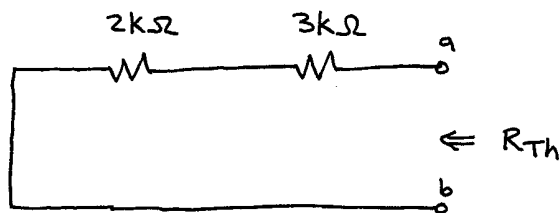For the circuit we are using here, we can find R_{TH} by turning off the independent 15V source:



$$R_{TH} = 2\text{k}\Omega + 3\text{k}\Omega = 5\text{k}\Omega \quad R_{TH}C = 5\text{k}\Omega \cdot 0.2\mu\text{F} = 1\text{ms}$$

$$\therefore v_c(t > 0) = 15\text{V} + (0\text{V} - 15\text{V}) e^{-t/1\text{ms}}$$

\uparrow \uparrow \uparrow
 $v_c(t \rightarrow \infty)$ $v_c(0^-)$ $v_c(t \rightarrow \infty)$