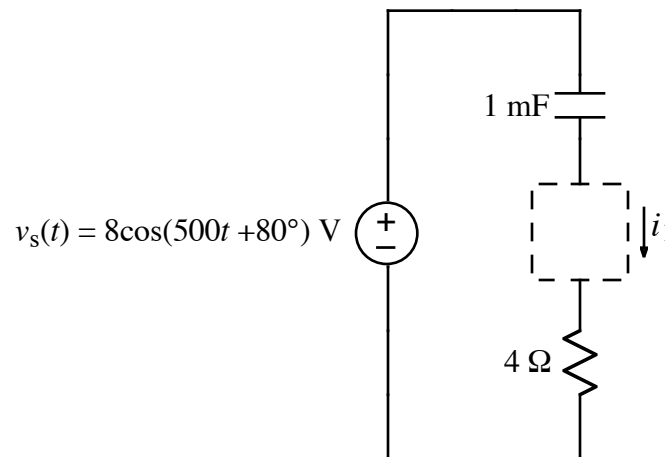


1. Give numerical answers to each of the following questions:
- Rationalize $\frac{1 - j\sqrt{3}}{1 + j\sqrt{3}}$. Express your answer in rectangular form.
 - Find the polar form of $[(j+1)(-1-j)]^*$. (Note: the asterisk means "conjugate".)
 - Find the following phasor: $P[-\sin(100t + 45^\circ)]$.
 - Find the magnitude of $\frac{(30 - j40)}{(7 - j24)e^{j30^\circ}}$.
 - Find the imaginary part of $\frac{6 - j}{3j}$.

2.




Choose an R , an L , or a C to be placed in the dashed-line box to make

$$i_1(t) = I_0 \sin(500t + 125^\circ)$$

where I_0 is a positive, (i.e., nonzero and non-negative), real constant. State the value of the component you choose.

3. With your component from part (a) in the circuit, calculate the resulting value of I_0 .

4.

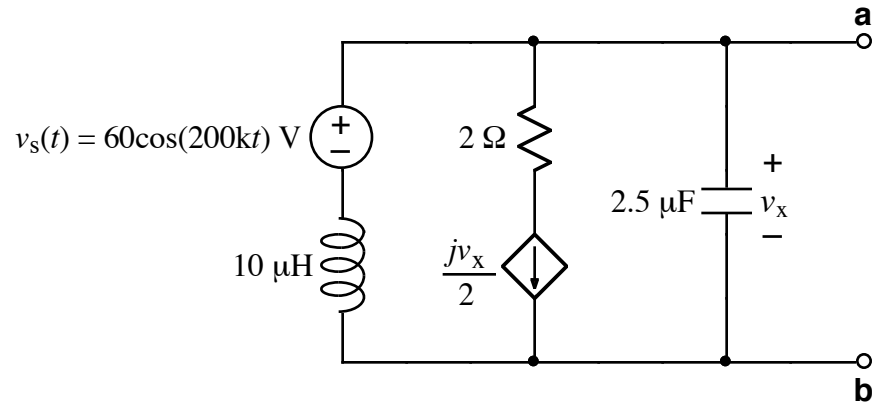

Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $v_s(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.

5.

Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for \mathbf{V}_{Th} and the numerical impedance value of z_{Th} .