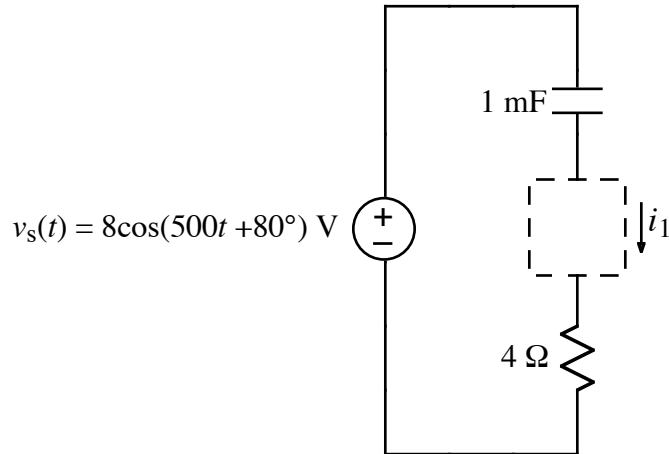



Ex:



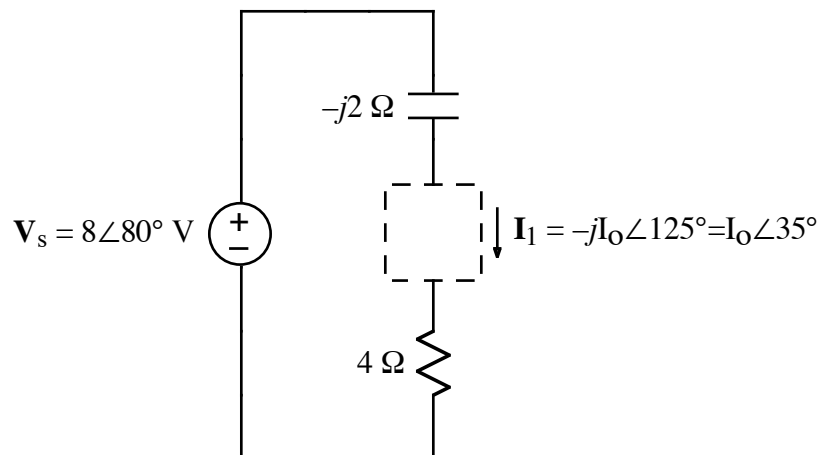- a) Choose an R , an L , or a C to be placed in the dashed-line box to make
- $$i_1(t) = I_o \sin(500t + 125^\circ)$$
- where I_o is a positive, (i.e., nonzero and non-negative), real constant. State the value of the component you choose.
- b) With your component from part (a) in the circuit, calculate the resulting value of I_o .

SOL'N: a) First, we convert the circuit to the frequency domain, where we have the circuit shown below. Note that for the capacitor, we have $z = 1/j\omega C =$

$$z = \frac{1}{j\omega C} = \frac{1}{j500 \text{ r/s} \cdot 1 \text{ mF}} = -j2 \Omega$$



Current \mathbf{I}_1 is given by the voltage of the source divided by the total impedance in the circuit:

$$\mathbf{I}_1 = I_o \angle 35^\circ = \frac{\mathbf{V}_s}{z_{\text{Tot}}} = \frac{8 \angle 80^\circ \text{ V}}{4 - j2 + z_{\text{box}}}$$

Rearranging gives a formula for z_{box} :

$$4 - j2 + z_{\text{box}} = \frac{8 \angle 80^\circ \text{ V}}{I_o \angle 35^\circ} = \frac{8 \text{ V}}{I_o} \angle 45^\circ$$

We see that the total impedance must have a phase angle of 45° . This is only possible if the total impedance has positive and equal real and imaginary parts. Since the capacitor gives a negative imaginary value, the value of z_{box} must overcome this negative imaginary value. Since z_{box} is the impedance of a single R , L , or C , it can be only purely real (and positive) or purely imaginary. We conclude that z_{box} must be imaginary and positive and yield a total impedance with the real and imaginary parts equal to the real part of the total impedance:

$$4 \ \Omega - j2 \ \Omega + z_{\text{box}} = 4 + j4 \ \Omega$$

or

$$z_{\text{box}} = j6 \ \Omega$$

To obtain this impedance, we use an inductor:

$$z_{\text{box}} = j\omega L = j6 \ \Omega$$

or

$$\omega L = 6 \ \Omega$$

or

$$L = \frac{6 \ \Omega}{\omega} = \frac{6 \ \Omega}{500} = 12 \text{ mH}$$

- b) From part (a), we see that $z_{\text{box}} = 4 + j4 \ \Omega$. We use Ohm's law to find the current, and we take the magnitude of the equation to find I_o :

$$\mathbf{I}_1 = \frac{\mathbf{V}_s}{4 + j4 \, \Omega} = \frac{8\angle 80^\circ \text{ V}}{4\sqrt{2}\angle 45^\circ \, \Omega} = 2\sqrt{2}\angle 35^\circ \text{ A}$$

or

$$I_o = \left| \frac{\mathbf{V}_s}{4 + j4 \, \Omega} \right| = \left| \frac{8\angle 80^\circ \text{ V}}{4\sqrt{2}\angle 45^\circ \, \Omega} \right| = \left| \frac{8 \text{ V}}{4\sqrt{2} \, \Omega} \right| = 2\sqrt{2} \text{ A}$$