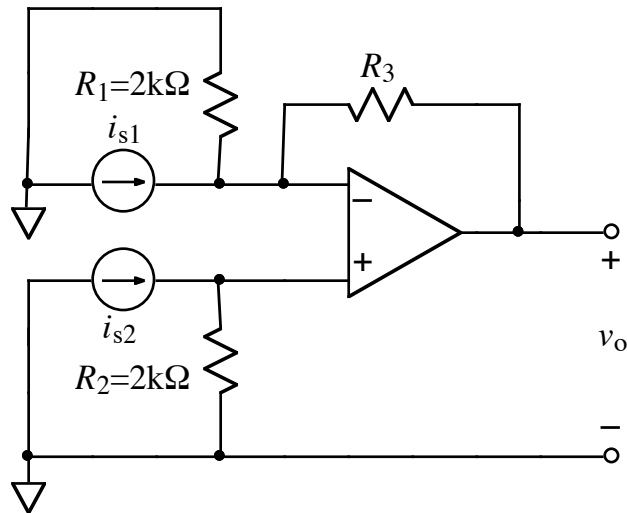


Ex:



Rail voltages = ± 10 V

- The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_{s1} , i_{s2} , R_1 , R_2 , and R_3 .
- If $i_{s1} = 0$ μA , find the value of R_3 that will yield an output voltage of $v_o = 1$ V when $i_{s2} = 10$ μA .
- Derive a symbolic expression for v_o in terms of common mode and differential input currents:

$$i_{\Sigma} \equiv \frac{i_{s1} + i_{s2}}{2} \quad \text{and} \quad i_{\Delta} \equiv \frac{i_{s1} - i_{s2}}{2}$$

The expression must contain not more than the parameters i_{Σ} , i_{Δ} , R_1 , R_2 , and R_3 . Write the expression as i_{Σ} times a term plus i_{Δ} times a term. Hint: start by writing i_{s1} and i_{s2} in terms of i_{Σ} and i_{Δ} :

$$i_{s1} \equiv i_{\Sigma} + i_{\Delta} \quad \text{and} \quad i_{s2} \equiv i_{\Sigma} - i_{\Delta}$$

- If $i_{\Delta} = 0$ and $R_1 = R_2$, write a formula for the current flowing from left to right in R_3 as a function of not more (and possibly less) than the following terms: i_{Σ} , R_1 , R_2 , and R_3 .

sol'n: a) First, we find v_p (voltage at + input):

$$v_p = i_{s2} R_2$$

Second, we find the current flowing toward the - input from the left, using v_n (voltage at - input) = v_p :

$$i_l = i_{s1} - \frac{v_n}{R_1} = i_{s1} - \frac{i_{s2} R_2}{R_1}$$

Third, we find the current flowing in the feedback resistor, R_3 , from left to right:

$$i_r = \frac{v_n - v_o}{R_3} = \frac{i_{s2} R_2 - v_o}{R_3}$$

Fourth, we set $i_r = i_l$ and solve for v_o :

$$i_{s1} - \frac{i_{s2} R_2}{R_1} = \frac{i_{s2} R_2 - v_o}{R_3}$$

$$\text{or } v_o = -i_{s1} R_3 + i_{s2} R_2 \left(1 + \frac{R_3}{R_1}\right)$$

$$\text{b) } 1V = 10\mu A \cdot 2k\Omega \left(1 + \frac{R_3}{2k\Omega}\right) = 20mV \left(1 + \frac{R_3}{2k\Omega}\right)$$

$$\therefore 1 + \frac{R_3}{2k\Omega} = 50 \quad \text{or} \quad \frac{R_3}{2k\Omega} = 49$$

$$\text{or } R_3 = 98 k\Omega$$

$$c) \quad v_o = -(i_\Sigma + i_\Delta) R_3 + (i_\Sigma - i_\Delta) R_2 \left(1 + \frac{R_3}{R_1}\right)$$

or

$$v_o = i_\Sigma \left(R_2 + \frac{R_2 R_3}{R_1} - R_3 \right) - i_\Delta \left(R_2 + \frac{R_2 R_3}{R_1} + R_3 \right)$$

d) For $i_\Delta = 0$ and $R_1 = R_2$, we have

$$v_o = i_\Sigma \left(R_2 + \frac{R_2 R_3}{R_1} - R_3 \right)$$

$$\text{or } v_o = i_\Sigma R_2$$

$$\text{Then } i_{R3} = \frac{v_n - v_o}{R_3} = \frac{v_n - i_\Sigma R_2}{R_3}$$

$$\text{But } v_n = v_p = i_{s2} R_2 = \frac{i_{s1} + i_{s2}}{2} R_2$$

$$\text{(since } i_{s1} = i_{s2}) \quad = i_\Sigma R_2$$

$$\text{Then } i_{R3} = \frac{i_\Sigma R_2 - i_\Sigma R_2}{R_3} = 0 \text{ A}$$

Note: When $i_{s1} = i_{s2}$, the current in R_1 and R_2 is the same (since $v_n = v_p$), so there is no current left over to flow in R_3 .