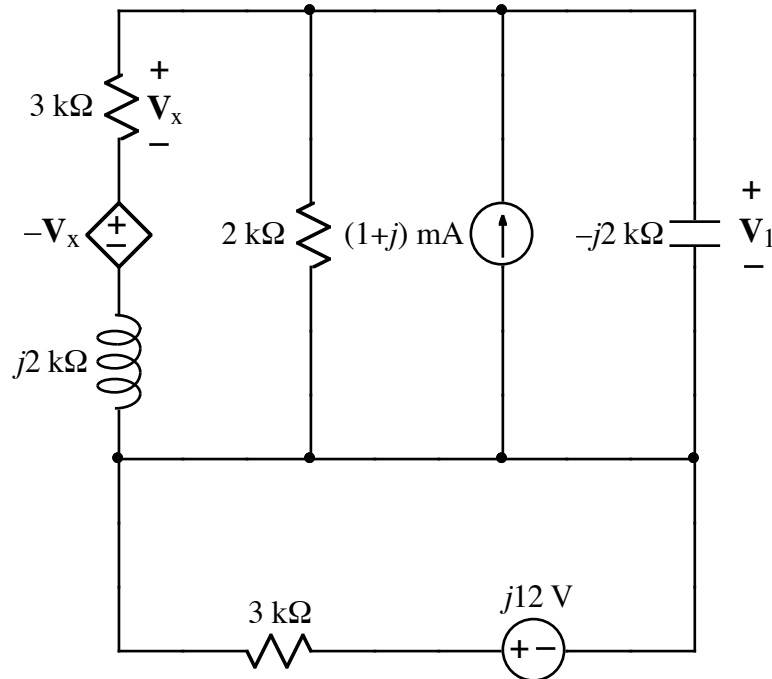


Ex:




- A frequency-domain circuit is shown above. Write the value of phasor voltage V_1 in rectangular form.
- Given $\omega = 500$ rad/s, write a numerical time-domain expression for $v_1(t)$, the inverse phasor of V_1 .

sol'n: a) The dependent -source voltage cancels out the voltage across the $3k\Omega$ resistor, yielding the equivalent of a wire, (i.e. 0V).

We may also ignore the bottom part of the circuit, which is shorted out by the middle wire.


Thus far, we have the following circuit:

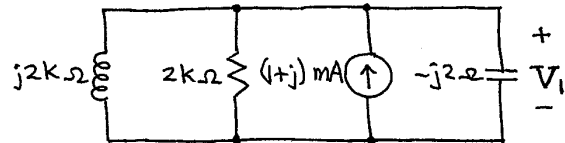

Now we observe that the $j2k\Omega$ and $-j2k\Omega$ in parallel are equivalent to an open circuit:

$$j2k\Omega \parallel -j2k\Omega = j2k\Omega \cdot \frac{1}{-1} = j2k\Omega \cdot \frac{-1}{1} = -j2k\Omega$$

Thus, the L and C disappear:

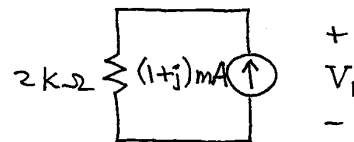

Now we use Ohm's Law:

$$V_1 = (1+j) \text{ mA} \cdot 2k\Omega = 2 + j2 \text{ V}$$

b) In polar form, $V_1 = 2\sqrt{2} \angle 45^\circ \text{ V}$

In the time domain, we have

$$v_1(t) = 2\sqrt{2} \cos(500t + 45^\circ) \text{ V}$$

Note: We could also directly take the inverse phasor of $2 + j2 \text{ V}$:

$$v_1(t) = 2 \cos(500t) - 2 \sin(500t) \text{ V}$$