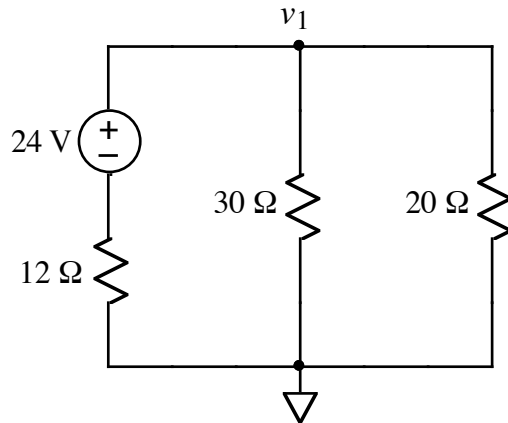


Ex:



- Use the node-voltage method to find v_1 .
- Find the equivalent resistance for the 30Ω and 20Ω resistors in parallel. Then use the voltage divider formula to find v_1 . Verify that both (a) and (b) have the same answer.

SOL'N: a) We set the sum of currents out of v_1 equal to zero:

$$\frac{v_1 - 24 \text{ V}}{12 \Omega} + \frac{v_1 - 0 \text{ V}}{30 \Omega} + \frac{v_1 - 0 \text{ V}}{20 \Omega} = 0 \text{ V}$$

or, if we group terms multiplying v_1 and put constants on the right,

$$v_1 \left(\frac{1}{12 \Omega} + \frac{1}{30 \Omega} + \frac{1}{20 \Omega} \right) = \frac{24 \text{ V}}{12 \Omega} = 2 \text{ A}$$

or, multiply by the common denominator,

$$60 \Omega \cdot v_1 \left(\frac{1}{12 \Omega} + \frac{1}{30 \Omega} + \frac{1}{20 \Omega} \right) = 60 \Omega \cdot 2 \text{ A}$$

or

$$v_1(5 + 2 + 3) = 120 \text{ V}$$

or

$$v_1 = \frac{120 \text{ V}}{10} = 12 \text{ V}$$

b) First, we calculate the parallel resistance of the 20 Ω and 30 Ω :

$$20 \Omega \parallel 30 \Omega = 10 \Omega \cdot 2 \parallel 3 = 10 \Omega \frac{2(3)}{2+3} = 10 \Omega \frac{6}{5} = 12 \Omega$$

The voltage divider formula gives the following result that agrees with the previous answer:

$$v_1 = 24 \text{ V} \frac{12 \Omega}{12 \Omega + 12 \Omega} = 12 \text{ V}$$

NOTE: For the voltage divider, the 12 Ω on top is from 20 $\Omega \parallel 30 \Omega$.