
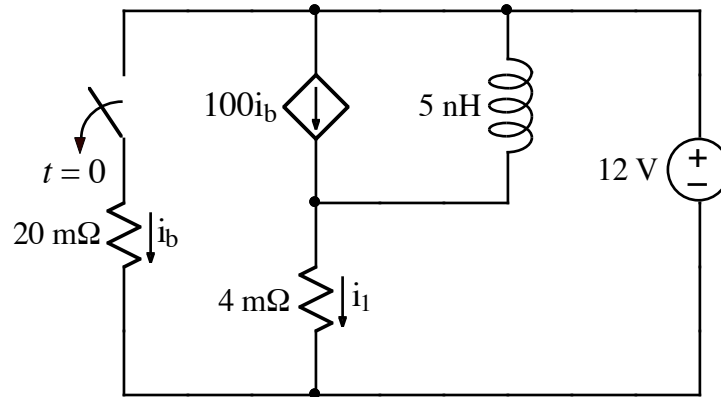


Ex:

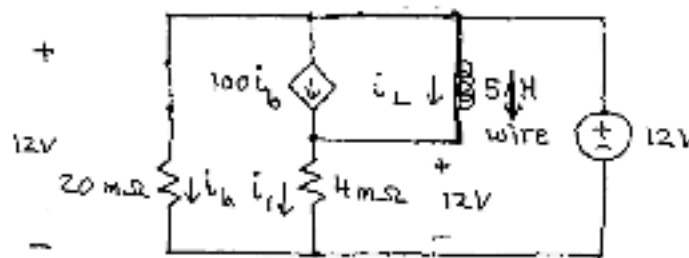

After being closed for a long time, the switch opens at $t = 0$. Find $i_1(t)$ for $t > 0$.

sol'n: $t = 0^-$ model: (to find $i_L(0^-)$) L acts like wire



We see that the 12V source is across the $20\text{ m}\Omega$ and the $4\text{ m}\Omega$.

$$\therefore i_b = \frac{12\text{V}}{20\text{ m}\Omega} = 600\text{ A}$$

$$\text{and } 100 i_b = 100 \cdot 600\text{ A} = 60\text{ kA}.$$

$$i_1 = \frac{12\text{V}}{4\text{ m}\Omega} = 3\text{ kA}$$


We find i_L from a current sum at the center node.

$$-100i_b + i_1 - i_L(0^-) = 0 \text{ A}$$

$$-60 \text{ kA} + 3 \text{ kA} = i_L(0^-)$$

$$\text{or } i_L(0^-) = -57 \text{ kA}$$

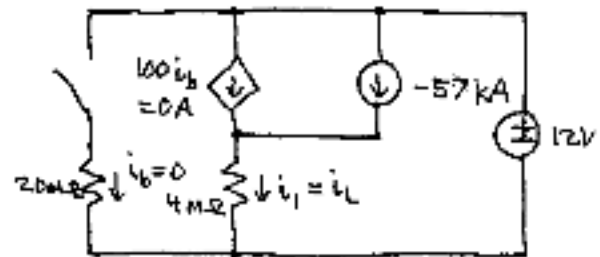$t = 0^+$ model: $i_L(0^+) = i_L(0^-) = -57 \text{ kA}$
 L modeled as current source




Because of the open circuit on the left, we have $i_b = 0$ and $100i_b = 0$.

From a current summation at the center node, we have $i_1(0^+) = i_L(0^+) = -57 \text{ kA}$.

$$i_1(0^+) = -57 \text{ kA}$$

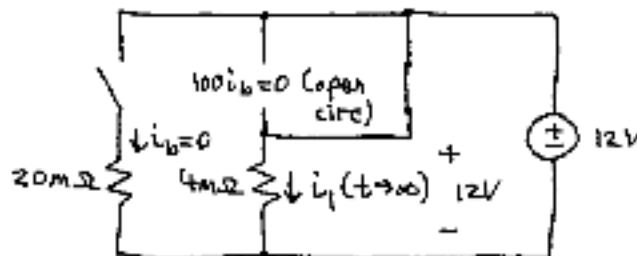
$t \rightarrow \infty$ model: (to find $i_1(t \rightarrow \infty)$) L acts like wire




We have 12V across the $4\text{ m}\Omega$.

$$i_1(t \rightarrow \infty) = \frac{12\text{V}}{4\text{ m}\Omega} = 3\text{ kA}$$

model for $\tau = L/R_{\text{Th}}$:

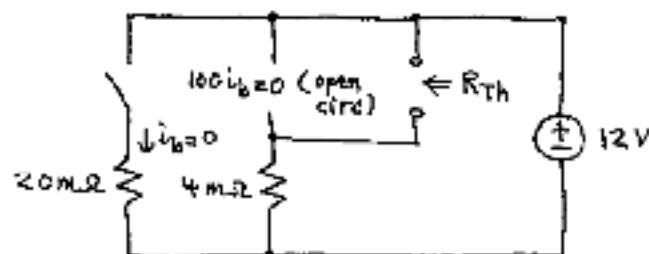

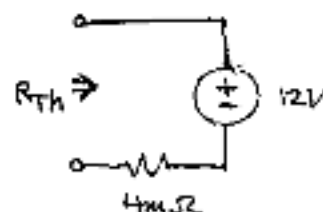We observe that the Thevenin equivalent seen from the terminals where the L is connected is just the $4\text{ m}\Omega$ and 12V:



We find R_{Th} by turning off the 12V source, causing it to be a wire. We see $R_{\text{Th}} = 4\text{ m}\Omega$. (The circuit is already a Thevenin equivalent.)

$$\therefore \tau = \frac{L}{R_{\text{Th}}} = \frac{5\text{ nH}}{4\text{ m}\Omega} = 1.2\text{ }\mu\text{s}$$

Now we use the general form of solution:

$$i_1(t) = i_1(t \rightarrow \infty) + [i_1(0^+) - i_1(t \rightarrow \infty)] e^{-t/\tau}$$

$$\text{or } i_1(t) = 3 \text{ kA} + [-57 \text{ kA} - 3 \text{ kA}] e^{-t/1.2 \mu\text{s}}$$

$$\text{or } i_1(t) = 3 \text{ kA} + -60 \text{ kA} e^{-t/1.2 \mu\text{s}}$$