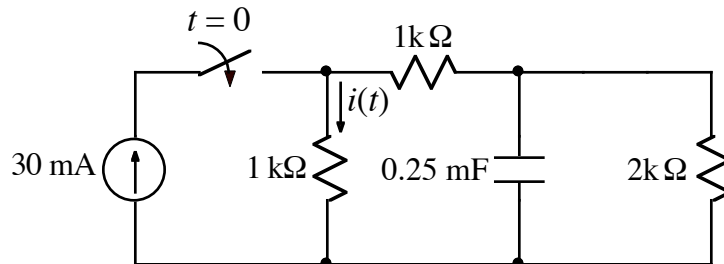



Ex:



After being open for a long time, the switch closes at $t = 0$.

Calculate the energy stored on the capacitor as $t \rightarrow \infty$.

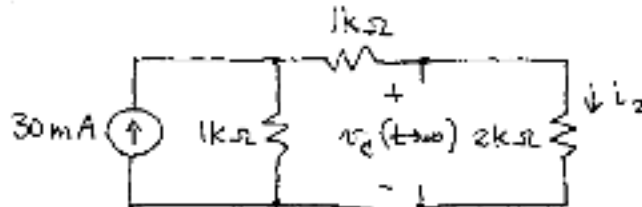sol'n: We use the general solution approach and treat C as an open circuit as $t \rightarrow \infty$.



We observe that v_c is the same as the voltage across the $2\text{ k}\Omega$ resistor, $i_2 \cdot 2\text{ k}\Omega$:

$$v_c(t \rightarrow \infty) = i_2 \cdot 2\text{ k}\Omega$$

To find i_2 , we use a current divider:

$$i_2 = 30\text{ mA} \cdot \frac{1\text{ k}\Omega}{1\text{ k}\Omega + 1\text{ k}\Omega + 2\text{ k}\Omega} = 7.5\text{ mA}$$

1 kΩ on left side

$$v_c(t \rightarrow \infty) = 7.5\text{ mA} \cdot 2\text{ k}\Omega = 15\text{ V}$$

$$\text{Energy on C} \equiv w_c = \frac{1}{2} C v_c^2 = \frac{1}{2} \cdot \frac{1}{4}\text{ mF} \cdot (15\text{ V})^2$$

$$w_c = 28.125\text{ mJ}$$