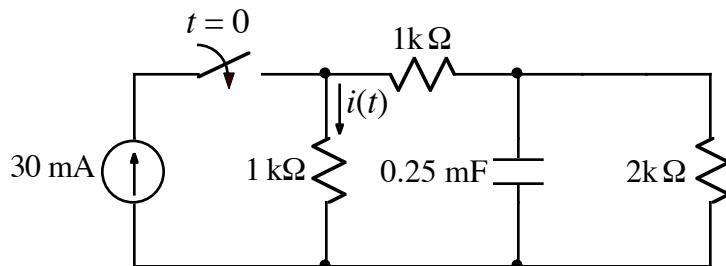


Ex:


After being open for a long time, the switch closes at $t = 0$.

Write a numerical expression for $i(t)$ for $t > 0$.

Sol'n: We use the general form of solution:

$$i(t) = i(t \rightarrow \infty) + [i(t=0^+) - i(t \rightarrow \infty)] e^{-t/R_{Th}C}, \quad t > 0$$

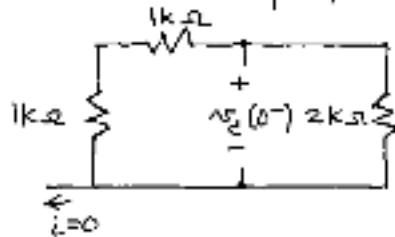$t=0^-$ models: $C = \text{open circuit}$, find $v_C(0^-)$
switch open, 30mA disconnected




Since there is no power source and there is a resistor across C to discharge it, we must have

$$v_C(0^-) = 0V$$


Note: No current can flow in the single wire to the left since that would cause charge to accumulate in that part of the circuit. There is no complete circuit.

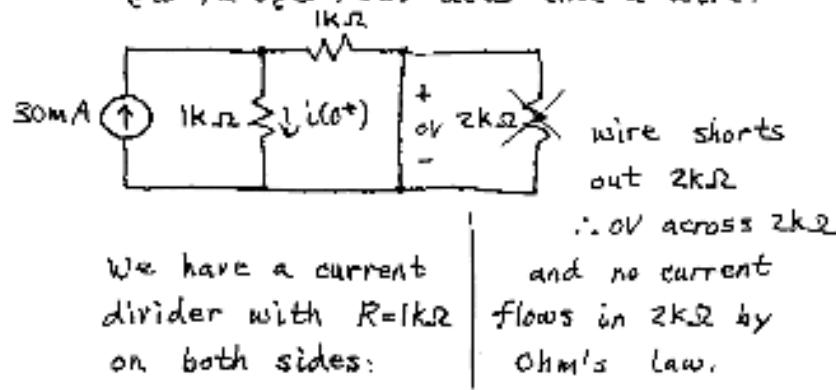$t=0^+$: $v_c(t=0^+) = v_c(t=0^-)$ since the energy variable v_c cannot change instantly. We model C as a v -src for the instant in time $t=0^+$.
 $v_c(0^+) = v_c(0^-) = 0V$ acts like a wire.



$$i(0^+) = 30mA \cdot \frac{1k\Omega}{1k\Omega + 1k\Omega} = 15mA$$

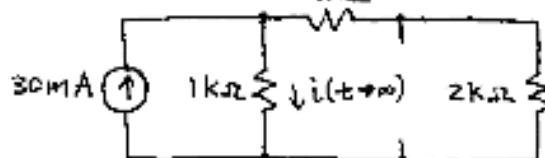$t \rightarrow \infty$: C acts like open circuit




We have a current divider with $1k\Omega$ on left and $1k\Omega + 2k\Omega = 3k\Omega$ on right.


$$\therefore i(t \rightarrow \infty) = 30mA \cdot \frac{3k\Omega}{1k\Omega + 3k\Omega} = 22.5mA$$

$\tau = R_{TH} C$: We find R_{TH} looking into terminals where C is connected.

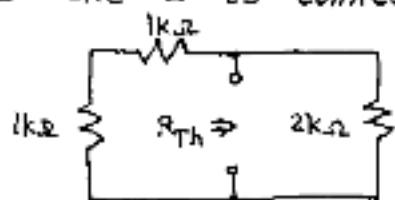In this circuit, we need only turn off the independent source and look into the circuit from the terminals where the C is connected to find R_{Th} .



We may redraw the circuit as follows:

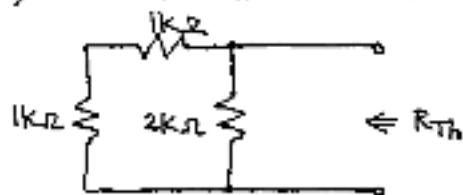

We have

$$R_{Th} = 2k\Omega \parallel (1k\Omega + 1k\Omega) = 1k\Omega$$

$$R_{Th}C = 1k\Omega \cdot 0.25\text{ mF} = 0.25\text{ s}$$

Combining results, we have our final answer:

$$i(t) = 22.5\text{ mA} + (15\text{ mA} - 22.5\text{ mA}) e^{-t/0.25\text{ s}}, \quad t > 0$$