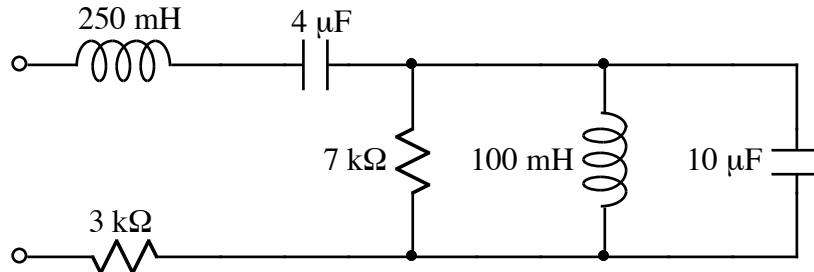


**Ex:** Find the total impedance of the circuitry shown below if  $\omega = 1000$  rad/s.



**SOL'N:** We convert to the frequency-domain by computing impedances.


$$j\omega L = j1k \cdot 250m \Omega = j250 \text{ k}\Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j1k \cdot 4\mu} \Omega = -j250 \Omega$$

$$j\omega L = j1k \cdot 100m \Omega = j100 \text{ k}\Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j1k \cdot 10\mu} \Omega = -j100 \Omega$$

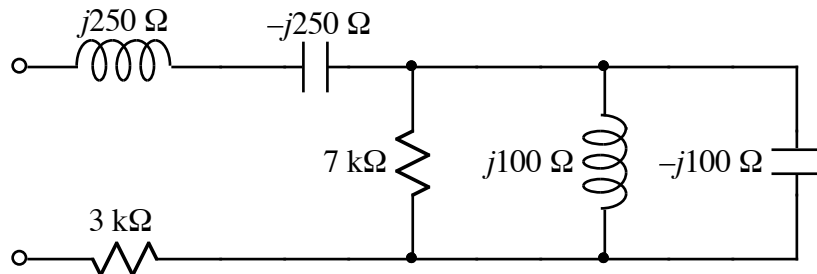
The circuit diagram in the frequency-domain is shown below.



The series  $L$  and  $C$  in series at the top left of the circuit sum to zero, which means they cancel out to act like a wire. The parallel  $L$  and  $C$  at the right combine to create an equivalent impedance of infinity, or an open circuit.

$$j100 \parallel -j100 \Omega = j100 \Omega \cdot 1 \parallel -1 = j100 \Omega \cdot \frac{1(-1)}{1-1} = j100 \Omega \cdot \frac{1}{0} = \infty \Omega$$

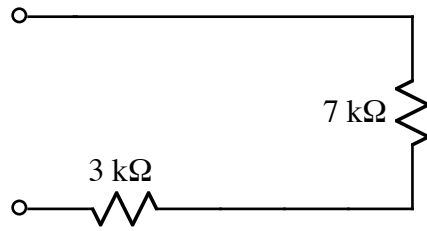Thus, the  $L$  and  $C$  on the right disappear. We are left with a simple circuit consisting of only two resistors:



The equivalent impedance is obviously 10 kΩ.

$$z_{\text{tot}} = 10 \text{ k}\Omega$$