
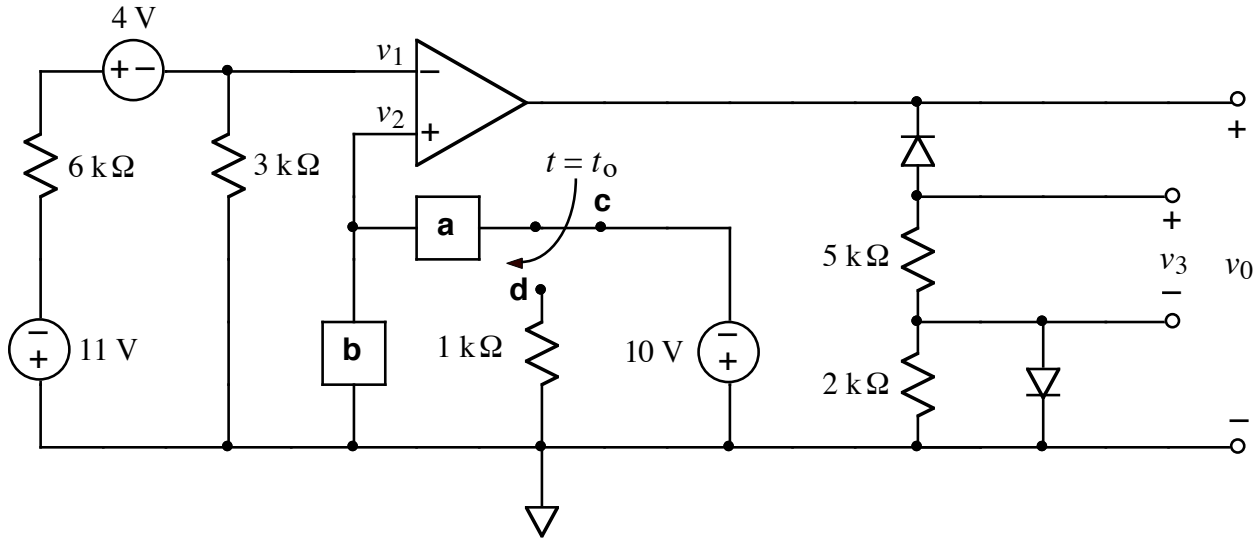


Ex:

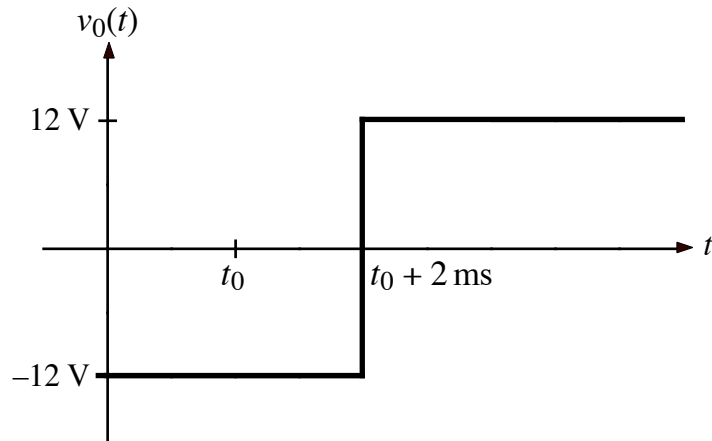

After being in position **c** for a long time, the switch moves from **c** to **d** at  $t = t_0$ .

Rail voltages =  $\pm 12$  V



- Choose either an  $R$  or  $C$  to go in box **a** and either an  $R$  or  $C$  to go in box **b** to produce the  $v_0(t)$  shown above. (Note that  $v_0$  stays high forever after  $t_0 + 2$  ms.) Specify which element goes in each box and its value.
- Sketch  $v_1(t)$ , showing numerical values appropriately.
- Sketch  $v_2(t)$ , showing numerical values appropriately.
- Sketch  $v_3(t)$ . Show numerical values for  $t < t_0$ , for  $t_0 < t < t_0 + 2$  ms, and for  $t_0 + 2$  ms  $< t$ . Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: a) For  $v_o$  to be low, (i.e.,  $-12V$ ), we must have  $v_2 < v_1$ .

To find  $v_1$ , we slide the  $4V$  source through the  $6k\Omega$  resistor and find that we have the equivalent of a  $-15V$  source and a voltage divider formed by the  $3k\Omega$  and  $6k\Omega$  resistors.

$$v_1 = -15V \cdot \frac{3k\Omega}{3k\Omega + 6k\Omega} = -5V$$

At  $t=0^-$ , we must have  $v_2 < -5V$ .

$a=R$   
 $b=C$   $\left[ \begin{array}{l} \text{This is possible only if box } \mathbf{a} \\ \text{contains a resistor and box } \mathbf{b} \\ \text{contains a capacitor. If } \mathbf{a} \text{ is} \\ \text{an } R \text{ and } \mathbf{b} \text{ is a } C, \text{ then the} \\ C \text{ will charge until } v_2 = -10V < v_1. \end{array} \right.$

When the switch moves from  $c$  to  $d$ , the capacitor voltage start charging toward  $0V$ , but it will still be  $-10V$  initially. This gives the desired waveform for  $v_o(t)$ :  $v_o$  will go high when  $v_2 = v_1 = -5V$ .

Note: The reasons why other components in boxes  $a$  and  $b$  fail to yield the desired  $v_o(t)$  are as follows:


---

$a = R$  and  $b = R$  cannot give a waveform that changes after a delay.  $v_o$  would have to change instantly at  $t = t_0$ .

$a = C$  and  $b = R$  would result in  $C$  charging until no current flows in  $R$ . This means  $v_2 = 0V$ , or  $v_2 > v_1$ , causing  $v_o$  to be high before  $t = t_0$ .

$a = C$  and  $b = C$  would result in an arbitrary voltage at  $v_2$ . The total voltage drop across the two  $C$ 's would be  $10V$ . When the switch changes from  $c$  to  $d$ , the capacitors would charge until the total voltage drop across them was  $0V$ . The same current would flow in both  $C$ 's, causing a voltage change that would be inversely proportional to the  $C$  values. The waveform shown for  $v_o(t)$  could be produced, but there is a lack of control over the initial value of  $v_2$ . This would make the timing of the  $v_o(t)$  waveform uncertain. Thus, we reject this solution.

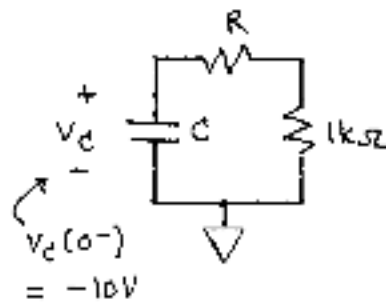Now we find possible values for  $R$  and  $C$ . We have the following circuit model for  $t > t_0$ :



$$v_c(t > t_0) = v_c(t \rightarrow \infty) + \left[ v_c(t_0^+) - v_c(t \rightarrow \infty) \right] e^{-t/\tau}$$

$\parallel$                        $\parallel$                        $\parallel$   
 $0V$                        $-10V$                        $0V$

$$v_c(t > t_0) = -10 e^{-t/\tau} \text{ V (where we take } t_0 = 0)$$

$$\text{where } \tau = (R + 1k\Omega) C$$

$$\text{We want } v_c(t = 2\text{ms}) = v_1 = -5V$$

$$\text{or } -10 e^{-2\text{ms}/\tau} = -5V$$

$$e^{-2\text{ms}/\tau} = \frac{1}{2}$$


$$-2\text{ms} = \tau \ln \frac{1}{2}$$

$$\tau = \frac{2\text{ms}}{\ln 2} \approx 2.9\text{ms}$$


One sol'n is  $R = 1.9k\Omega$  and  $C = 1\mu F$ .

Note:  $R = 0\Omega$  is min  $R$ ,  $C = 2.9\mu F$  is max  $C$ .


b)  $v_1(t) = -5V$  as shown earlier.

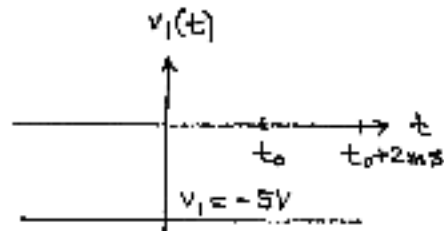

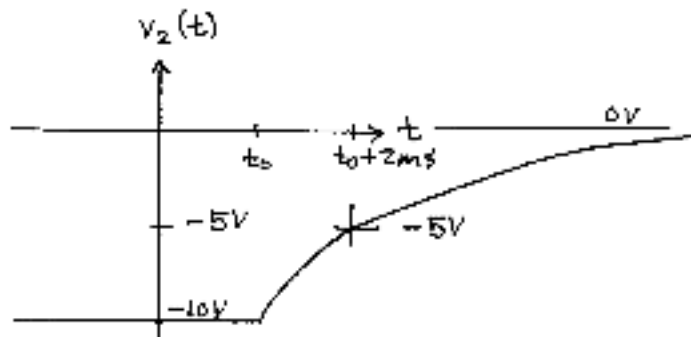c)  $v_2 = v_c(t > 0) = -10V e^{-t/2.9ms}$  from (a)



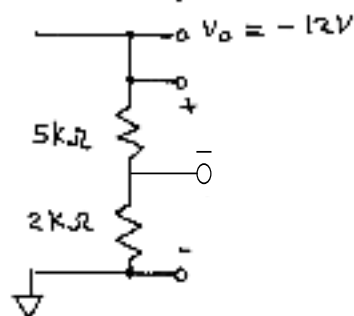d) When  $v_o$  is low, the top diode will act like a wire and the bottom diode will act like an open circuit.



We have a voltage divider:  $v_3 = -12V \cdot \frac{5k\Omega}{2k\Omega + 5k\Omega} = -\frac{60}{7}V$ .

---

When  $v_0$  is high, the top diode will act like an open circuit, leaving the bottom part of the circuit disconnected from  $v_0$ , (or any other power source).

Thus  $v_3 = 0V$  when  $v_0$  is high.

