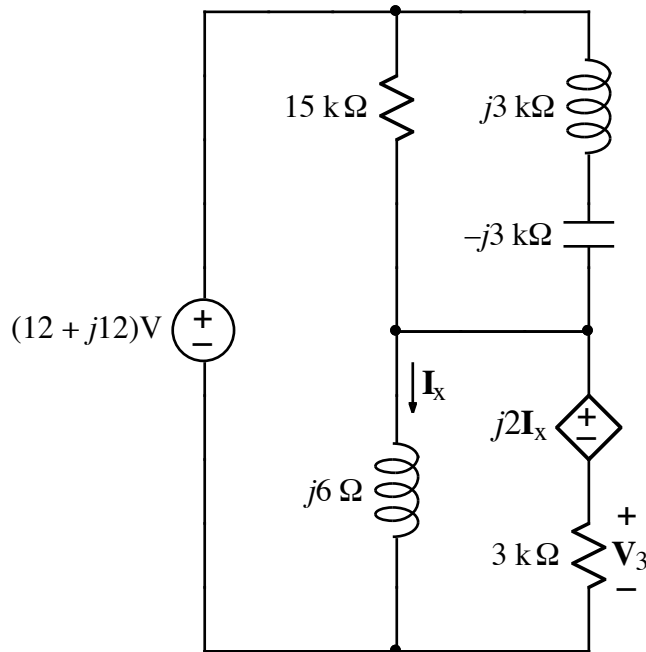


Ex:




- A frequency-domain circuit is shown above. Write the value of phasor \mathbf{V}_3 in polar form.
- Given $\omega = 37$ rad/s, write a numerical time-domain expression for $v_3(t)$, the inverse phasor of \mathbf{V}_3 .

sol'n: a) The $j3k\Omega$ and $-j3k\Omega$ sum to $0\Omega = \text{wire}$.

Thus, the $15k\Omega$ is bypassed by a short and may be ignored.

It also follows that the $12+j12$ V is directly across the $j6\Omega$ and directly across the $j2I_x$ source in series with the $3k\Omega$ resistor.

Our circuit model is as follows:

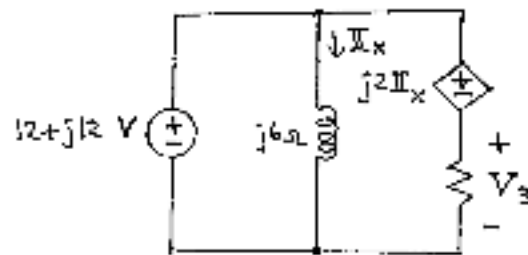

By Ohm's law, $I_x = \frac{12 + j12 \text{ V}}{j6 \Omega} = \frac{2(1+j)}{j} \text{ A}$

or $I_x = -j2(1+j) \text{ A}$

or $I_x = 2 - j2 \text{ A}$


It follows that $j2I_x = j2(2 - j2) \text{ V} = 4 + j4 \text{ V}$.

From a v-loop around the outside of the circuit, we have the following:

$$V_3 = (12 + j12) \text{ V} - (4 + j4) \text{ V}$$

or $V_3 = 8 + j8 \text{ V}$

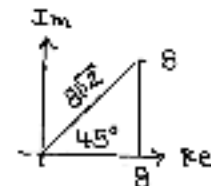or $V_3 = 8\sqrt{2} \angle 45^\circ \text{ V}$



b) $v_3(t) = \mathcal{P}^{-1} [8\sqrt{2} \angle 45^\circ \text{ V}], \quad \omega = 37 \text{ rad/s}$

$$v_3(t) = 8\sqrt{2} \cos(37t + 45^\circ) \text{ V}$$