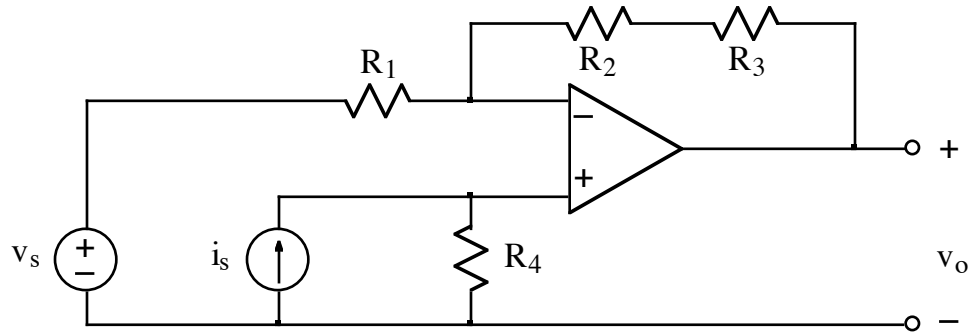



Ex:



The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for v_o in terms of not more than v_s , i_s , R_1 , R_2 , R_3 , and R_4 .

sol'n We treat the op-amp as ideal, meaning we remove it and replace the output with a source called v_o and assume a 0V drop across the +, - inputs.

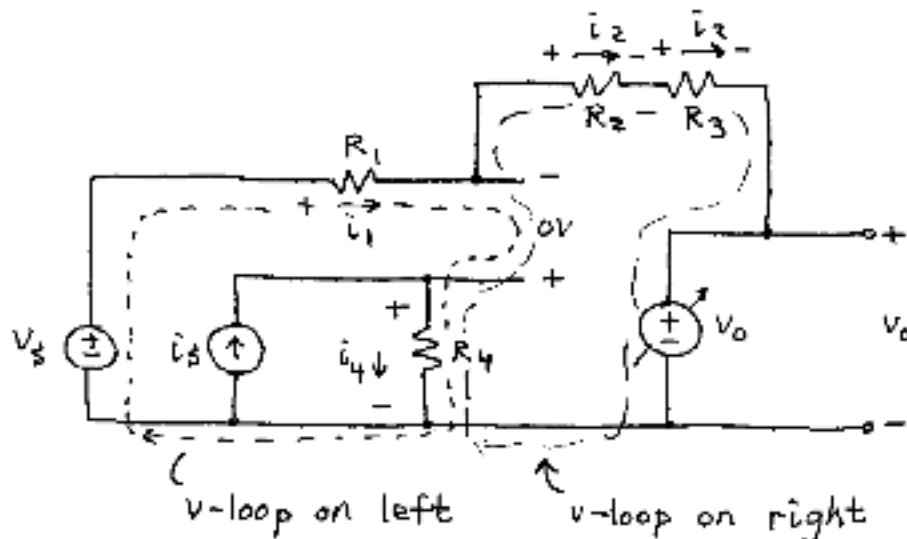After that, we take v -loops on the left and right that pass thru the 0V drop across the +, - inputs. We also take current sums at nodes.



For the v-loops, we have:

$$v_s - i_1 R_1 + 0V - i_4 R_4 = 0V \quad \text{(on)}$$

$$+ i_4 R_4 - 0V - i_2 R_2 - i_2 R_3 - v_o = 0V \quad \text{(on)}$$

Note: we use Ohm's law to write v-drop in terms of currents.

For current sums at nodes we have (for node to right of R_1):

$$-i_1 + i_2 + 0A = 0A \quad \text{or } i_1 = i_2$$

↑
no current into op-amp

For node above R_4 :

$$-i_3 + i_4 + 0A = 0A \quad \text{or } i_4 = i_3$$

↑
no current into op-amp

Substituting into v-loop eq'ns, we have

$$v_s - i_2 R_1 - i_3 R_4 = 0V$$

$$\text{and } i_3 R_4 - i_2 R_2 - i_2 R_3 = v_o.$$

The first eq'n gives $i_2 = \frac{v_s - i_3 R_4}{R_1}$.

Using this in the 2nd eq'n gives

$$v_o = i_3 R_4 - \left(\frac{v_s - i_3 R_4}{R_1} \right) (R_2 + R_3)$$

$$\text{or } v_o = i_3 R_4 \left(1 + \frac{R_2 + R_3}{R_1} \right) - v_s \frac{R_2 + R_3}{R_1}$$