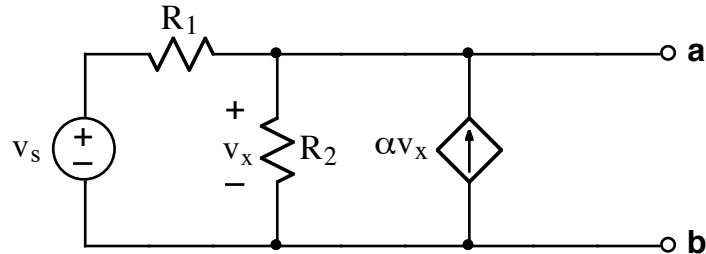


Ex:



Find the Thevenin equivalent circuit at terminals a-b. v_x must not appear in your solution. **Hint:** use the node-voltage method.

sol'n: $V_{Th} = V_{a,b}$ open circuit

We may use any method we desire to solve for V_{Th} . Here, we use the node-voltage method.

$$v_x = v_{Th} - 0V = v_{Th} \text{ for dependent src}$$

Current sum for v_{Th} node (dashed bubble):


$$\frac{v_{Th} - v_s}{R_1} + \frac{v_{Th}}{R_2} - \alpha v_{Th} = 0 \text{ A}$$

$$\text{or } v_{Th} \left(\frac{1}{R_1} + \frac{1}{R_2} - \alpha \right) = \frac{v_s}{R_1}$$

$$\text{or } v_{Th} = \frac{v_s}{R_1} \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} - \alpha}$$

$$v_{Th} = \frac{v_s}{1 + \frac{R_1}{R_2} - \alpha R_1} \text{ or } \frac{v_s \cdot R_1 \parallel R_2}{R_1} \frac{-1}{\alpha}$$

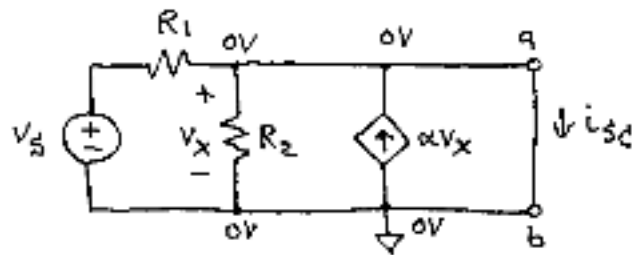
To find R_{Th} , we short a to b and find the short-circuit current, i_{sc} , that flows from a to b.



The wire from a to b means the top rail is at 0V. Thus, $V_X = 0V - 0V = 0V$

Also, it follows that $\alpha V_X = 0$ so the dependent current source effectively disappears.

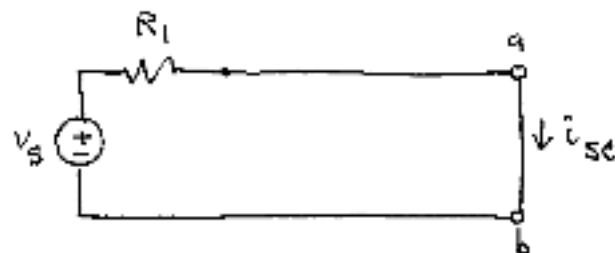Furthermore, R_2 is bypassed by the short, meaning no current flows in R_2 . Our equivalent circuit model is as follows:



$$\text{We have } i_{sc} = \frac{V_S}{R_1}.$$


$$\text{Now we use the formula } R_{Th} = \frac{V_{Th}}{i_{sc}}.$$

$$R_{Th} = \frac{V_s}{\frac{1 + \frac{R_1}{R_2} - \alpha R_1}{R_2}} = \frac{R_1}{1 + \frac{R_1}{R_2} - \alpha R_1}$$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} - \alpha}$$

or $R_1 \parallel R_2 \parallel -\frac{1}{\alpha}$

Thevenin equivalent circuit:

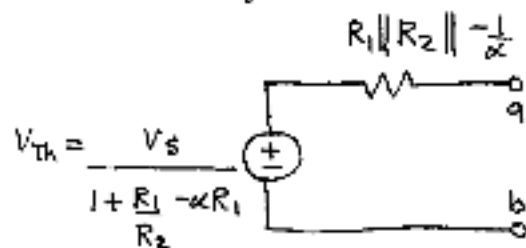

Note: In this circuit, we have voltage $-V_x$ across the dependent source and can use Ohm's law to find a resistance equivalent to the dependent source:

$$R_{eq} = \frac{-V_x}{\alpha V_x} = -\frac{1}{\alpha}$$

We can use R_{eq} in place of the dependent src, leading to a simpler solution for V_{Th} from a v-divider and for R_{Th} from looking into the a,b terminals with V_s off.