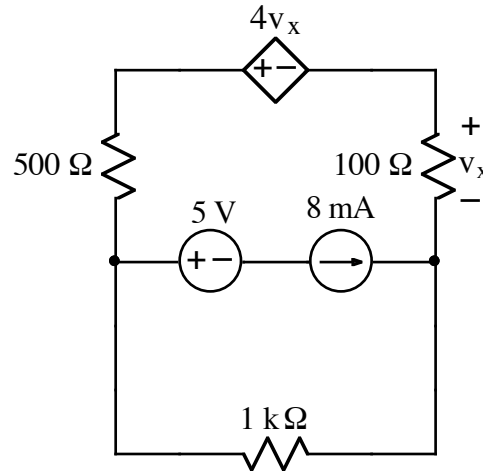



Ex:



Calculate the power dissipated by the dependent voltage source, (labeled  $4v_x$ ).

sol'n: Any method of solution is acceptable.  
Here, we'll use the node-voltage method.

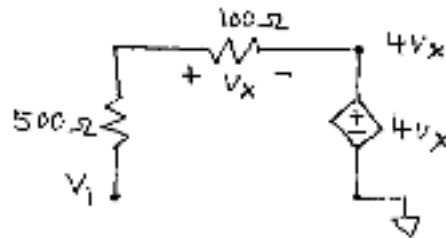First, we find  $v_x$  in terms of node voltages. If we slide the  $100\Omega$  resistor thru the dependent source, we get the following view of the top branch:



We can find  $v_x$  by using a v-divider:

$$-v_x = \frac{(4v_x - v_1) 100\Omega}{100\Omega + 500\Omega}$$

$$\text{or } \frac{2}{3}v_x + v_x = \frac{v_1}{6}$$

$$\text{or } \frac{4}{5} V_x = \frac{V_1}{6}$$

$$\text{or } V_x = \frac{V_1}{6} \cdot \frac{3}{5} = \frac{V_1}{10}$$

For the node-voltage eq'n, we have the following:

$$\frac{\left( V_1 - 4 \frac{V_1}{10} \right)}{100\Omega + 500\Omega} + 8\text{mA} + \frac{V_1 - 0\text{V}}{1\text{k}\Omega} = 0\text{A}$$

Note: The 5V src has no effect as it is in series with a current source.

Now we solve for  $V_1$ .

$$V_1 \left( \frac{1 - \frac{4}{10}}{600\Omega} + \frac{1}{1\text{k}\Omega} \right) = -8\text{mA}$$

$$\text{or } V_1 \left( \frac{0.6}{600\Omega} + \frac{1}{1\text{k}\Omega} \right) = -8\text{mA}$$

$$\text{or } V_1 = \frac{-8\text{mA}}{\frac{2}{1\text{k}\Omega}} = \frac{-8\text{mA} \cdot 1\text{k}\Omega}{2} = -4\text{V}$$

$$\text{Thus, } 4V_x = 4 \cdot \frac{V_1}{10} = -1.6\text{V.}$$

To find the current thru the  $4V_x$  src, we use a term from the node-v eq'n:

$$i = \frac{V_1 - 4V_x}{100\Omega + 500\Omega} = \frac{-4V - (-1.6V)}{600\Omega}$$

$$\text{or } i = \frac{-4 + 1.6}{600\Omega} V = \frac{-2.4V}{600\Omega} = -4 \text{ mA}$$

The power dissipated is  $p = i \cdot 4V_x$

$$p = -4 \text{ mA} \cdot (-1.6V)$$

$$p = +6.4 \text{ mW}$$

Note: In this problem, the dependent source is equivalent to a resistor. That is, we can write both the voltage and current for the source as  $V_x$  multiplied by a constant. In particular, the current for the  $4V_x$  source is the same as the current in the  $100\Omega$  resistor and is  $i = \frac{V_x}{100\Omega}$ .

Using Ohm's Law, we have the following expression for the resistor that is equivalent to the source:

$$R_{eq} = \frac{4V_x}{i} = \frac{4V_x}{\frac{V_x}{100\Omega}} = 400\Omega$$

We may use  $400\Omega$  in place of the dependent src and solve the problem as an i-divider.