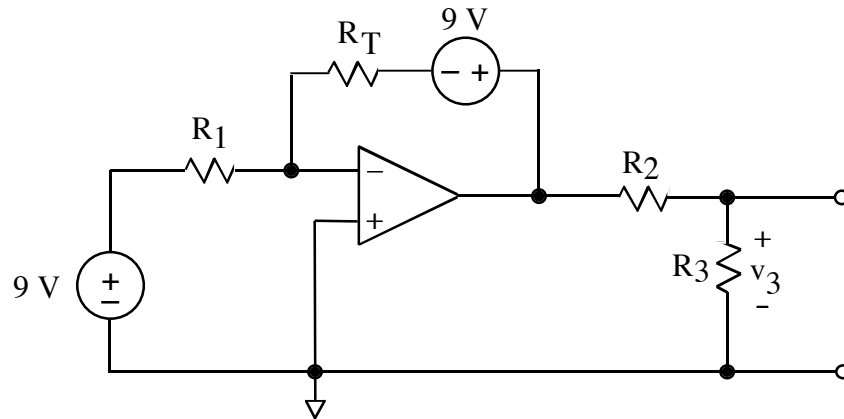


1. (75 points)



Rail voltages = ± 8 V

Design an electronic thermometer using the circuit diagram shown above. The voltage v_3 is used to indicate temperature. Use a thermistor with a resistance described by

$$R_T = R_o e^{2000 \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_o = 12 \text{ k}\Omega$ and T is temperature in $^\circ\text{K}$.


a. Choose circuit components that will produce the following:

$$\begin{array}{lll} v_3 = 0 \text{ V} & \text{when} & T = 273^\circ\text{K} \\ v_3 = 1 \text{ V} & \text{when} & T = 373^\circ\text{K}. \end{array}$$


Be sure the operational amplifier would not saturate. Explain your work carefully.

b. Using the component values you chose above, calculate v_3 when $T = 323^\circ\text{K}$. Make a rough sketch of v_3 vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response. Comment on the quality of the response compared to the desired linear response.

2. (70 points)

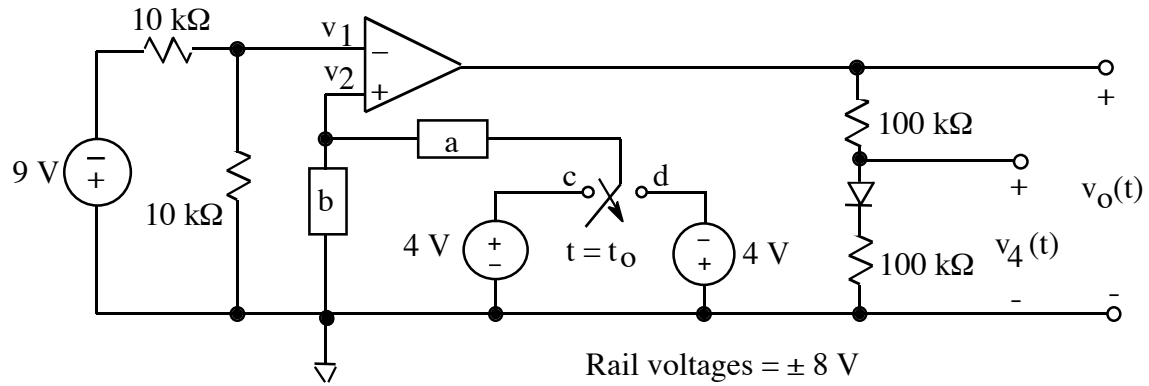

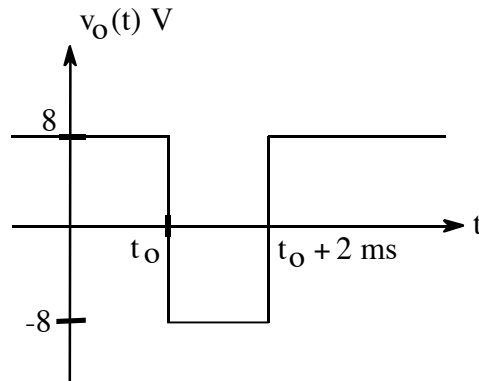
After having been c for a long time, the switch is moved to position d at $t = t_0$.



- Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_o(t)$ shown in the diagram. Specify which element goes in each box, and specify each value.
- Sketch $v_2(t)$, the voltage across the circuit element in box b. Show numerical values appropriately.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_4(t)$. Show numerical values for $t < t_0$, for $t_0 < t < (t_0 + 2\text{ ms})$, and for $t > (t_0 + 2\text{ ms})$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reversed biased, its resistance is infinite.


Explain your work carefully.

3. (30 points)

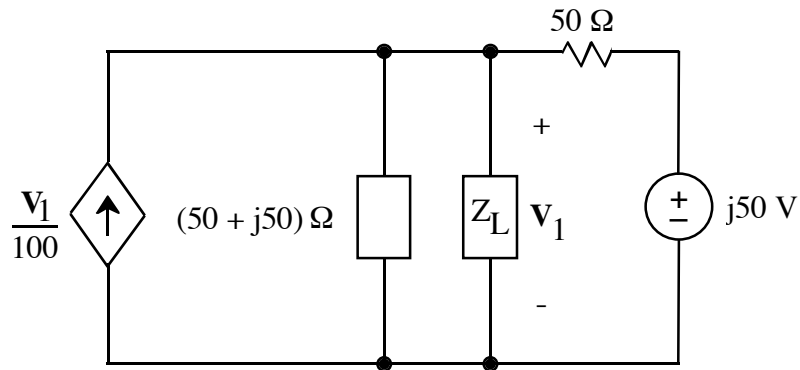

- a. Choose the value of Z_L that will absorb maximum average power.
- b. Calculate the value of that maximum average power absorbed by Z_L .

4. (25 points)

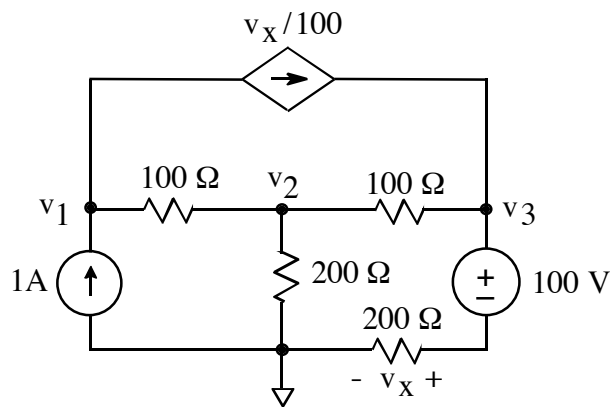

- a. Write an equation for the node voltages v_1 , v_2 , and v_3 in the form:

$$g_{11}v_1 + g_{12}v_2 + g_{13}v_3 = i_1$$

$$g_{21}v_1 + g_{22}v_2 + g_{23}v_3 = i_2$$

$$g_{31}v_1 + g_{32}v_2 + g_{33}v_3 = i_3$$

List the numerical values of g_{ij} 's and i_j 's.