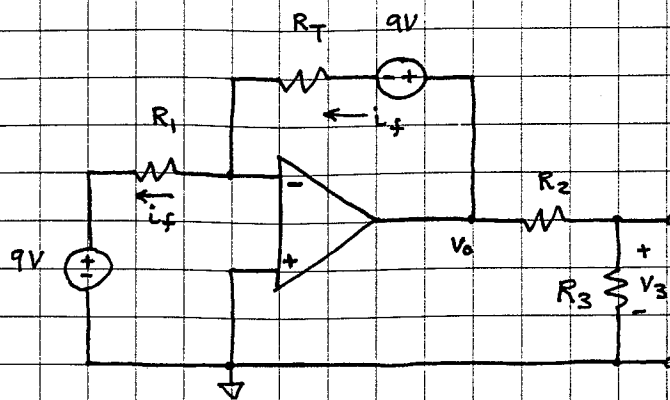


1.



Rail voltages $\pm 8V$

$$R_T = R_o e^{2000 \left(\frac{1}{T} - \frac{1}{300} \right)} \quad R_o = 12k\Omega \quad T \text{ in } ^\circ K$$

- a) Choose components that give $V_3 = 0V$ when $T = 273^\circ K$
 $V_3 = 1V$ when $T = 373^\circ K$

sol'n: First we ^{find} V_3 as a function of R_T . Assume linear mode and ideal op-amp:

- 1) $V_p = 0V$ Always find V_+ (i.e. V_p) first
(or V_+ if you prefer to call it that)
- 2) $V_n = V_p = 0V$ $V_- = V_+$ (i.e. $V_n = V_p$) for linear mode
- 3) i_f thru R_T and $9V$ in feedback = i_f thru R_1 and $9V$ on left since i_n (or i_-) = $0A$ (no input current).

Call op-amp output v_o .

$$i_f = \frac{v_o - 9V - v_n}{R_T} = \frac{v_o - 9V}{R_T} \quad \text{for feedback}$$

$$i_f = \frac{v_n - 9V}{R_1} = \frac{-9V}{R_1} \quad \text{for input } v_n \text{ from left}$$

$$\therefore \frac{v_o - 9V}{R_T} = \frac{-9V}{R_1} \quad \text{or} \quad \frac{v_o}{R_T} = 9V \left(\frac{1}{R_T} - \frac{1}{R_1} \right)$$

$$v_o = 9V \left(1 - \frac{R_T}{R_1} \right)$$

1. a) (cont)

$$V_o = 0V \text{ when } R_T = R_1$$

$$V_3 = \frac{V_o \cdot R_3}{R_2 + R_3} = 0 \text{ when } V_o = 0V$$

$$\text{So } R_1 = R_T(T=273^\circ K) = 12k e^{2000\left(\frac{1}{273} - \frac{1}{300}\right)} = 23.2k$$

$$\text{for } T=373^\circ K: V_o = 9V \left[1 - \frac{R_T(373^\circ K)}{23.2k} \right] = 9V \left[1 - \frac{12k e^{2000\left(\frac{1}{373} - \frac{1}{300}\right)}}{23.2k} \right]$$

$$\text{Note } R_T(373^\circ K) = 3.25k$$

$$V_o = 7.74V \text{ not quite saturated (but close!)}$$

$$\text{For } V_3 = 1V, \text{ we need } \frac{R_3}{R_2 + R_3} = \frac{1}{7.74}$$

$$\text{or } \frac{R_2 + R_3}{R_3} = 1 + \frac{R_2}{R_3} = 7.74$$

$$\therefore \frac{R_2}{R_3} = 6.74$$

$$\text{Use } R_2 = 6.74k\Omega \text{ (or } 6.8k \text{ if } 10\% R\text{'s required)}$$

$$R_3 = 1k\Omega$$

In practice we would use a $10k\Omega$ potentiometer for R_2 , or 510Ω in series with $1k\Omega$ pot for R_1 .

Note: Any R_2 and R_3 in the proper ratio is mathematically correct, but the values I chose limit the op-amp output current to $i_f + \frac{7.74V}{R_2 + R_3} = i_f + \frac{7.74V}{7.74k} = i_f + 1mA$


$$i_f \text{ is on the order of } \frac{7.74V - 9V}{3.25k} = -0.39mA$$

So we have $i_f \approx 2mA < 10mA$ (limit typical for max op-amp output current).

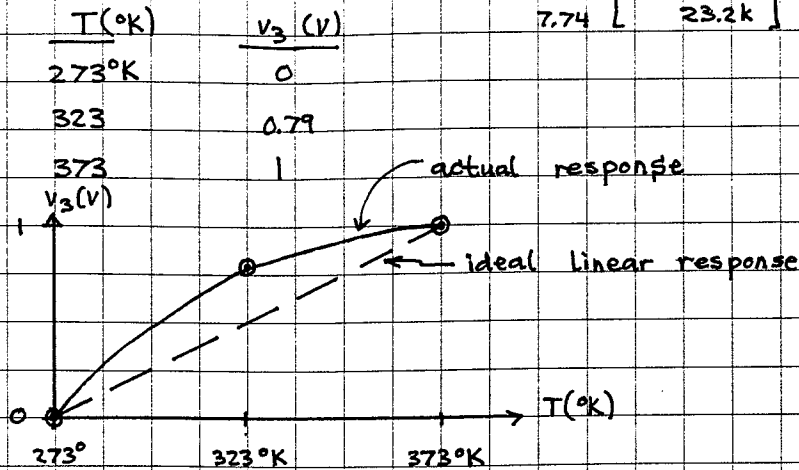1. b) Calculate R_T ($T = 323^\circ\text{K}$). Make rough sketch of v_3 vs T .
On same axes, plot ideal linear response. Comment on results.

$$\text{sol'n: } R_T(T = 323^\circ\text{K}) = 12\text{ k}\Omega \cdot \frac{2000 \left(\frac{1}{323} - \frac{1}{300} \right)}{1} = 7.46\text{ k}\Omega$$


$$v_3 = \frac{9\text{V}}{7.74} \left[1 - \frac{7.46\text{k}}{23.2\text{k}} \right] = 0.79\text{V}$$



Comment: The actual response is quite nonlinear.
It is off by $0.79\text{ actual} - 0.5\text{ desired} = 0.29$
at $T = 323^\circ\text{K}$. This is an error of $\frac{0.29}{0.50} \approx 60\%$.

This circuit would not be a good thermometer.


2.

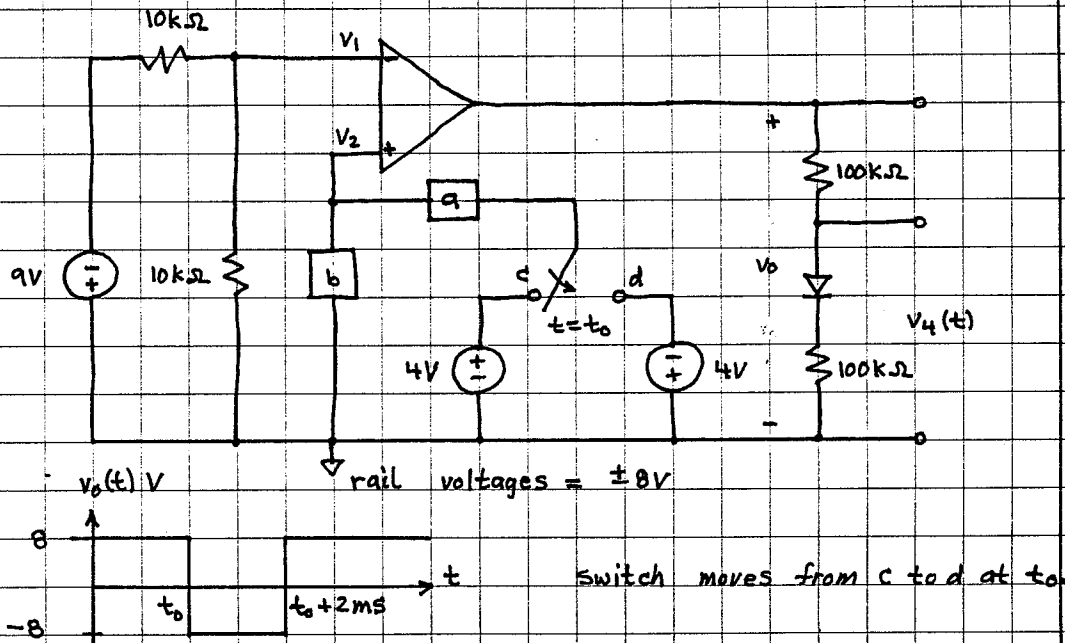

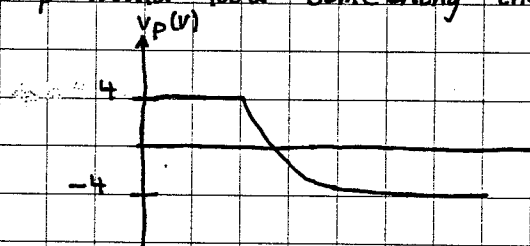2.a) Choose R or C for 'a' and 'b' to produce $v_o(t)$ as shown.

sol'n:
$$V_n = -9V \cdot \frac{10k\Omega}{10k\Omega + 10k\Omega} = -4.5V$$

To change the output to $-8V$ for the op-amp, we have to have $V_p < V_n = -4.5V$. If we put a C in 'b' and an R in 'a', then the C would charge up to $4V$ and down to $-4V$ when the switch goes from 'c' to 'd'. The voltage at V_p would look something like this:



We would never have $V_p < -4.5V$, so this is not the right solution.

The other choice is to put a C in 'a' and an R in 'b'. When the C is charged, we will have $+4V$ across the C and no current will be flowing at t_0^- . Since there is no current there will be no V drop across R, and $V_p = 0V$ for $t = t_0^-$.

When we switch from 'c' to 'd', we will start with $4V$ across C from 'c' to 'd'. Added to the $-4V$ source connected to 'd', we will have $V_p = -8V$ at $t = t_0^+$. This will give $V_p < V_n$ and cause the op-amp output to go negative, as desired.

Starting at t_0^+ , the C will start charging toward $-4V$ across C. When the C starts charging, the current thru (and V drop across) R will start declining exponentially to zero from an initial maximum of $8V/R$ (and V drop of $8V$).


2. a) (cont)




When v_p reaches the value of $v_n = -4.5V$, the output of the op-amp will again go high.

Thus, we get the behavior we are seeking.

\therefore Put a C in 'a' and R in 'b'.

The waveforms:

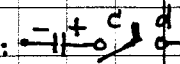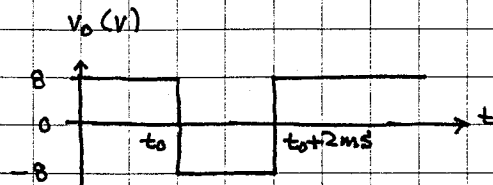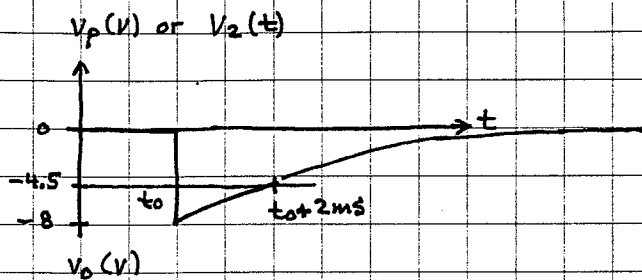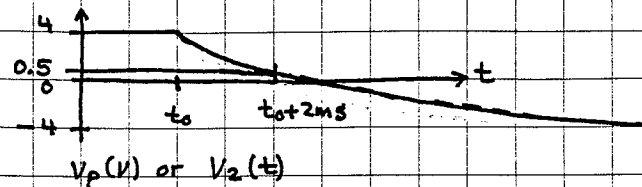$v_c(V) \leftarrow V$ across C with - on left + on right: 



The general sol'n for $v_p(t)$ is clearly $v_p(t) = -8ve^{-t'/RC}$, where $t' = 0$ when $t = t_0$, (i.e. shift time origin).

We want $v_p(t' = 2ms) = -4.5V$.

$$-4.5V = -8e^{-2ms/RC}$$

$$\ln \frac{4.5}{8} = -2ms/RC$$

$$RC = \frac{-2ms}{\ln \frac{4.5}{8}} = 3.5ms$$


$$C = 1\mu F \quad R = 3.5k \text{ (or } 3.6k \text{ } 10\% \text{ value)}$$

Other answers with $RC = 3.5ms$ acceptable if R not too small and C not too large.

2. b) Sketch $v_2(t)$. sol'n: see middle sketch on previous page.

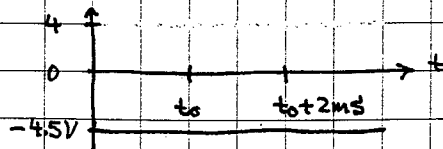c) Sketch $v_1(t)$.

sol'n: $v_1(t) = -9V \cdot \frac{10k\Omega}{10k\Omega + 10k\Omega} = -4.5V$ all the time




d) Sketch $v_4(t)$. Use ideal model of diode.

sol'n: When $v_0(t) > 0V$ the diode is forward biased and we have V-divider: (diode acts like wire)

$$v_4(t) = v_0(t) \cdot \frac{100k\Omega}{100k\Omega + 100k\Omega} = \frac{v_0(t)}{2} \quad v_0(t) > 0V$$

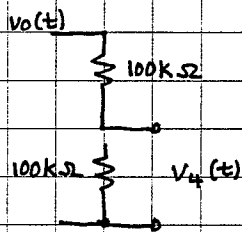When $v_0(t) < 0V$, the diode is reverse biased and acts like an open circuit:



Since there is no load, no current flows in the $100k\Omega$ in series with $v_0(t)$.

Thus, $v_4(t) = v_0(t)$ $v_0(t) < 0$.

