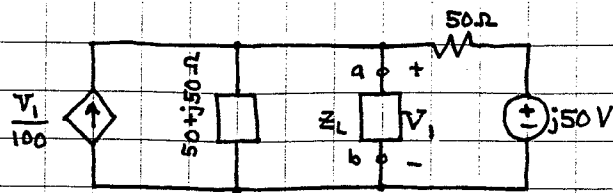


3.



a) Choose z_L that will absorb max ave power. Hint $z_L = z_{Th}^*$.

sol'n: Take Thevenin equivalent of circuit with respect to terminals a-b (without z_L).

V_{Th} = open circuit V_{a-b} or V_1 .

Use Node-V method to find V_1 :

$$-\frac{V_1}{100} + \frac{V_1}{50+j50\Omega} + \frac{V_1 - j50V}{50\Omega} = 0A$$

$$V_1 \left(-\frac{1}{100} + \frac{1}{50+j50\Omega} + \frac{1}{50\Omega} \right) = \frac{j50V}{50\Omega}$$

$$V_1 \left(-\frac{(50+j50\Omega)}{100} + 1 + \frac{50+j50\Omega}{50\Omega} \right) = j\frac{50V}{50\Omega} (50+j50\Omega)$$

$$V_1 \left(-\frac{1}{2} - j\frac{1}{2} + 1 + 1 + j \right) = j(50+j50) V$$

$$V_1 \left(\frac{3}{2} + j\frac{1}{2} \right) = -50 + j50 V$$

$$V_1 (3+j) = -100 + j100 V$$

$$V_1 = \frac{-100 + j100}{3+j} = \frac{-100 + j100}{10} (3-j) V$$

$$V_1 = (-10 + j10)(3-j) = -30 + 10 + j(30 + 10) V$$

$$V_{Th} = V_1 = -20 + j40 V$$

To find z_{Th} we connect a 1V source at a & b and turn the independent j50V source to 0V.

We must keep the dependent source, however.

3. a) (cont.)

$$z_{Th} = \frac{1V}{I_a} \quad \text{where } I_a \text{ flows into 'a' terminal} \\ \text{with } V_1 = 140^\circ V.$$

$$I_a = \frac{-V_1}{100} + \frac{V_1}{50+j50\Omega} + \frac{V_1}{50\Omega} \quad (\text{remember, } j50V \text{ source is now } 0V, \text{ or wire})$$

$$\text{but } V_1 = 1V \text{ so } z_{Th} = \frac{1V}{\frac{-1V}{100} + \frac{1V}{50+j50\Omega} + \frac{1V}{50\Omega}}$$

$$z_{Th} = \frac{1}{\frac{-1}{100} + \frac{1}{50+j50} + \frac{1}{50}}$$

$$= \frac{50+j50}{\frac{-50-j50}{100} + 1 + \frac{50+j50}{50}}$$

$$= \frac{50+j50}{-\frac{1}{2} - j\frac{1}{2} + 1 + 1 + j} = 50 \frac{1+j}{\frac{3}{2} + j\frac{1}{2}}$$

$$= 100 \frac{1+j}{3+j} \frac{3-j}{3-j} = \frac{100}{10} [3+1 + j(3-1)]$$

$$= 10 (4+j2)$$


$$z_{Th} = 40 + j20 \Omega$$

ave
For max power in z_L we use $z_L = z_{Th}^*$

$$\therefore z_L = 40 - j20 \Omega$$

b) Calculate max ave power absorbed by z_L .

$$\text{sol'n: } P \equiv \text{ave power} = |I_{\text{eff}}|^2 \cdot R_L = \left| \frac{I_{z_L}}{\sqrt{2}} \right|^2 \cdot R_L = \frac{|I_{z_L}|^2}{2} \cdot R_L$$

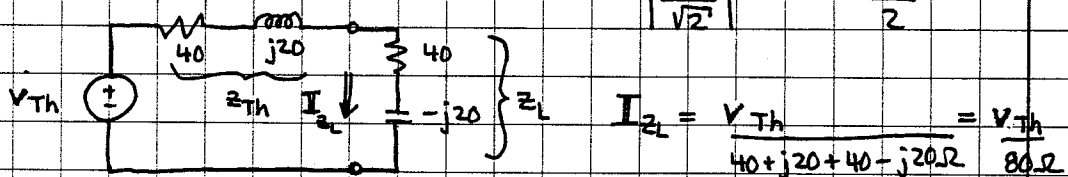

$$\therefore P = \frac{1}{2} \frac{|V_{Th}|^2}{(80\Omega)^2} \cdot 40\Omega = \frac{1}{2} \frac{(-20)^2 + 40^2}{80^2} \cdot 40 W = \frac{1}{2} \cdot \frac{20 \cdot 40}{64 \cdot 16} = 6.25 W$$