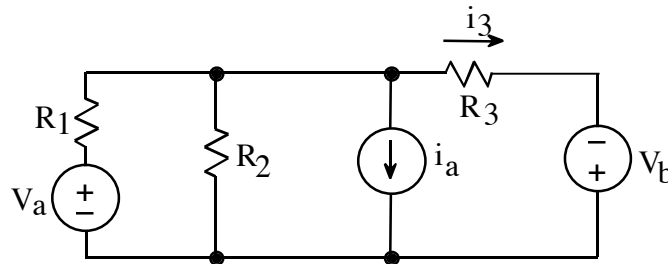



2. (30 points)

Derive an expression for  $i_3$ . The expression must not contain more than the circuit parameters  $V_a$ ,  $V_b$ ,  $i_a$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .



ans: 
$$i_3 = \frac{V_a R_2 + V_b (R_1 + R_2) - i_a R_1 R_2}{R_1 R_2 + R_3 (R_1 + R_2)}$$

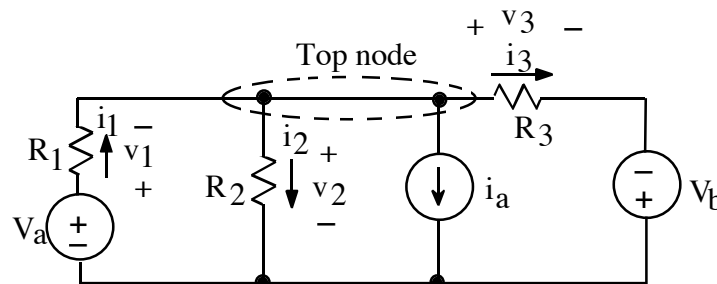sol'n: Using passive sign convention, label voltage drop and current measurement polarities.



Use Kirchhoff's laws:

$$\begin{aligned} \text{sum } v \text{ drops around loop} &= 0 \\ \text{sum } i \text{ out of node} &= 0 \end{aligned}$$

$v$  drops for loop on left, using Ohm's law for  $v_1$  and  $v_2$ :

$$V_a - i_1 R_1 - i_2 R_2 = 0 \text{ V}$$

Middle loop would include current source, so use slightly larger loop with  $R_2$  on left and  $V_b$  on right:

$$i_2 R_2 - i_3 R_3 + V_b = 0 \text{ V}$$

Now sum currents out of top node (that consists of the two top nodes connected by a wire). Note: We are always allowed to combine nodes connected by wires.

$$-i_1 + i_2 + i_a + i_3 = 0 \text{ A}$$

We now have three equations in three unknowns. We solve for  $i_3$ . Use the second equation to eliminate  $i_2$ :

$$i_2 = \frac{i_3 R_3 - V_b}{R_2}$$

Use the first equation to eliminate  $i_1$ :

$$i_1 = \frac{V_a - i_2 R_2}{R_1} = \frac{1}{R_1} \left[ V_a - \left( \frac{i_3 R_3 - V_b}{R_2} \right) R_2 \right] = \frac{1}{R_1} (V_a + V_b - i_3 R_3)$$

Substitute for  $i_1$  and  $i_2$  in the third equation:

$$-\frac{1}{R_1} (V_a + V_b - i_3 R_3) + \frac{i_3 R_3 - V_b}{R_2} + i_a + i_3 = 0 \text{ A}$$

Solve for  $i_3$ :

$$-\frac{1}{R_1} (V_a + V_b) - \frac{V_b}{R_2} + i_a + \frac{1}{R_1} i_3 R_3 + \frac{i_3 R_3}{R_2} + i_3 = 0 \text{ A}$$

$$i_3 \left( \frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right) = \frac{1}{R_1} (V_a + V_b) + \frac{V_b}{R_2} - i_a$$

Multiply both sides by  $R_1 R_2$  to clear fractions:


$$i_3 (R_3 R_2 + R_3 R_1 + R_1 R_2) = R_2 (V_a + V_b) + R_1 V_b - i_a R_1 R_2$$

or


$$i_3 = \frac{V_a R_2 + V_b (R_1 + R_2) - i_a R_1 R_2}{R_1 R_2 + R_3 (R_1 + R_2)}$$

**Now for consistency checks to verify our answer.** (Optional)

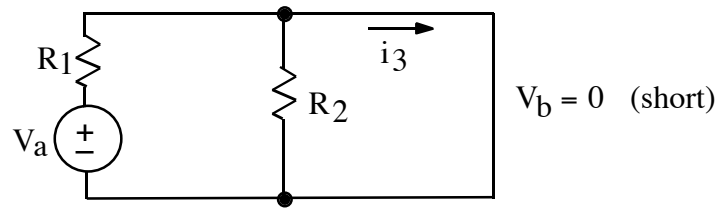- 1) Consider  $i_a = 0$ ,  $V_b = 0$ , and  $R_3 = 0$ :



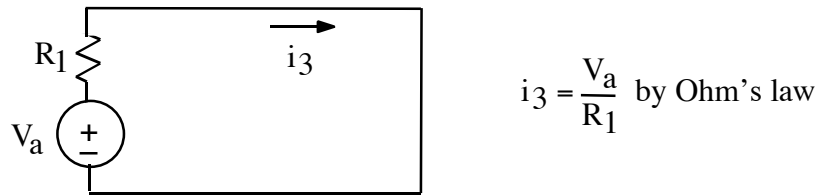Since  $R_2$  is bypassed by a short, no current flows in  $R_2$ . Therefore, we can remove  $R_2$  without changing  $i_3$ :



Our formula gives  $i_3 = \frac{V_a}{R_1}$ . ✓

- 2) Consider  $i_a = 0$  (open circuit) and  $R_2 = \infty$  (open circuit):

Removing  $R_2$  and  $i_a$  leaves total voltage  $V_a + V_b$  across  $R_1 + R_3$  in outside loop.

Therefore, we have

$$i_3 = \frac{(V_a + V_b)}{(R_1 + R_3)}$$


For our formula, we use the following identities:

$$\lim_{R_2 \rightarrow \infty} \frac{R_2}{R_1 R_2 + R_3 (R_1 + R_2)} = \frac{1}{R_1 + R_3} \quad \lim_{R_2 \rightarrow \infty} \frac{R_1 + R_2}{R_1 R_2 + R_3 (R_1 + R_2)} = \frac{1}{R_1 + R_3}$$

Making these substitutions in our formula gives

$$i_3 = \frac{(V_a + V_b)}{(R_1 + R_3)} \quad \checkmark$$


- (3) Consider  $V_a = 0$ ,  $i_a = 0$ :

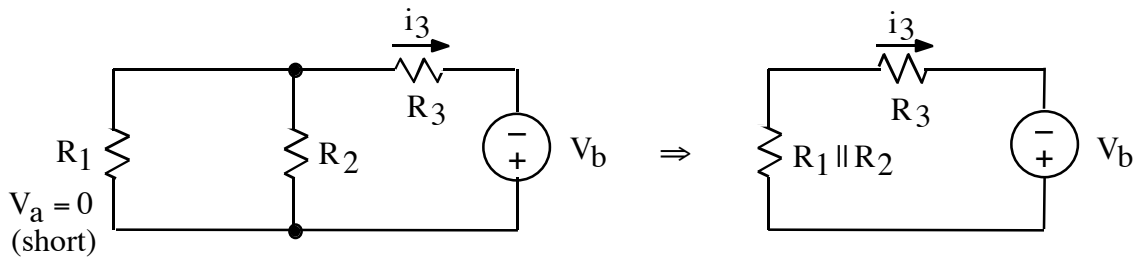

$$i_3 = \frac{V_b}{R_1 \parallel R_2 + R_3}$$

Our formula gives  $i_3 = \frac{V_b(R_1 + R_2)}{R_1 R_2 + R_3(R_1 + R_2)}$  or  $i_3 = \frac{V_b}{R_1 \parallel R_2 + R_3}$ . ✓


(4) Consider  $V_a = 0$ ,  $V_b = 0$ :

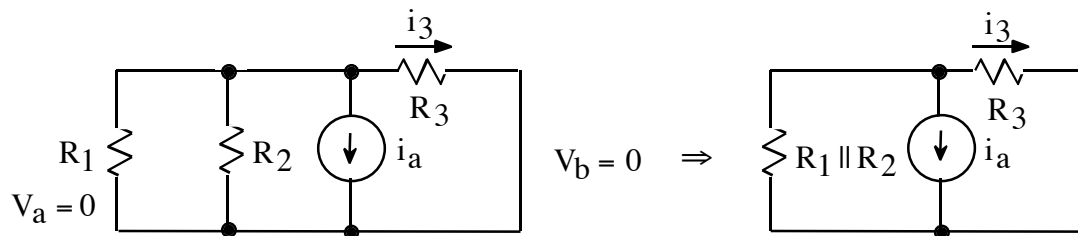

By current divider formula, we have  $i_3 = -\frac{i_a R_1 \parallel R_2}{R_1 \parallel R_2 + R_3}$ .

Our formula gives  $i_3 = -\frac{i_a R_1 R_2}{R_1 R_2 + R_3(R_1 + R_2)}$  or  $i_3 = -\frac{i_a R_1 \parallel R_2}{R_1 \parallel R_2 + R_3}$ . ✓

(5) Consider  $i_a = 0$ ,  $V_b = 0$ .

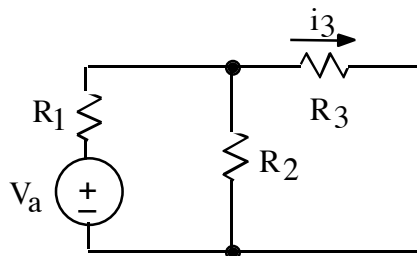

v-divider gives v across  $R_2 \parallel R_3$

$$v_3 = V_a \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1}$$

Now

$$i_3 = \frac{V_3}{R_3} = \frac{V_a R_2 \parallel R_3}{R_3(R_1 + R_2 \parallel R_3)} = \frac{V_a \frac{R_2 R_3}{R_2 + R_3}}{R_3 \left( R_1 \frac{R_2 + R_3}{R_2 + R_3} + \frac{R_2 R_3}{R_2 + R_3} \right)} = \frac{V_a R_2}{R_1(R_2 + R_3) + R_2 R_3}$$

Our formula gives  $i_3 = \frac{V_a R_2}{R_1 R_2 + R_3(R_1 + R_2)}$ . ✓