
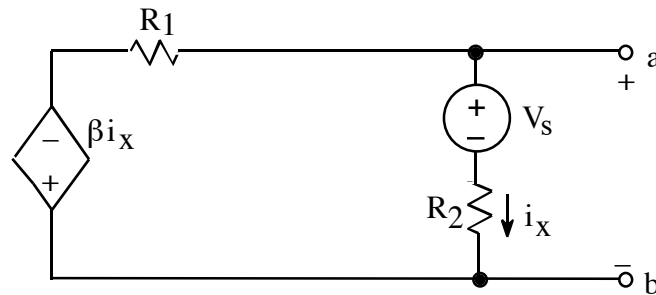


2.

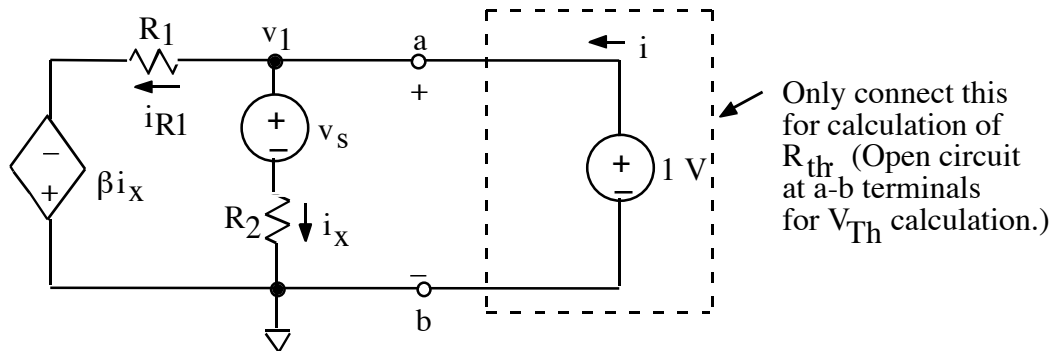

Find the Thevenin's equivalent circuit at terminals a-b. Hint: Use node voltage method to find V_{Th} .

Solution:

First, we find V_{Th} by node-V method (with nothing connected at a-b). We have one node, v_1 , to write an equation for: ($V_{Th} = v_1$ no load)

$$\frac{v_1 + \beta i_x}{R_1} + \frac{v_1 - v_s}{R_2} = 0 \text{ A}$$

We have $i_x = \frac{v_1 - v_s}{R_2}$. Substitute this into our equation

$$\frac{v_1 + \beta \left(\frac{v_1 - v_s}{R_2} \right)}{R_1} + \frac{v_1 - v_s}{R_2} = 0 \text{ A}$$

or

$$v_1 \left(\frac{1}{R_1} + \frac{\beta}{R_1 R_2} + \frac{1}{R_2} \right) = v_s \left(\frac{1}{R_2} + \frac{\beta}{R_1 R_2} \right)$$

Multiply both sides by $R_1 R_2$:

$$v_1 (R_2 + \beta + R_1) = v_s (R_1 + \beta)$$

$$V_{Th} = v_1 = v_s \frac{R_1 + \beta}{R_2 + \beta + R_1}$$

To find R_{Th} , we have two possible approaches:

1. Find current in wire shorting a to b. Then use $R_{Th} = \frac{V_{Th}}{i_{ab}}$.
2. Connect V source to ab with independent source $v_s = 0$.
Then use $R_{Th} = \frac{V}{i}$ where i = current flowing into "a" terminal.

We'll use the second approach. Set $v_s = 0V$. Connect 1 V source to a-b. Then

$$i_x = \frac{1V}{R_2}, \quad i_{R_1} = \frac{1V + \beta i_x}{R_1} = \frac{1V + \beta \cdot \frac{1V}{R_2}}{R_1} = 1V \left(\frac{1}{R_1} + \frac{\beta}{R_1 R_2} \right)$$

$$i = i_x + i_{R_1} = 1V \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{\beta}{R_1 R_2} \right) = 1V \left(\frac{R_1 + R_2 + \beta}{R_1 R_2} \right)$$

$$R_{Th} = \frac{1V}{i} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{\beta}{R_1 R_2}} = R_1 \parallel R_2 \parallel \frac{R_1 R_2}{\beta} = \frac{R_1 R_2}{R_1 + R_2 + \beta}$$