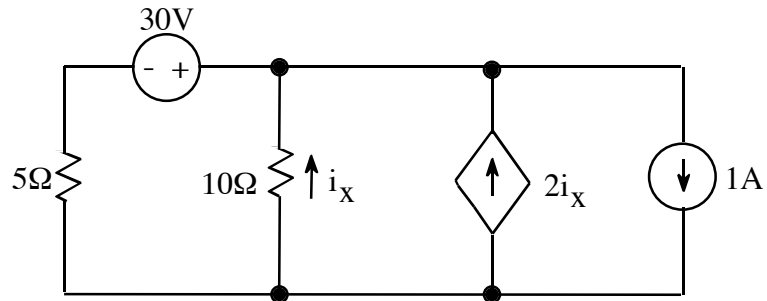


3.



Calculate the power furnished or absorbed by the 30V voltage source, and state whether it is furnished or absorbed.

**Solution:**

Because there are several current sources, the node-V method is a good choice here. For node  $v_1$ :

$$\frac{v_1 - 30 \text{ V}}{5 \Omega} + \frac{v_1}{10 \Omega} - 2i_x + 1 \text{ A} = 0 \text{ A}$$

Our constraint equation:  $i_x = -\frac{v_1}{10 \Omega}$ . Substitute this into the node  $v_1$  equation:

$$\frac{v_1 - 30 \text{ V}}{5 \Omega} + \frac{v_1}{10 \Omega} + \frac{2v_1}{10 \Omega} + 1 \text{ A} = 0 \text{ A}$$

or

$$v_1 \left( \frac{1}{5 \Omega} + \frac{3}{10 \Omega} \right) = \frac{30 \text{ V}}{5 \Omega} - 1 \text{ A} = 5 \text{ A}$$

or

$$v_1 = 5 \text{ A} \cdot 5 \Omega \left\| \frac{10}{3} \Omega = 5 \text{ A} \cdot 5 \Omega \cdot 1 \left\| \frac{2}{3} \right. \right.$$

or

$$v_1 = 25 \text{ V} \cdot \frac{2/3}{5/3} = 10 \text{ V}$$


Current  $i$  flowing from + to - in 30 V source:

$$i = \frac{v_1 - 30 \text{ V}}{5 \Omega} = \frac{10 \text{ V} - 30 \text{ V}}{5 \Omega} = -\frac{20 \text{ V}}{5 \Omega} = -4 \text{ A}$$

$$\text{Power} = i \cdot v = -4 \text{ A} \cdot 30 \text{ V} = -120 \text{ W} < 0 \Rightarrow \text{pwr furnished}$$

Power 120 W furnished (or delivered)

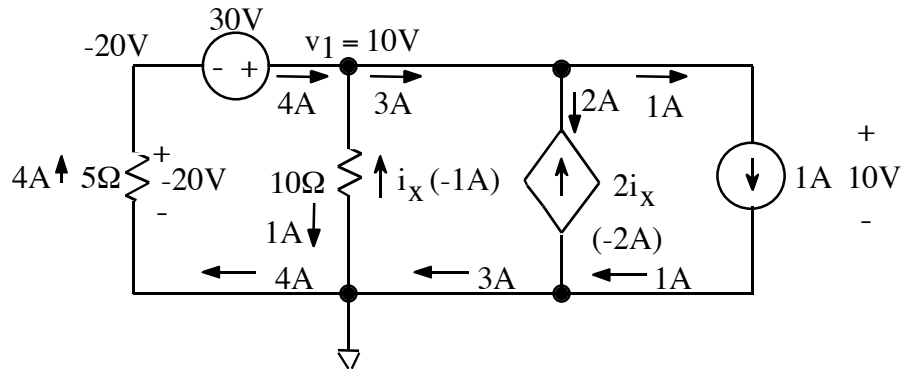**Check:** Calculate all i's and v's and verify Kirchoff's laws.



All sums of currents out of nodes = 0 A ✓

All sums of V-drops around loops = 0 V ✓