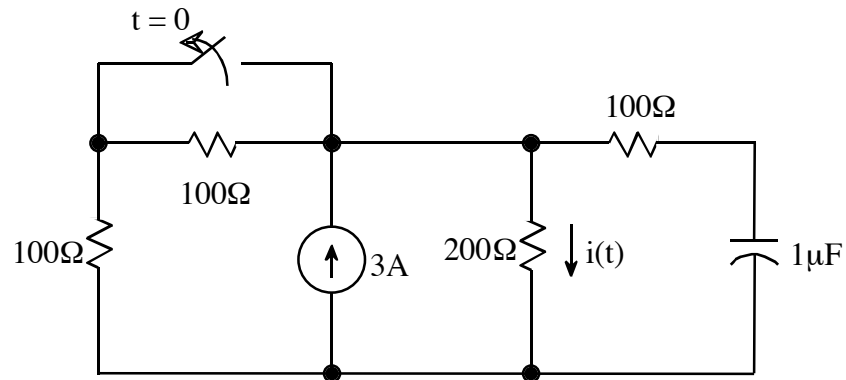



1. (30 points)



After being closed for a long time, the switch is opened at $t = 0$.

- Write a numerical expression for $i(t)$, $t > 0$.
- Calculate the energy stored in the capacitor at $t = 0^+$.
- Calculate the energy stored in the capacitor as $t \rightarrow \infty$.


2. (25 points)

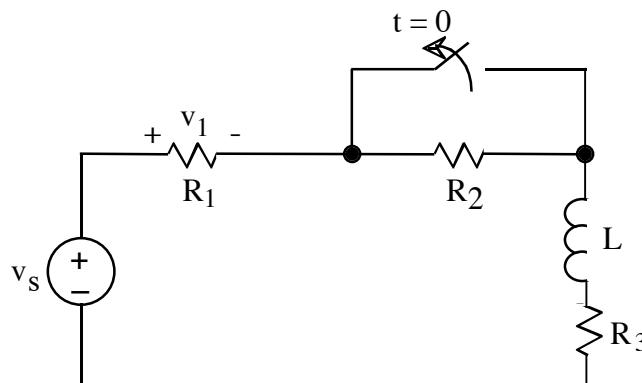

After being closed for a long time, the switch is opened at $t = 0$.


- Write an expression for $v_1(t)$, $t > 0$.
- Make one consistency check (other than units) on your answer.

3. (20 points)

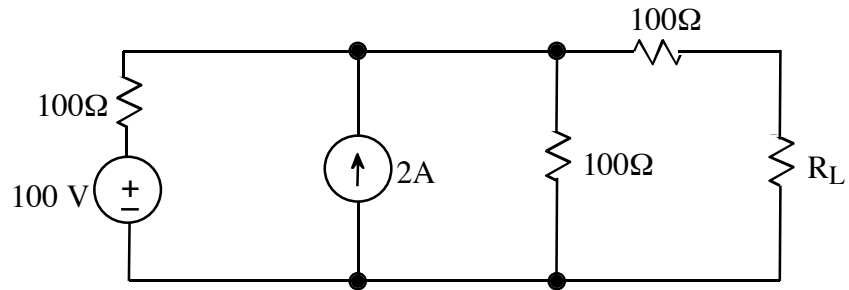

- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

4. (25 points)

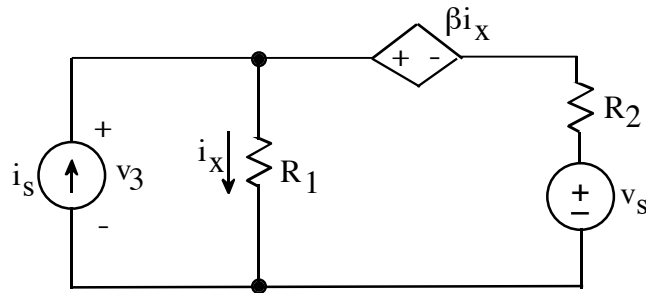

Using superposition, derive an expression for v_3 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and β .