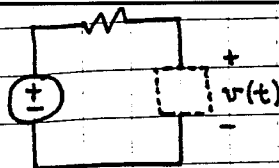


2.

$$v_g(t) = 200 \sin(1000t - 30^\circ) \text{ V}$$




Choose R, L, or C in dashed box to make $v(t) = V_n \sin(1000t) \text{ V}$ where V_n is real constant.
State component value and resulting value of V_n .

sol'n: $V_g = 200 \angle -90^\circ - 30^\circ \text{ V} = 200 \angle -120^\circ \text{ V}$ (phasor)
↑ from sin()

$$V = \mathcal{P}[v(t)] = V_n \angle -90^\circ \text{ V} \quad (\text{phasor})$$

Phasor diagram:

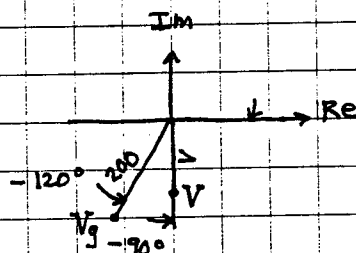

$$V = V_g \cdot \frac{z}{1k+z} \quad \text{where } z \text{ is impedance of dashed box}$$


From phasor diagram, we need a phase shift of $+30^\circ$ to get from -120° for V_g to -90° for V .

$$\therefore \frac{z}{1k+z} \text{ must give } \angle +30^\circ$$

Consider $z = R$ $\frac{z}{1k+z} = \frac{\text{real \#}}{\text{real \#} + \text{real \#}} = \text{real \#} \quad \therefore \angle = 0^\circ$
 So R won't work

Consider $z = \frac{-j}{\omega C}$ $\angle \frac{-j/\omega C}{1k - j/\omega C} = \angle -j/\omega C - \angle(1k - j/\omega C)$

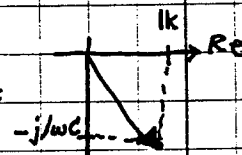but $\angle -j/\omega C = -90^\circ$ since ωC is real
 $\angle 1k - j/\omega C$ will be in range -90° to 0° :



$$\therefore \angle \frac{z}{1k+z} = -90^\circ - \underbrace{(-90^\circ \text{ to } 0^\circ)}_{\text{range of possible } \angle} = \angle \underbrace{-90^\circ \text{ to } 0^\circ}_{\text{range pass}} \neq 30^\circ$$


2. (cont)

 $\therefore C$ won't work

$$\text{Consider } z = j\omega L \quad \angle \frac{j\omega L}{1k + j\omega L} = \angle j\omega L - \angle (1k + j\omega L)$$

$$\angle j\omega L = 90^\circ$$

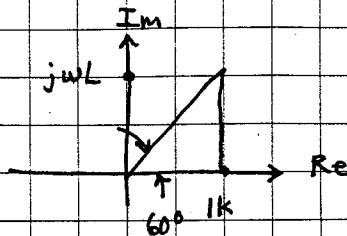\therefore we need $\angle 1k + j\omega L = 60^\circ$ to get
 $\angle j\omega L - \angle 1k + j\omega L = 30^\circ$, as desired.



On phasor diagram, $1k\Omega$ is real part, and $j\omega L$ is imaginary part

$$\angle 1k + j\omega L = \tan^{-1} \frac{\omega L}{1k} = 60^\circ \text{ desired}$$

$$\therefore \frac{\omega L}{1k} = \tan 60^\circ = \sqrt{3}$$

$$\omega L = \sqrt{3} \cdot 1k$$

$$\omega = 1k \quad \text{so} \quad L = \sqrt{3} \text{ H.}$$