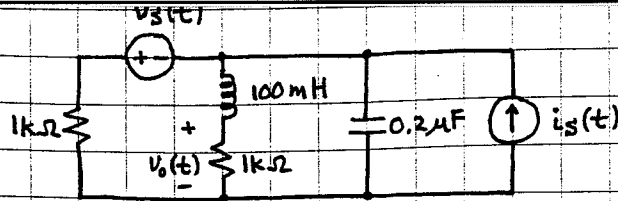


PRACTICE EXAM SOLUTION Probs 3 and 4

3.



$$v_s(t) = 100 \cos(10^4 t) \text{ V}$$


$$i_s(t) = \sin(10^4 t) \text{ A}$$

a) Find a numerical, time-domain expression for $v_o(t)$.


sol'n: I'll use superposition. Other approaches such as node-V or mesh current would work, too.

circuit 1: $V_s = 100 \angle 0^\circ \text{ V}$ set $I_s = 0 \text{ A}$

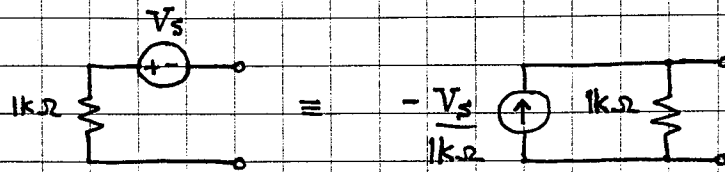Convert V_s and $1k\Omega$ on left to Norton equivalent:




Our circuit 1 is now:

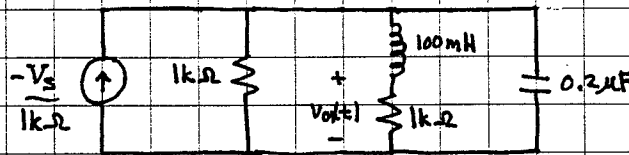

circuit 2: $V_s = 0 \text{ V}$ and $I_s = 1 \angle -90^\circ \text{ A}$ (phasor for i_s)

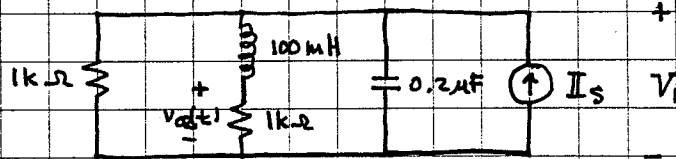Keeping the Norton equivalent, our circuit 2 is:



Clearly, we can sum the current sources from circuits 1 & 2 to find V_o drop from top rail to bottom rail.

$$3.a(\text{cont}) \quad V_1 = \left(-\frac{V_s}{1k\Omega} + I_s \right) 1k\Omega \parallel (j\omega L + 1k\Omega) \parallel \frac{-j}{\omega C}$$

$$j\omega L = j 10^4 100m = j 1k\Omega$$

$$\frac{-j}{\omega C} = \frac{-j}{10^4 0.2\mu} = \frac{-j}{2m} = \frac{-j \cdot 1k\Omega}{2}$$

$$-\frac{V_s}{1k\Omega} + I_s = \frac{-100 \angle 0^\circ V}{1k\Omega} + 1 \angle -90^\circ A$$

$$= -0.1 \angle 0^\circ A + 1 \angle -90^\circ A$$

$$= -0.1 - j$$

$$= \sqrt{0.1^2 + 1^2} \angle \tan^{-1} \frac{-1}{-0.1}$$

$$= 1.005 \angle -95.7^\circ$$

$$1k\Omega \parallel (j1k\Omega + 1k\Omega) \parallel \frac{-j}{2} 1k\Omega = 1k\Omega \cdot \frac{1}{\frac{1}{1} + \frac{1}{1+j} - \frac{2}{j}}$$

$$= \frac{1k}{1 + \frac{1-j}{2} + 2j} = \frac{1k}{\frac{3}{2} + j\frac{3}{2}} = \frac{2}{3} \cdot \frac{1k}{1+j}$$

$$= \frac{2k}{3} \frac{1-j}{2} = 1k \cdot \frac{(1-j)}{3}$$

$$V_1 = 1.005k \angle -95.7^\circ \cdot \frac{1-j}{3} V$$

V_o from v-divider:

$$V_o = V_1 \cdot \frac{1k\Omega}{1k\Omega + j\omega L} = V_1 \cdot \frac{1k\Omega}{1k\Omega + j1k\Omega} = V_1 \frac{1}{1+j} = V_1 \frac{(1-j)}{2}$$

$$V_o = 1.005k \angle -95.7^\circ \left(\frac{1-j}{3} \cdot \frac{1-j}{2} = \frac{-j2}{6} \right) = \frac{1.005k \angle -105.7^\circ}{3}$$


3a(cont) $V_o = 0.335 \angle -185.7^\circ \text{ V}$

$$v_o(t) = 0.335 \text{ kcos}(10^4 t - 185.7^\circ) = 0.335 \text{ kcos}(10^4 t + 174.3^\circ) \text{ V}$$


or $v_o(t) = -0.335 \text{ kcos}(10^4 t - 5.7^\circ) \text{ V}$

b) Show V_o on a phasor diagram.

sol'n:

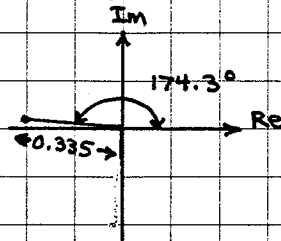

4.

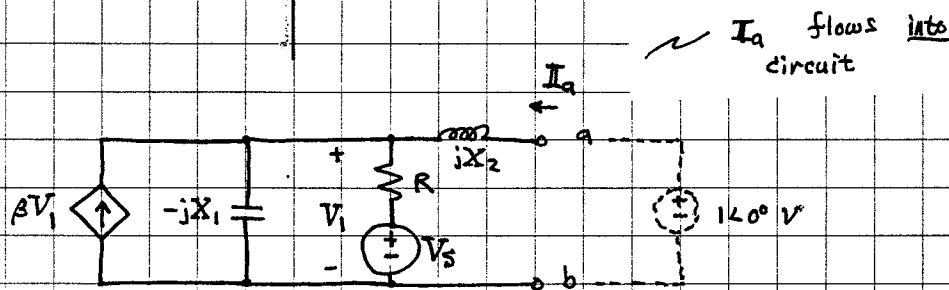

Construct a frequency domain Thevenin equivalent.

sol'n: $V_{Th} = \text{open circuit output } V \text{ (phasor)} = V_1$ (since no drop across jX_2)

Use Node-V: $\frac{V_1 - V_s}{R} + \frac{V_1}{-jX_1} - \beta V_1 = 0 \text{ A}$

$$V_1 \left(\frac{1}{R} - \frac{1}{jX_1} - \beta \right) = \frac{V_s}{R}$$

$$V_{Th} = V_1 = V_s \frac{(R \parallel -jX_1 \parallel -\beta)}{R} \text{ or } V_s \left(1 \parallel \frac{jX_1}{R} \parallel \frac{1}{R\beta} \right)$$

$$Z_{Th} = \frac{140^\circ \text{ V}}{I_a} \text{ with } V_s \text{ set to } 0 \text{ V}$$

Use Node-V: $\frac{V_1 - 140^\circ \text{ V}}{jX_2} + \frac{V_1}{R} + \frac{V_1}{-jX_1} - \beta V_1 = 0 \text{ A}$

$$V_1 \left(\frac{1}{jX_2} + \frac{1}{R} - \frac{1}{jX_1} - \beta \right) = \frac{140^\circ \text{ V}}{jX_2}, \quad -I_a = \frac{V_1 - 140^\circ \text{ V}}{jX_2}$$

$$Z_{Th} = \frac{-jX_2 \cdot 140^\circ \text{ V}}{V_1 - 140^\circ \text{ V}} = -jX_2 \left/ \left(1 \parallel \frac{R}{jX_2} \parallel \frac{-X_1}{X_2} \parallel \frac{-1}{jX_2\beta} - 1 \right) \right.$$