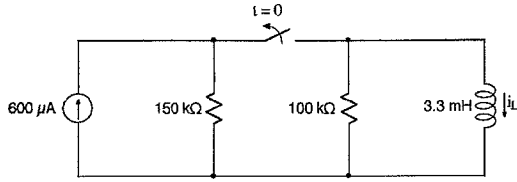



Problem Set #6

1.




After being closed for a long time, the switch opens at $t = 0$. Find $i_L(t)$ for $t > 0$.

2.

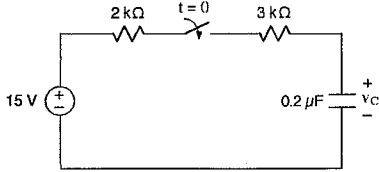


After being open for a long time, the switch closes at $t = 0$. $v_C(t = 0^-) = 0V$. Find $v_C(t)$ for $t > 0$.

3.

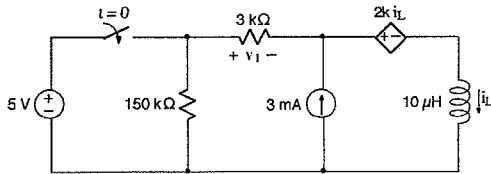


After being open for a long time, the switch closes at $t = 0$. Find $v_1(t)$ for $t > 0$.

4.

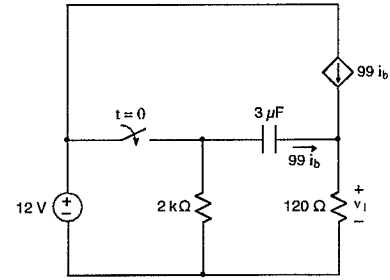

After being open for a long time, the switch closes at $t = 0$. Find $v_1(t)$ for $t > 0$.

EX:

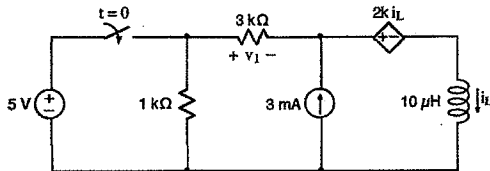

After being open for a long time, the switch closes at $t = 0$. Find $v_1(t)$ for $t > 0$.

Soln: To find $v_1(t > 0)$, we use the general form of solution, (which applies to any current or voltage):

$$v_1(t > 0) = v_1(t \rightarrow \infty) + [v_1(0^+) - v_1(t \rightarrow \infty)] e^{-t/\tau_{\text{em}}}$$


We have an inductor whose behavior at time $t = 0^+$ will affect the value of $v_1(0^+)$.

We find the value of i_L at time $t = 0^-$ and employ the concept that i_L , being an energy variable, cannot change instantly. Thus, $i_L(0^+) = i_L(0^-)$.

At $t = 0^+$, currents and voltages have stabilized, and time derivatives = 0. Thus, $v_L = L di/dt = 0V$ and the L acts like a wire: it has no v drop but it can carry current.


At $t = 0^-$, the switch is open, removing the 5V source from the circuit.

$t = 0^-$:

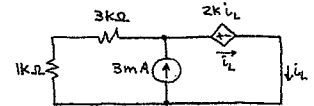

We observe that the dependent source is equivalent to a resistor.
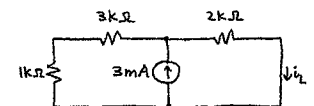
$$R_{\text{eq}} = \frac{V}{i} = \frac{2k i_L}{i_L} = 2k\Omega$$



This is a current divider.


$$i_L(0^-) = 3mA \frac{1k\Omega + 3k\Omega}{1k\Omega + 3k\Omega + 2k\Omega} = 2mA$$

Note that we do not find $v_1(0^-)$ since it may change instantly when the switch closes.

$t = 0^+$: We model the L as a current source with $i_L(0^+) = i_L(0^-)$.

The switch is closed for $t > 0$.

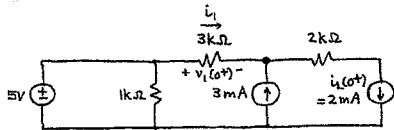As before the dependent source acts like a $2k\Omega$ resistor.



A current summation at the node shown as a large dot gives the current thru the $3k\Omega$ resistor:

$$-i_1 - 3\text{mA} + 2\text{mA} = 0\text{A}$$

or


$$i_1 = -1\text{mA}$$

By Ohm's Law, we have


$$v_1(0^+) = i_1 \cdot 3k\Omega = -1\text{mA} \cdot 3k\Omega = -3\text{V}$$

Now we find $v_1(t \rightarrow \infty)$.

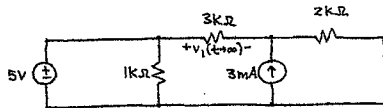$t \rightarrow \infty$: The L again acts like a wire, and the switch is closed.



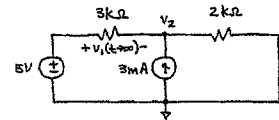We may ignore the $1k\Omega$ resistor since it acts like a separate circuit across the 5V source. (The other circuit across the 5V source consists of $3k\Omega$, $2k\Omega$, and L.)



Using the node-voltage method, we have

$$\frac{v_2 - 5\text{V}}{3k\Omega} - 3\text{mA} + \frac{v_2}{2k\Omega} = 0\text{A}$$

Multiplying both sides by $6k\Omega$ yields

$$v_2(2 + 3) = 2 \cdot 5\text{V} + 6k\Omega \cdot 3\text{mA}$$

or


$$5v_2 = 28\text{V}$$

or

$$v_2 = \frac{28\text{V}}{5}$$


$$\text{Thus, } v_1(t \rightarrow \infty) = 5\text{V} - v_2 = 5\text{V} - \frac{28\text{V}}{5} = -\frac{3}{5}\text{V}$$

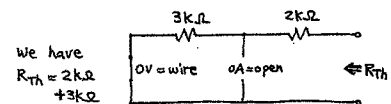R_{Th} : We can use the circuit at the top of the page with the independent sources set to zero and the L (i.e., wire) removed.



$$\therefore v_1(t > 0) = -\frac{3\text{V}}{5} + \left[-3\text{V} - \left(-\frac{3\text{V}}{5}\right) \right] e^{-\frac{t}{10\mu\text{s}/5\text{H}}} = -0.6 - 2.4e^{-t/50\mu\text{s}}\text{V}$$

Ex:

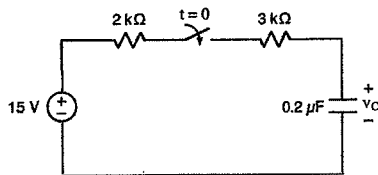

After being open for a long time, the switch closes at $t=0$. $v_c(t=0^-) = 0\text{V}$. Find $v_c(t)$ for $t > 0$.

sol'n: Use the general form of solution for RC problems.

$$v_c(t > 0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/R_{\text{Th}}\tau}$$

We now proceed to find the following values:


$$v_c(0^+), v_c(t \rightarrow \infty), \text{ and } R_{\text{Th}}$$

To find $v_c(0^+)$, we consider $t=0^-$ and find $v_c(0^-)$. Since v_c is an energy variable that cannot change instantly, we have $v_c(0^+) = v_c(0^-)$.

At $t=0^-$, currents and voltages have stabilized, and all time derivatives of currents and voltages are zero.

Thus, $i_c = C \frac{dv_c}{dt} = C \cdot 0 = 0$. C looks like open.

$t=0^-$: C = open, switch open

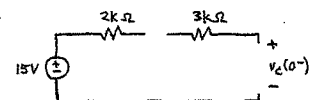


From the circuit diagram, we cannot determine $v_c(0^-)$. The C could be charged to some voltage, and it would remain at that voltage forever.

Fortunately, the problem states that $v_c(0^-) = 0\text{V}$.

$t=0^+$: v_c cannot change instantly, so


$$v_c(0^+) = v_c(0^-) = 0\text{V}$$

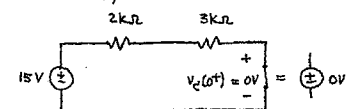If needed a circuit model at $t=0^+$, we would model the C as a v src with value 0V . In other words, C = wire at $t=0^+$.



To find $v_c(t \rightarrow \infty)$, we again use the idea that currents and voltages are stable and C = open.

EX:

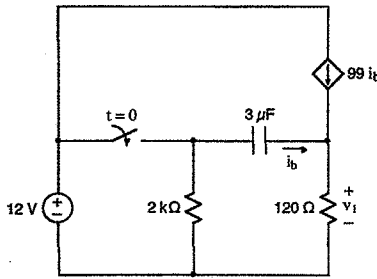


After being open for a long time, the switch closes at $t=0$. Find $v_1(t)$ for $t>0$.

soln: Use general form of solution for RC problems:


$$v_1(t>0) = v_1(t \rightarrow \infty) + [v_1(0^+) - v_1(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

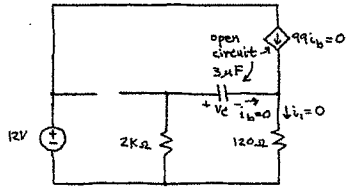$t=0^-$: C acts like open circuit $\Rightarrow i_b=0, 99i_b=0$
switch is open



Since no power is connected to C, $v_c(0^-)=0V$

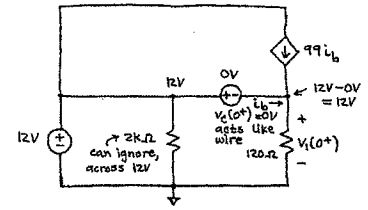
$t=0^+$: C acts like v src, $v_c(0^+) = v_c(0^-)$.
switch is closed




If we consider a v-loop around the outside of the bottom half of the circuit, we find that we have 12V across the 120Ω resistor:

$$v_1(0^+) = 12V$$

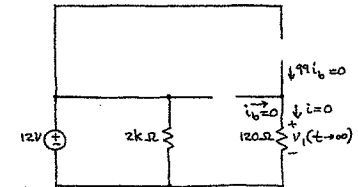$t \rightarrow \infty$: C acts like open circuit $\Rightarrow i_b=0, 99i_b=0$
switch is closed



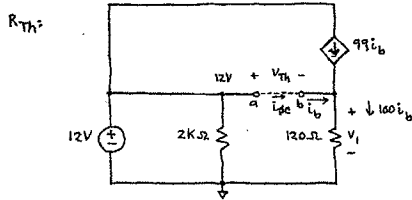No power is connected to 120Ω.
Thus, $v_1(t \rightarrow \infty) = 0V$



$$R_{Th} = \frac{V_{Th}}{i_{sc}} \quad V_{Th} = v_{a,b} \text{ with C removed (a,b open circuit)}$$

With open circuit a,b we have $i_b=0$
and $99i_b=0$. Thus, $v_1=0V$.

$$V_{Th} = 12V - v_1 = 12V - 0V = 12V$$

Now connect wire from a to b and measure current, i_{sc} .

We have $v_1=12V$ since it is now connected across 12V source by wires.

The current thru the 120Ω resistor is $100i_b$:


$$\frac{v_1}{120\Omega} = \frac{12V}{120\Omega} = 100mA = 100i_b$$

$$\text{Thus, } i_{sc} = i_b = \frac{100mA}{100} = 1mA$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{12V}{1mA} = 12k\Omega$$

Note: We get the same result if we remove the dependent source and multiply the 120Ω resistor by 100 to account for the $100i_b$ flowing thru it.

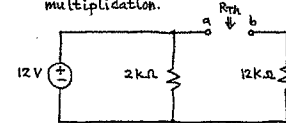This is the concept of impedance multiplication.



We find R_{Th} by turning off the 12V source (which becomes a wire) and determining R seen looking into a,b.

We have $R_{Th} = 12k\Omega$, as before.

Plugging values into the general solution yields our final answer:

$$v_1(t) = 0V + [12V - 0V] e^{-t/12k\Omega \cdot 3\mu F}, \quad t>0$$

or

$$v_1(t>0) = 12V e^{-t/36ms}$$