


Problem Set #7

ECE 1600

Exam #3 Sol'n

Sp '04


1. (30 points)

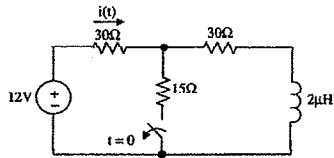

After being closed for a long time, the switch is opened at $t=0$.

- Calculate the energy stored on the inductor at $t \rightarrow \infty$.
- Write a numerical expression for $i(t)$, $t > 0$.

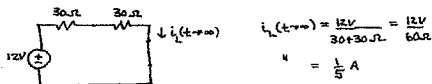sol'n: a) $t \rightarrow \infty$: model L as wire, switch open




$$i_L(t \rightarrow \infty) = \frac{12V}{30\Omega + 30\Omega} = \frac{12V}{60\Omega} = \frac{1}{5} A$$

$$\text{Energy } w_L(t \rightarrow \infty) = \frac{1}{2} L i_L^2(t \rightarrow \infty) = \frac{1}{2} (2\mu H) \left(\frac{1}{5} A\right)^2$$

$$w_L(t \rightarrow \infty) = \frac{1}{25} \mu J \text{ or } 40 nJ$$

Note: $i(t \rightarrow \infty) = i_L(t \rightarrow \infty) = \frac{1}{5} A = 200 \text{ mA}$

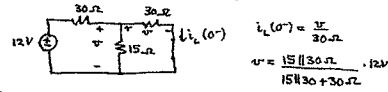b) $t=0^-$: switch closed, $L = \text{wire}$, find $i_L(0^-)$



$$i_L(0^-) = \frac{12V}{30\Omega}$$


$$v = \frac{15 \parallel 30 \Omega}{15 \parallel 30 + 30 \Omega} \cdot 12V$$

$t=0^+$: switch open, $L = \text{current src}$

$$15 \parallel 30 \Omega = 10 \Omega \quad \parallel 2 = 15 \Omega \cdot \frac{2}{3} = 10 \Omega$$

$$v = \frac{10}{10+30} \cdot 12V = 3V$$

Find $i(0^+)$

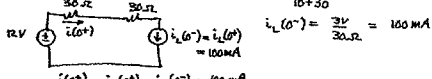


$$i_L(0^+) = \frac{3V}{30\Omega} = 100 \text{ mA}$$

$$i(0^+) = i_L(0^+) = i_L(0^-) = 100 \text{ mA}$$

$$0 < t < \infty: R_{\text{th}} \text{ of circuit} = 30\Omega + 30\Omega = 60\Omega \quad \tau = \frac{L}{R_{\text{th}}} = \frac{2\mu H}{60\Omega} = \frac{1}{30}$$

$$i(t > 0) = i(t \rightarrow \infty) + [i(0) - i(t \rightarrow \infty)] e^{-t/\tau} = 200 - 100 e^{-t/30} \text{ mA}$$

2. (25 points)

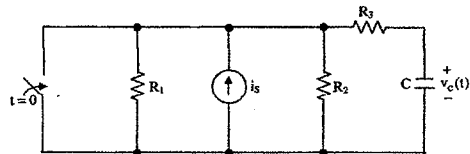


After being open for a long time, the switch is closed at $t=0$.

- Write an expression for $v_C(t=0^+)$.
- Write an expression for $v_C(t)$, $t > 0$.

sol'n: a) $t=0^-$: switch open, $C = \text{open}$, find $v_C(0^-)$ since $v_C(0^+) = v_C(0^-)$




Use Thevenin equiv of i_s, R_1 , and R_2

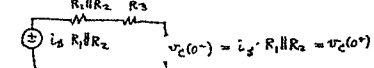

$$v_C(0^+) = i_s \cdot R_1 \parallel R_2 \text{ or } i_s \cdot \frac{R_1 R_2}{R_1 + R_2}$$

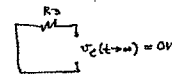b) $v_C(0^+) = i_s \cdot R_1 \parallel R_2$ so move on to $t \rightarrow \infty$ and R_{th}

$t \rightarrow \infty$: switch closed (so we can ignore R_1, i_s , and R_2), $C = \text{open}$, find $v_C(t \rightarrow \infty)$




$0 < t < \infty$: from circuit for $t \rightarrow \infty$ we see that R_{th} of circuit where C is connected is just R_3

$$\tau = R_{\text{th}} C = R_3 C$$

$$v_C(t > 0) = v_C(t \rightarrow \infty) + [v_C(0^+) - v_C(t \rightarrow \infty)] e^{-t/\tau}$$

$$v_C(t > 0) = i_s \cdot R_1 \parallel R_2 e^{-t/R_3 C}$$


3. (20 points)

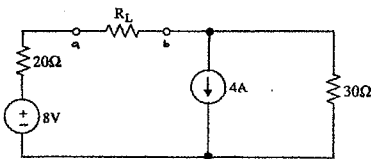

- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

sol'n: a) $R_L = R_{\text{Th}}$ of circuit where R_L connected gives max pow xfer

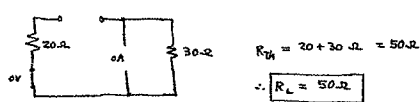$R_{\text{Th}} = R$ looking into circuit at terminals a,b without R_L and srcs = 0 (i.e. $8V = 0V = \text{wire}$, $4A = 0A = \text{open}$)




$$R_{\text{th}} = 20 + 30 \Omega = 50 \Omega$$

$$\therefore R_L = 50 \Omega$$

$$\text{b) } \max p = \frac{v_{\text{Th}}^2}{4 R_{\text{Th}}}$$

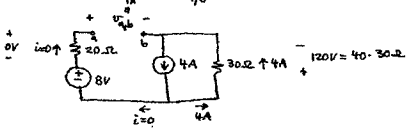Find $v_{\text{Th}} = v_{a,b}$ without R_L




$$\text{From outer } v\text{-loop, we have } v_{\text{Th}} = -8V - (20V) = -128V$$

$$\max p = \frac{(-128V)^2}{4 \cdot 50 \Omega} = \frac{32 \cdot 128}{50} W = \frac{82 \cdot 128}{1k} W = \frac{81.92 \cdot 1k}{1k} W$$


$$\boxed{\max p = 81.92 \text{ W}}$$

4. (25 points)

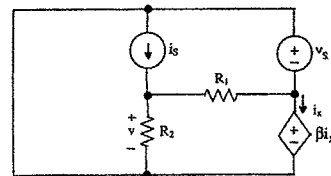

Using superposition, derive an expression for v that contains no circuit quantities other than i_s, v_s, R_1, R_2 , and β , where $\beta > 0$.


sol'n: case I: i_s on, v_s off

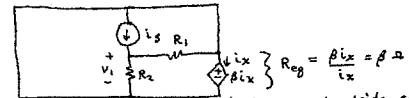

i -divider with R_1 and R_2 in parallel. $R_{\text{eq}} = \frac{\beta i_x}{i_x} = \beta \Omega$

$$v_1 = i_s \cdot R_1 \parallel R_2$$

case II: i_s off, v_s on

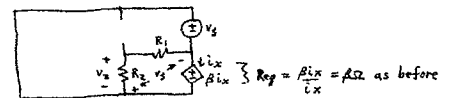

v -divider with v_s across R_1 and R_2 in series

$$v_2 = -v_s \frac{R_2}{R_1 + R_2}$$

$$\boxed{v = v_1 + v_2 = i_s \cdot R_1 \parallel R_2 - v_s \frac{R_2}{R_1 + R_2}}$$