
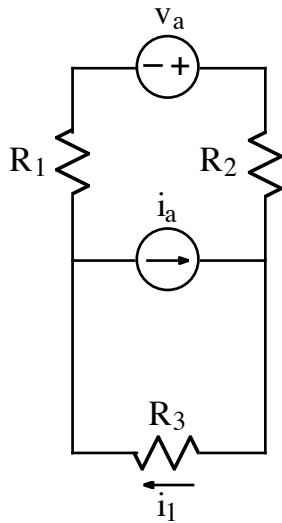


Ex:

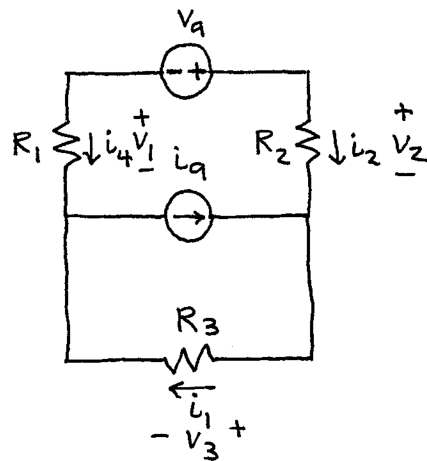

Derive an expression for i_1 . The expression must not contain more than the circuit parameters v_a , i_a , R_1 , R_2 , and R_3 .

sol'n: We label i 's and v 's for R 's.



We have a v -loop around the outside.
(Other loops would include i -src, i_a .)

$$+v_1 + v_a - v_2 - v_3 = 0V$$

We could write an i -sum eq'n for either the node on the left or right. We only need one node. The other node is redundant.

If we use the node on the left, our eq'n is

$$-i_4 + i_q - i_1 = 0A$$

We look for components in series carrying the same current. R_1 and R_2 are in series.

$$i_4 = -i_2$$

From Ohm's law, we have

$$v_1 = i_4 R_1 = -i_2 R_1$$

$$v_2 = i_2 R_2$$

$$v_3 = i_1 R_3$$

Substituting Ohm's law and $i_4 = -i_2$ into our v -loop and i -sum eq'ns gives

$$-i_2 R_1 + v_q - i_2 R_2 - i_1 R_3 = 0V$$

$$i_2 + i_q - i_1 = 0A$$

Solving the second eq'n for i_2 gives

$$i_2 = i_1 - i_q$$

Substituting for i_2 in the first eq'n gives

$$-(i_1 - i_a)(R_1 + R_2) + V_a - i_1 R_3 = 0V$$

$$\text{or } -i_1(R_1 + R_2 + R_3) = -i_a(R_1 + R_2) - V_a$$

$$\text{or } i_1 = \frac{i_a(R_1 + R_2) + V_a}{R_1 + R_2 + R_3}$$

Consistency checks:

$$\text{Set } i_a = 0A. \quad i_1 = \frac{V_a}{R_1 + R_2 + R_3}$$

$$\text{Eq'n gives } i_1 = \frac{0 \cancel{(R_1 + R_2)} + V_a}{R_1 + R_2 + R_3} \quad \checkmark$$

$$\text{Set } V_a = 0V. \quad i_1 = \frac{i_a(R_1 + R_2)}{R_1 + R_2 + R_3}$$

(current divider)

$$\text{Eq'n gives } i_1 = \frac{i_a(R_1 + R_2) + 0V}{R_1 + R_2 + R_3} \quad \checkmark$$