
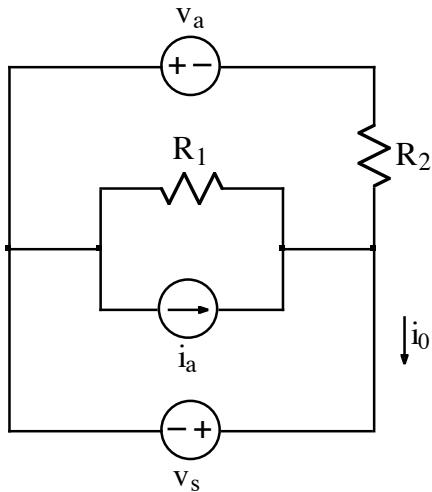


Ex:

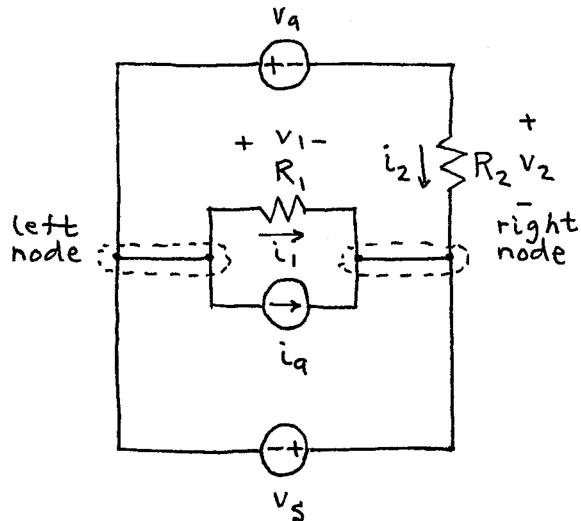

Derive an expression for i_0 . The expression must not contain more than the circuit parameters v_a , v_s , i_a , R_1 , and R_2 .

sol'n: Label R's first.



V-loops: (v_a and R_1, R_2 ; v_s and R_1)

$$-v_a - v_2 + v_1 = 0V$$

$$-v_1 - v_s = 0V$$

We observe that we can solve these 2 eqns in 2 unknowns without proceeding further.

$$v_1 = -v_s \quad \text{from 2nd eqn}$$

$$v_2 = -v_a + v_1 = -v_a - v_s \quad \text{from 1st eq'n}$$

Note: If we try to write current-sum eqns, we find that the left node and right node are connected by only v-src v_s . Thus, we should not write i-sum eqns. (And we don't need them!)

Note: We also have no components in series that carry the same current, (except v-src v_a and R_2).

We now use Ohm's law:

$$v_1 = i_1 R_1$$

$$v_2 = i_2 R_2$$

Using v-eqns:

$$i_1 = \frac{v_1}{R_1} = \frac{-v_s}{R_1}$$

$$i_2 = \frac{v_2}{R_2} = \frac{-v_a - v_s}{R_2}$$

Now that we have solved the circuit,
we can find i_o from an i-sum eq'n
for the node on the right.

$$-i_2 - i_1 - i_q + i_o = 0A$$

$$\text{or } i_o = i_1 + i_2 + i_q$$

$$\text{or } i_o = -\frac{v_s}{R_1} - \frac{v_q + v_s}{R_2} + i_q$$