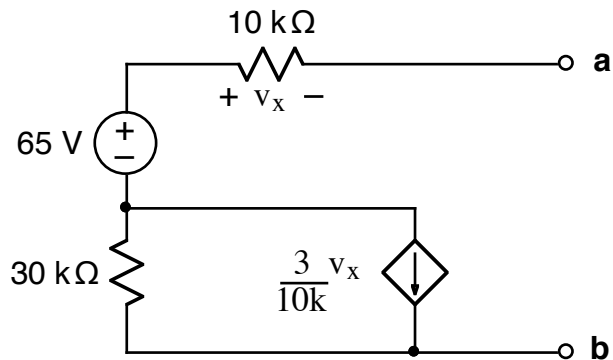


Ex:



- Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.
- If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .

Sol'n: a) $V_{Th} = V_{a,b \text{ open circuit}}$

With nothing across **a** and **b**, no current flows in the $10k\Omega$ resistor, and $v_x = 0V$.


With $v_x = 0$, the dependent source has zero current and disappears.

We are left with the $65V$ source and the two resistors in series. Since no current flows in the circuit, the voltage drop across the $30k\Omega$ resistor is zero volts.

$$\therefore V_{Th} = 65V$$

To find R_{Th} , we use $R_{Th} = \frac{V_{Th}}{i_{sc}}$

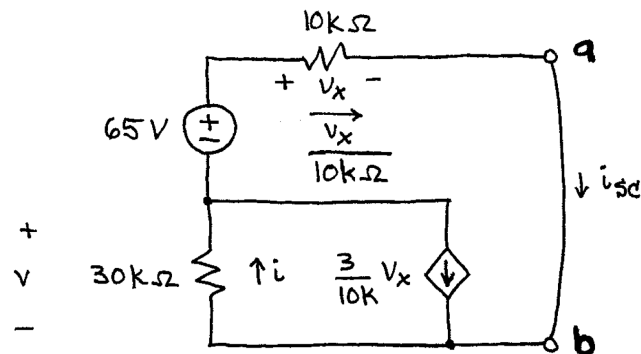where i_{sc} = current thru short from **a** to **b**.



If we sum currents at the node on the left side, we have

$$i = \frac{V_x}{10k\Omega} + \frac{3}{10k\Omega} V_x = \frac{4}{10k\Omega} V_x$$

This allows us to write the voltage, v , across the $30k\Omega$ and the dependent source in terms of V_x :

$$v = -i \cdot 30k\Omega = -\frac{4}{10k\Omega} V_x \cdot 30k\Omega$$

Now we can replace the dependent source with an equivalent R :


$$R_{eq} = \frac{v}{\frac{3}{10k} V_x} = \frac{-\frac{4}{10k\Omega} V_x \cdot 30k\Omega}{\frac{3}{10k} V_x} = -40k\Omega$$

This R_{eq} in parallel with the $30k\Omega$ gives

$$30k\Omega \parallel R_{eq} = 30k\Omega \parallel -40k\Omega = 10k\Omega \cdot 3 \parallel -4$$

$$30 \text{ k}\Omega \parallel R_{eq} = 10 \text{ k}\Omega \cdot \frac{-12}{-1} = 120 \text{ k}\Omega$$

New circuit model:

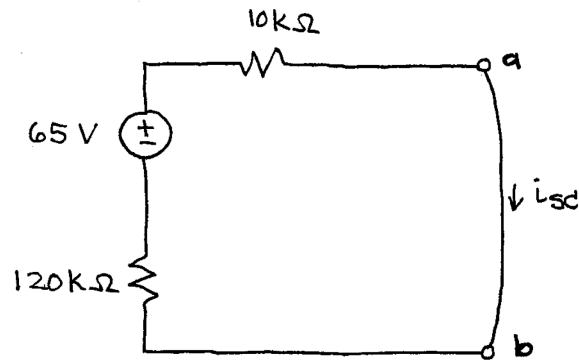


$$i_{sc} = \frac{65 \text{ V}}{10 \text{ k}\Omega + 120 \text{ k}\Omega} = \frac{65 \text{ V}}{130 \text{ k}\Omega} = \frac{1}{2} \text{ mA}$$

$$\therefore R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{65 \text{ V}}{\frac{1}{2} \text{ mA}} = 130 \text{ k}\Omega$$

Note: The method we used to find R_{eq} actually works all the time, and we have the above circuit, (without the short across **a** and **b**), as the equivalent of the original circuit.

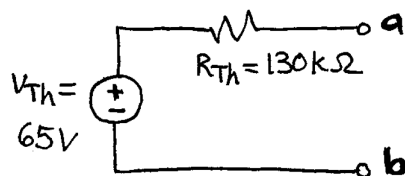With the equivalent circuit, we see that $V_{Th} = 65 \text{ V}$ and $R_{Th} = 10 \text{ k}\Omega + 120 \text{ k}\Omega$.



$$b) \quad R_L = R_{Th} = 130 \text{ k}\Omega \text{ for max pwr xfer}$$

$$c) \quad P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(65V)^2}{4 \cdot 130 \text{ k}\Omega} = \frac{65}{4 \cdot 2} \text{ mW}$$

$$P_{max} = \frac{65}{8} \text{ mW} = 8.125 \text{ mW}$$