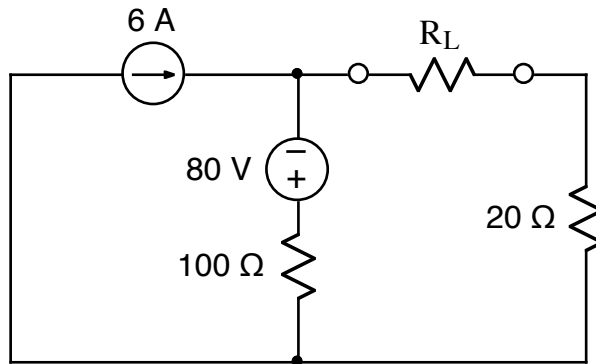



Ex:



- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

Sol'n: a) $R_L = R_{Th}$ for max pwr

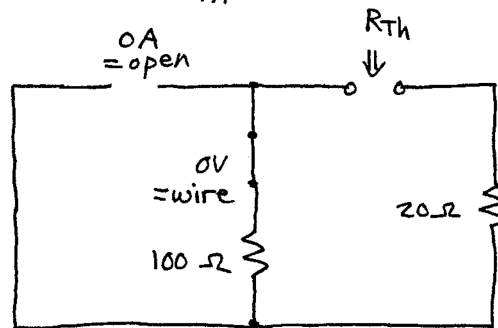Turn off sources, remove R_L , and look into circuit from R_L terminals to find R_{Th} .



$$R_{Th} = 100 \Omega + 20 \Omega = 120 \Omega$$


$$\therefore R_L = 120 \Omega$$

b) $\text{max pwr} = \frac{\left(\frac{V_{Th}}{2}\right)^2}{R_{Th}}$ from Thev equiv with $R_L = R_{Th}$. (R_L sees $V = \frac{V_{Th}}{2}$.)

$V_{Th} = V$ across R_L terminal with R_L removed.

Use superposition to find v_{Th} .


case I: 6A on, 80V off

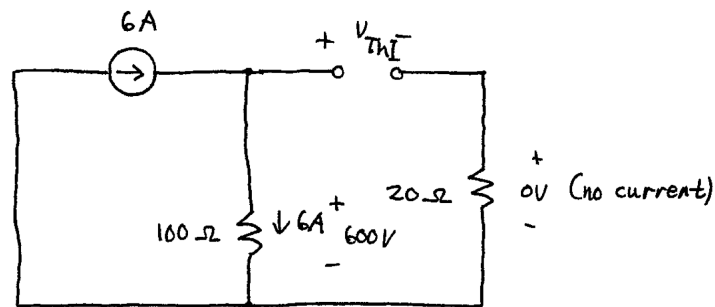

$$V_{Th1} = V \text{ across } 100\Omega \text{ resistor} = 6A \cdot 100\Omega$$

$$\therefore V_{Th1} = 600V$$

case II: 6A off, 80V on

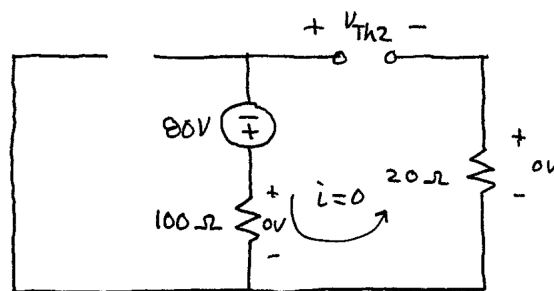

We have no current no V drop across R 's.
The 80V appears as $-V_{Th2}$ across the terminals. $V_{Th2} = -80V$.

$$V_{Th} = V_{Th1} + V_{Th2} = 600 - 80V = 520V$$

$$P_{max} = \left(\frac{520}{2}\right)^2 / R_{Th} = \left(\frac{520}{2}\right)^2 / 120\Omega = \frac{1690}{3}W = 563.3W$$