
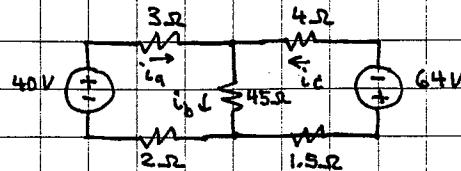


ex:

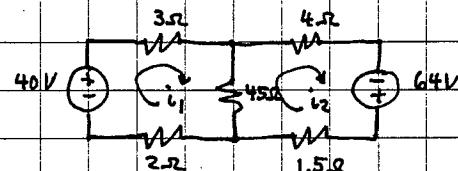a) Use mesh-current method to find branch currents i_1, i_2, i_3 .

We define the mesh currents around the loops:



Now we write eq'n's for V-drops around loops:

$$\text{Loop 1: } 40V - i_1 \cdot 3\Omega - (i_1 - i_2) 45\Omega - i_1 \cdot 2\Omega = 0V$$

$$\text{Loop 2: } 64V - i_2 \cdot 1.5\Omega - (i_2 - i_1) 45\Omega - i_2 \cdot 4\Omega = 0V$$

$$\text{or Loop 1: } 40V = i_1 \cdot \underbrace{(3\Omega + 45\Omega + 2\Omega)}_{50\Omega} - i_2 \cdot 45\Omega$$

$$\text{Loop 2: } 64V = -i_1 \cdot 45\Omega + i_2 \cdot \underbrace{(1.5\Omega + 45\Omega + 4\Omega)}_{50.5\Omega}$$

or

$$40V = i_1 \cdot 50\Omega - i_2 \cdot 45\Omega$$

$$64V = -i_1 \cdot 45\Omega + i_2 \cdot 50.5\Omega$$

or

$$45 \cdot 40V = i_1 \cdot 50 \cdot 45\Omega - i_2 \cdot 45 \cdot 45\Omega$$

$$50 \cdot 64V = -i_1 \cdot 45 \cdot 50\Omega + i_2 \cdot 50.5 \cdot 50\Omega$$

$$\text{sum } 45 \cdot 40 + 50 \cdot 64V = 0 + i_2 [50.5 \cdot 50 - 45(45)]\Omega$$

$$i_2 = \frac{1800 + 3200}{2525 - 2025} A = \frac{5000}{500} A = 10A$$

$$i_1 = (40V + 10A \cdot 45\Omega) / 50\Omega = 490V / 50\Omega = 9.8A$$

Now we observe that $i_3 = i_1 = 9.8A$ $i_3 = -i_2 = -10A$

$$i_b = i_3 + i_2 = 9.8A - 10A = -0.2A$$

b) Repeat part (a) for polarity of 64V source reversed.

Just replace 64V with -64V in loop 2 egn.

$$45 \cdot 40 + 50(-64)V = 0 + i_2 [(50.5)50 - 45(45)] \Omega$$

500 as before

$$i_2 = \frac{1800 - 3200}{500} = \frac{-1400}{500} = -2.8 \text{ A}$$

$$i_1 = \frac{40V + -2.8A \cdot 45 \Omega}{50} = -1.72 \text{ A}$$

Note: For Node-V method our consistency check is to calculate all currents flowing in circuit and to verify that sum of currents out of nodes = 0.

For Mesh-i method, our consistency check is to calculate all voltage drops in circuit and to verify that \sum of voltage drops around loop = 0.