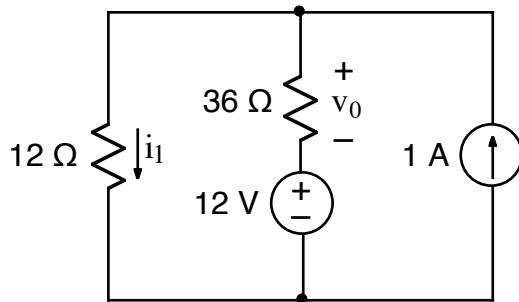



**Ex:**

Use the node-voltage method to find  $i_1$  and  $v_0$ .

*Sol'n:* We follow a standard procedure:

- 1) Assign a reference node, typically on the bottom of the circuit.
- 2) Assign node voltages such as  $v_1, v_2, \dots$  to nodes where 3 or more wires connect.

Here, we call the top node  $v_1$ .

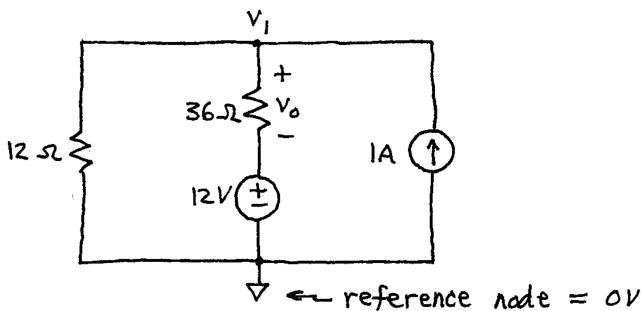

The  $-$  sign of all voltage measurements is at the reference node. Thus,  $v_1$  is the  $v$ -drop from the top node to the reference node.

- 3) Look for dependent sources. None here!

- 4) Look super nodes, (i.e., nodes connected by only a voltage source). None here!
- 5) Write current-summation eqns for each node.

$$V_1 \text{ node: } \frac{V_1 - 0V}{12\Omega} + \frac{V_1 - 12V}{36\Omega} - 1A = 0A$$

Note: We sum the currents flowing out of the node. Our terms are always of the same form: the voltage of the node we are at appears as a positive term from which we subtract the voltage at the neighboring node. We divide the v-drop by the total resistance between nodes to find the current.

- 6) We solve our eq'n for the node-voltage,  $V_1$ .

$$V_1 \left( \frac{1}{12\Omega} + \frac{1}{36\Omega} \right) = \frac{12V}{36\Omega} + 1A = \frac{4}{3} A$$

$$\text{or } V_1 = \frac{4}{3} A \cdot \frac{1}{\frac{1}{12\Omega} + \frac{1}{36\Omega}} = \frac{4}{3} A \cdot 12\Omega \parallel 36\Omega$$

$$V_1 = \frac{4}{3} A \cdot 12\Omega \cdot 1 \parallel 3 = \frac{4}{3} A \cdot 12\Omega \cdot \frac{3}{4} = 12V$$

Given  $V_1 = 12V$ , we have  $i_1 = \frac{12V}{12\Omega} = 1A$  and

$$V_0 = V_1 - 12V = 12V - 12V = 0V.$$