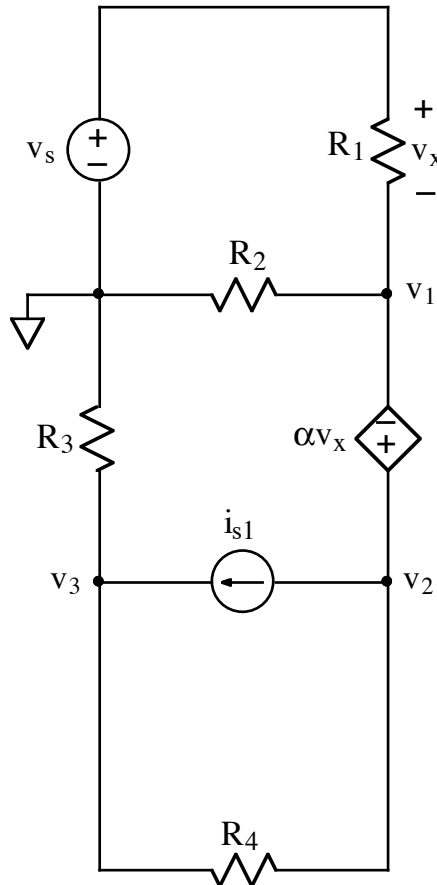


Ex:




For the circuit shown, write three independent equations for the node voltages v_1 , v_2 , and v_3 . The quantity v_x must not appear in the equations.

sol'n: First, we define v_x in terms of node- v 's:

$$v_x = v_s - v_1$$

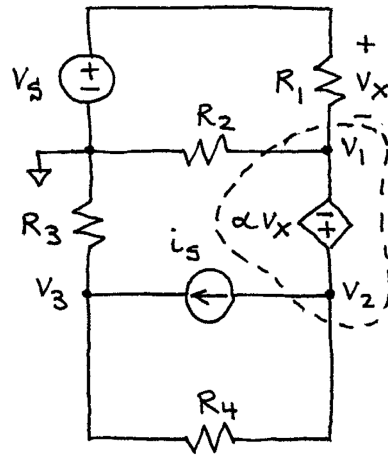Second, we see that v_1 and v_2 are connected by a v -src. Thus, we have a supernode for v_1 and v_2 . We draw a bubble enclosing v_1 and v_2 along with the αv_x source.



We sum the currents flowing out of the bubble:

$$(1) \quad \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + i_s + \frac{V_2 - V_3}{R_4} = 0A$$

Third, we write a voltage eq'n for V_1 and V_2 :

$$(2) \quad V_1 + \underbrace{\alpha(V_s - V_1)}_{V_x} = V_2$$

Fourth, we write a current-sum eq'n for node V_3 :

$$(3) \quad \frac{V_3}{R_3} - i_s + \frac{V_3 - V_2}{R_4} = 0A$$

We now have three independent eq'ns, (1), (2), and (3) that we could solve to find V_1 , V_2 , and V_3 .