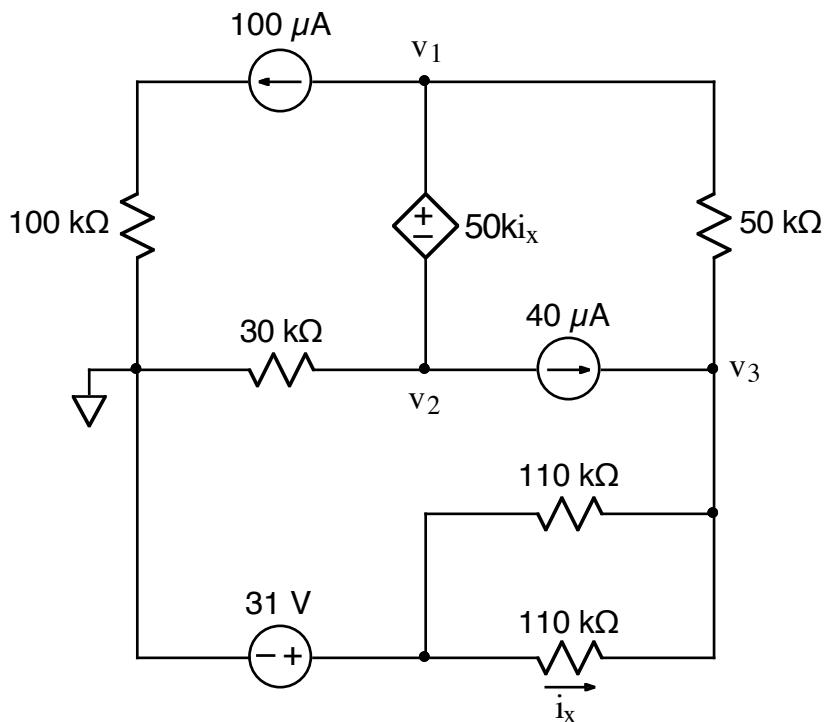


Ex:



Use the node-voltage method to find v_1 , v_2 , and v_3 .

sol'n: We first write the variable for the dependent source, i_x , in terms of node V 's.

$$i_x = \frac{31V - v_3}{110\text{ k}\Omega}$$

We have a super node for v_1 and v_2 since these nodes are connected only by a V -src. Thus, we sum all the currents flowing out of a bubble drawn around v_1 , v_2 , and the V -src between them.

$$v_1, v_2 \text{ node: } 100\mu\text{A} + \frac{v_1 - v_3}{50\text{ k}\Omega} + \frac{v_2}{30\text{ k}\Omega} + 40\mu\text{A} = 0\text{A}$$

We also write a voltage eq'n for v_1 & v_2 :

$$v_1 = v_2 + 50\text{ k}\Omega i_x = v_2 + 50\text{ k}\Omega \left(\frac{31V - v_3}{110\text{ k}\Omega} \right)$$

(Remember to use only node V's in eqns.)

For the v_3 node, we only have a current sum.

$$v_3 \text{ node: } \frac{v_3 - v_1}{50\text{ k}\Omega} + -40\mu\text{A} + \underbrace{\frac{v_3 - 31V}{110\text{ k}\Omega \parallel 110\text{ k}\Omega}}_{55\text{ k}\Omega} = 0\text{A}$$

Now we solve the 3 eqns. We put terms multiplying v_1 , v_2 , and v_3 on the left side and constant terms on the right side.

$$v_1 \frac{1}{50\text{ k}\Omega} + v_2 \frac{1}{30\text{ k}\Omega} + v_3 \left(\frac{-1}{50\text{ k}\Omega} \right) = -100\mu\text{A} - 40\mu\text{A}$$

$$v_1 - v_2 + v_3 \frac{50\text{ k}\Omega}{110\text{ k}\Omega} = 31V \cdot \frac{50\text{ k}\Omega}{110\text{ k}\Omega}$$

$$v_1 \left(\frac{-1}{50\text{ k}\Omega} \right) + v_3 \left(\frac{1}{50\text{ k}\Omega} + \frac{1}{55\text{ k}\Omega} \right) = 40\mu\text{A} + \frac{31V}{55\text{ k}\Omega}$$

We multiply both sides of the 1st eq'n by $150\text{ k}\Omega$ to clear the denominators.

$$v_1 \cdot 3 + v_2 \cdot 5 + v_3 (-3) = -140\mu\text{A} \cdot 150\text{ k}\Omega \approx -21V$$

We multiply both sides of the 2nd eq'n by 11Ω to clear the denominators.

$$v_1 (11) + v_2 (-11) + v_3 (5) = 31V (5) = 155V$$

We multiply the 3rd egn by $1100\text{ k}\Omega = 1.1\text{ M}\Omega$

$$v_1(-22) + v_3(22 + 20) = 40 \cancel{\text{mA}} \cdot 1.1\text{ M}\Omega + 31V(20)$$

$$\text{or } v_1(-22) + v_3(42) = 44V + 620V = 664V$$

Now we start eliminating variables. From the 1st egn, we have

$$v_2 = \frac{-21V - 3v_1 + 3v_3}{5}$$

Our 2nd and 3rd egn's with this v_2 become

$$11v_1 - 11\left(\frac{-21V - 3v_1 + 3v_3}{5}\right) + 5v_3 = 155V$$

and

$$-22v_1 + 42v_3 = 664V$$

Solving the last egn for v_3 gives

$$v_3 = \frac{664V + 22V_1}{42}$$

Substituting into the 1st egn (and collecting terms multiplying v_3) yields the following egn:

$$\left(11 + \frac{33}{5}\right)v_1 + \left(-\frac{33}{5} + 5\right)\left(\frac{664V + 22V_1}{42}\right) = 155V - \frac{21(11)V}{5}$$

or, after multiplying both sides by 5,

$$88V_1 - 8\left(\frac{664V + 22V_1}{42}\right) = 775V - 231V = 544V.$$

Dividing both sides by 4 and moving constant term:

$$22v_1 - \frac{2(22)}{42}v_1 = 136V + \frac{2(664)}{42}v.$$

Multiplying both sides by 42 gives

$$[42(22) - 44]v_1 = 136V(42) + 2(664)V$$

$$\text{or } v_1 = \frac{5712 + 1328V}{924 - 44} = \frac{7040V}{880} = 8V$$

$$\text{Then } v_3 = \frac{664V + 22(8V)}{42} = 20V$$

$$\text{and } v_2 = -\frac{21V - 3(8V) + 3(20V)}{5} = 3V.$$

Consistency check: Calculate currents from these voltages and verify that currents sum to zero at nodes... They do!

