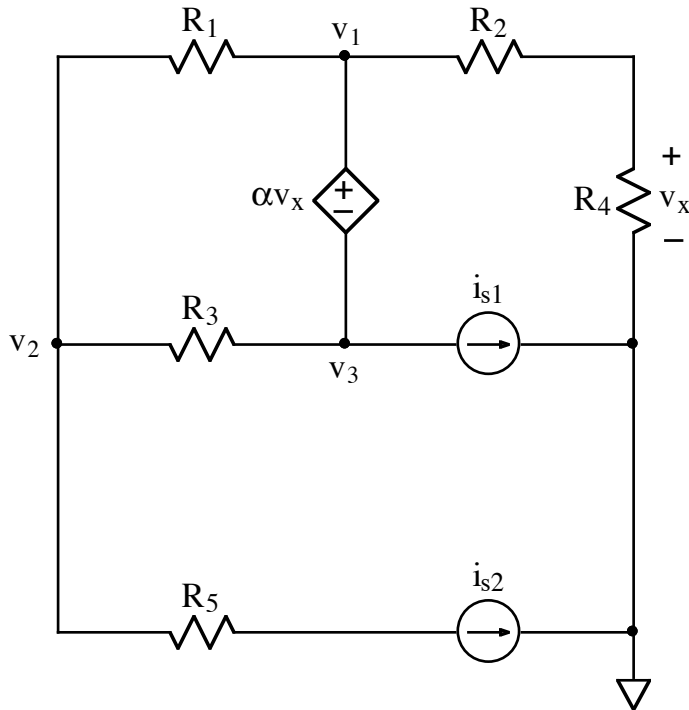



Ex:



For the circuit shown, write three independent equations for the node-voltages,  $v_1$ ,  $v_2$ , and  $v_3$ . The quantity  $v_x$  must not appear in the equations.

sol'n: We first write  $v_x$  in terms of node-v's.

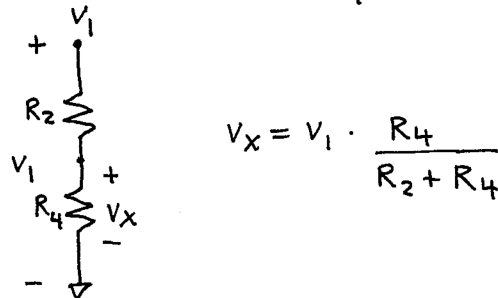We use a v-divider since we have  $v_1$  across  $R_2$  in series with  $R_4$ :



We have a v-src connecting  $v_1$  to  $v_3$ .  
 So  $v_1, v_3$  form a supernode.

We write a current summation eq'n for  $v_1, v_3$ . We find sum of i's flowing out of bubble containing  $v_1, v_3$ , and the dependent  $v$ -src.

$$(1) \quad v_1, v_3 \text{ node: } \frac{v_1 - v_2}{R_1} + \frac{v_1 - 0V}{R_2 + R_4} + \frac{v_3 - v_2}{R_3} + i_{s1} = 0A$$

We also write a voltage eq'n for  $v_1$  and  $v_3$ . Note that we substitute for  $v_x$  to obtain an eq'n containing only node voltages.

$$(2) \quad v_1 = v_3 + \underbrace{\alpha \left( \frac{v_1 R_4}{R_2 + R_4} \right)}_{v_x}$$

For  $v_2$ , we just sum currents out of node.

$$(3) \quad v_2 \text{ node: } \frac{v_2 - v_1}{R_1} + \frac{v_2 - v_3}{R_3} + i_{s2} = 0A$$

We now have our 3 eq'ns for  $v_1, v_2$ , and  $v_3$ .