
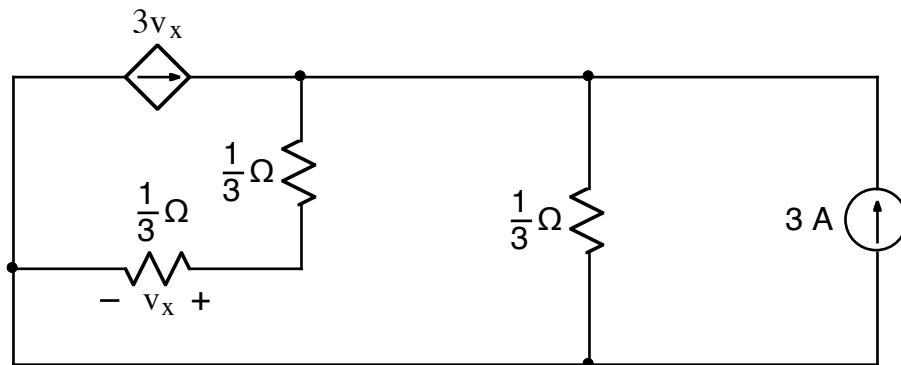


**Ex:**

Calculate the power dissipated in the dependent current source, (labeled  $3v_x$ ).

*Sol'n:* Any method of solution is allowed, (provided it is a valid approach),

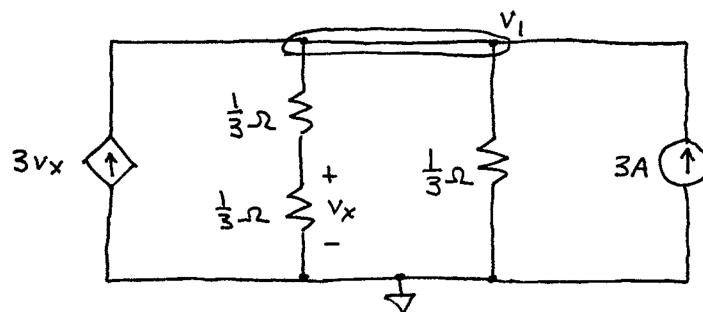We'll use node-voltage method with reference on bottom and  $v_1$  on top. It also helps to redraw circuit.



We write  $v_x$  in terms of  $v_1$  by using a voltage divider:

$$v_x = v_1 \cdot \frac{\frac{1}{3} \Omega}{\frac{1}{3} \Omega + \frac{1}{3} \Omega} = \frac{v_1}{2}$$


Now we write the current summation eq'n for node  $v_1$ .

$$-3\left(\frac{v_1}{2}\right) + \frac{v_1}{\frac{1}{3}\Omega + \frac{1}{3}\Omega} + \frac{v_1}{\frac{1}{3}\Omega} - 3A = 0A$$

$v_x$

$$\text{or } v_1 \left( -\frac{3}{2\Omega} + \frac{3}{2\Omega} + \frac{3}{\Omega} \right) = 3A$$
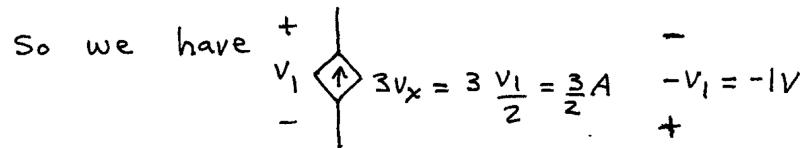
$$\text{or } v_1 = 1A \cdot \Omega = 1V$$




Power is  $P = i v$  where  $i, v$  follow passive sign convention.

$$P = \frac{3}{2}A \cdot (-1V) = -\frac{3}{2}W$$

Note: In this problem we can replace the dependent src with a resistor, (even before we know the value of  $v_1$ ).

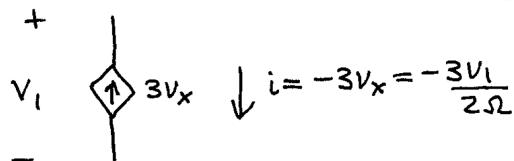We have voltage  $v_1$  across dependent src and current  $-3v_x = -\frac{3v_1}{2}$



Then  $R_{eq} = \frac{v_1}{-\frac{3}{2}v_1} = -\frac{2}{3}\Omega$ .

Use this instead of dependent src: