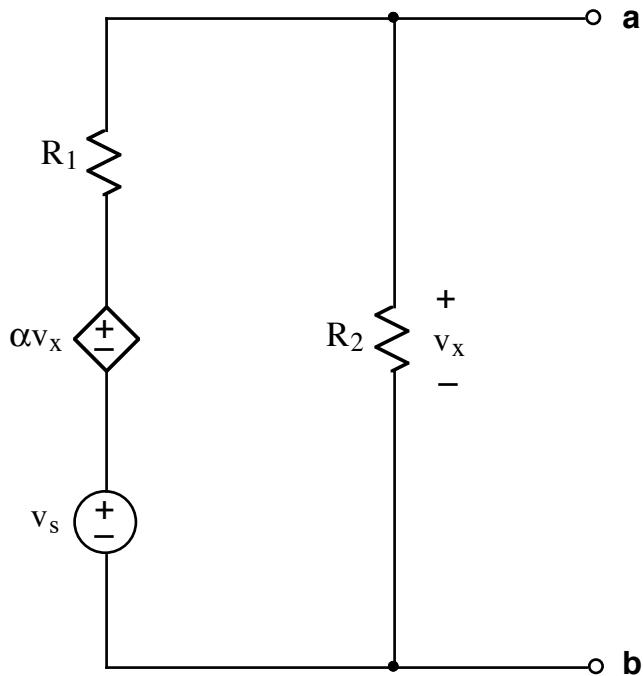



Ex:



Find the Thevenin equivalent circuit at terminals a-b.  $v_x$  must not appear in your solution. **Hint:** Use the node voltage method. **Note:**  $0 < \alpha < 1$ .

*Sol'n:  $V_{Th} = v_{a,b}$  with nothing connected across a, b*

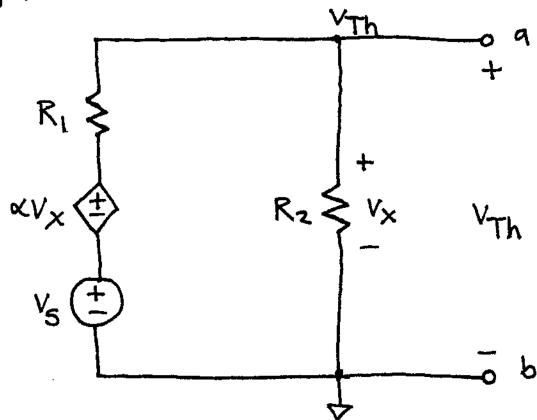Using the node-voltage method, with the reference at the bottom and  $v_{Th}$  at the top, our circuit is as follows:



We write  $v_x$  in terms of  $v_{Th}$ :

$$v_x = v_{Th}$$

The current summation for the  $v_1$  node has only two terms:

$$\frac{v_{Th} - (v_s + \alpha v_{Th})}{R_1} + \frac{v_{Th}}{R_2} = 0 \text{ mA}$$

or

$$v_{Th} \left( \frac{1}{R_1} - \frac{\alpha}{R_1} + \frac{1}{R_2} \right) = \frac{v_s}{R_1}$$

Multiplying both sides by  $R_1$  yields

$$v_{Th} \left( 1 - \alpha + \frac{R_1}{R_2} \right) = v_s$$

or


$$v_{Th} = \frac{v_s}{1 - \alpha + \frac{R_1}{R_2}} = v_s \frac{R_2}{R_2(1-\alpha)+R_1}$$

To find  $R_{Th}$ , we use  $R_{Th} = \frac{v_{Th}}{i_{sc}}$

where  $i_{sc} \equiv$  short circuit current flowing in a wire from a to b.

With a wire connecting a and b,  $v_x = 0V$  and the dependent source becomes a wire.

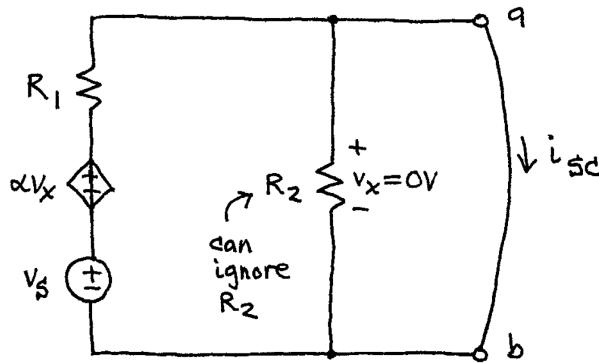Also, no current will flow thru  $R_2$ , and we may ignore  $R_2$ .



If we ignore  $R_2$ , we calculate  $i_{sc}$  from the outer loop:

$$i_{sc} = \frac{V_s}{R_1}$$

Thus, we have


$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{\frac{V_s}{1 - \alpha + \frac{R_1}{R_2}}}{\frac{V_s}{R_1}} = \frac{R_1}{1 - \alpha + \frac{R_1}{R_2}}$$

Other equivalent forms for  $R_{Th}$ :

$$R_{Th} = \frac{R_1 R_2}{R_2(1-\alpha) + R_1}$$

$$R_{Th} = \frac{1}{\frac{1-\alpha}{R_1} + \frac{1}{R_2}} = \frac{R_1}{1-\alpha} \parallel R_2$$

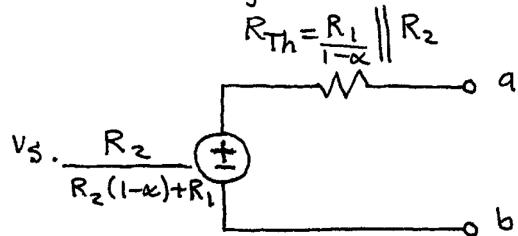The circuit diagram for the Thévenin equivalent:



Note: For the first part of this problem, when we calculate  $V_{Th}$ , we may use an equivalent resistance in place of the dependent source.

With  $a, b$  open circuit, the same current,  $i$ , flows in  $R_2$  and the dependent source.

$$\therefore V_x = i R_2 \quad \text{or} \quad i = \frac{V_x}{R_2}$$

The equivalent  $R$  for the dependent source is

$$R_{eq} = \frac{\alpha V_x}{-i} = \frac{\alpha V_x}{\frac{V_x}{R_2}} = -\alpha R_2$$

Using  $R_{eq}$  in place of  $\alpha V_x$  allows us to obtain  $V_{Th}$  from a  $V$ -divider formula:

$$V_{Th} = V_S \frac{R_2}{R_2 - \alpha R_2 + R_1} = V_S \frac{R_2}{R_2(1-\alpha) + R_1}$$

This agrees with our node-voltage result.