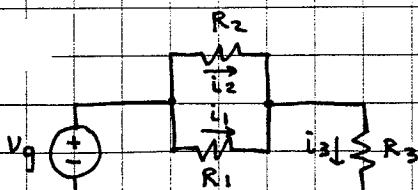


ex:

 V_g, R_2, R_3 fixed nonzero vals

Explain how i_3 would change as R_1 ranged from 0 to ∞ .
 " " " i_1 & i_2 " " " " " "

Sol'n: R_1 and R_2 form current divider for current i_3 .

$$\therefore i_1 = i_3 \cdot \frac{R_2}{R_1 + R_2} \quad i_2 = i_3 \cdot \frac{R_1}{R_1 + R_2}$$

$$\text{Also, } i_3 = \frac{V_g}{\text{tot } R} = \frac{V_g}{R_1 R_2 + R_3}$$

$$\begin{aligned} \text{Now, } R_1 R_2 &= 0 \quad (R_1 = 0) & R_1 R_2 + R_3 &= R_3 \quad (R_1 = 0) \\ &= R_2/2 \quad (R_1 = R_2) & &= R_2/2 + R_3 \quad (R_1 = R_2) \\ &= R_2 \quad (R_1 = \infty) & &= R_2 + R_3 \quad (R_1 = \infty) \end{aligned}$$

$$\begin{aligned} \text{Thus, } i_3 &= \frac{V_g}{R_3} \quad (R_1 = 0) \\ &= \frac{V_g}{\frac{R_2}{2} + R_3} \quad (R_1 = R_2) \\ &= \frac{V_g}{R_2 + R_3} \quad (R_1 = \infty) \end{aligned}$$

$$i_1 = \frac{i_3 R_2}{0 + R_2} = 1 \cdot i_3 \quad (R_1 = 0) \quad i_2 = i_3 \cdot \frac{0}{0 + R_2} = 0$$

$$i_1 = i_3 \frac{R_2}{R_2 + R_2} = \frac{i_3}{2} \quad (R_1 = R_2) \quad i_2 = i_3 \frac{R_2}{R_2 + R_2} = \frac{i_3}{2}$$

$$i_1 = i_3 \frac{R_2}{0 + R_2} = 0 \quad (R_1 = \infty) \quad i_2 = i_3 \frac{\infty}{0 + R_2} = i_3$$

use L'Hopital's rule