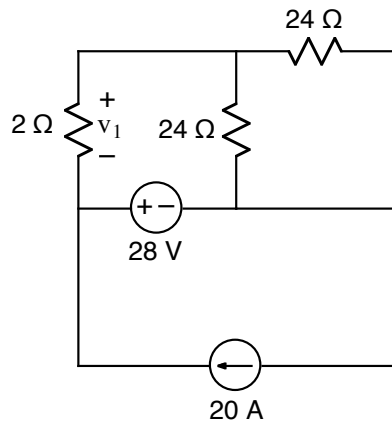


Ex:



Calculate  $v_1$ .

sol'n: We can use a voltage divider consisting of the 28V src, the 2Ω Resistor, and the two 24Ω resistors in parallel:

$$v_1 = -28V \cdot \frac{2\Omega}{2\Omega + 24\Omega \parallel 24\Omega}$$

$$= -28V \cdot \frac{2\Omega}{2\Omega + 24\Omega \cdot \frac{1}{1+1}} \quad \frac{1}{1+1} = \frac{1 \cdot 1}{1+1} = \frac{1}{2}$$

$$= -28V \cdot \frac{2\Omega}{2\Omega + 12\Omega}$$


$$v_1 = -4V$$

Note: We have a minus sign whenever the + sign of the resistor voltage measurement is on the side away from the + sign of the  $v$  src.

Note: We have a voltage divider when the following conditions are met:

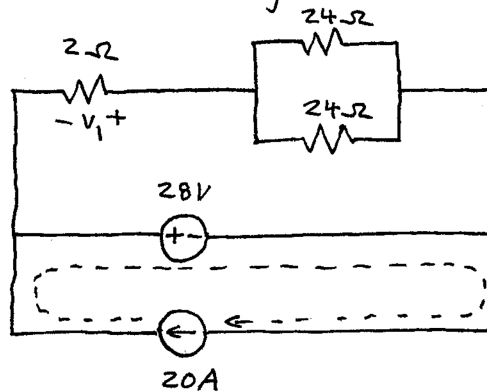- i) The voltage across two or more  $R$ 's in series is known.
- ii) The current thru the  $R$ 's in series is the same.

Note: We can verify that we have a v-divider in this circuit by redrawing it.



The  $20A$  affects the current in the  $28V$  source, but we still have  $28V$  across the  $R$ 's. The  $20A$  just circulates in the bottom half of the circuit.