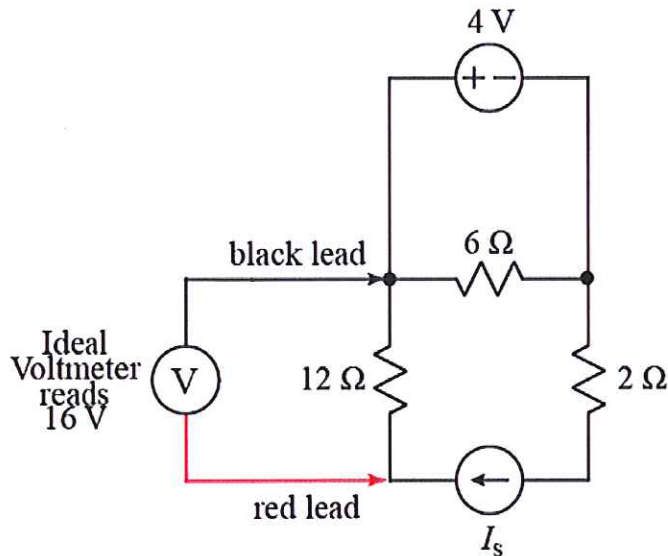


Ex:




- Find the numerical value of I_s .
- Find current flowing into the + input of the 4 V source.

sol'n: a) An ideal voltmeter draws no current, so I_s must flow thru the $12\ \Omega$ resistor (and thru the $2\ \Omega$ resistor, of course).

We can solve for I_s by using Ohm's law for the $12\ \Omega$ resistor. Note that the red lead is the + side of the voltage measurement, so we should measure the current in the $12\ \Omega$ resistor with an arrow pointing up. This is in the same direction as the arrow for I_s , so the sign of our I_s from Ohm's law will be correct.

$$I_s = \frac{16\text{V}}{12\ \Omega} = \frac{4}{3}\text{ A} \approx 1.333\text{ A}$$

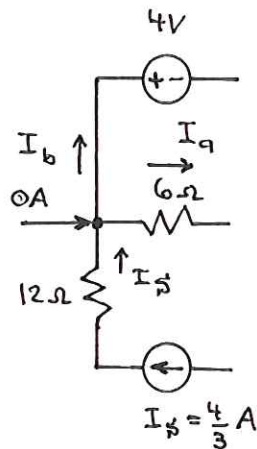b) We use a current summation to find the current flowing into the + input of the 4V source.




The voltmeter draws no current, and we have $I_s = \frac{4}{3} \text{ A}$ flowing into the node thru

the 12Ω resistor. We have the following current summation eq'n with unknown I_a and I_b .

$$I_s = I_a + I_b \quad (\text{what flows in must flow out})$$

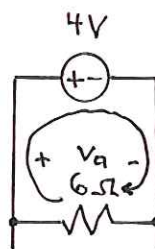To find I_a , we use a voltage loop on the top half of the circuit.



Using a clockwise loop, and using the sign where we exit a component as the sign of the term in the sum, we have the following:

$$-4V + v_a = 0V$$

So $V_a = 4V$. Now we use Ohm's law to find I_a .

$$I_a = \frac{4V}{6\Omega} = \frac{2}{3} A \approx 0.667 A$$

Combining results, we have enough information to determine I_b .

$$I_s = I_a + I_b$$

or

$$\frac{4}{3} A = \frac{2}{3} A + I_b$$

or

$$I_b = \frac{2}{3} A \approx 0.667 A$$