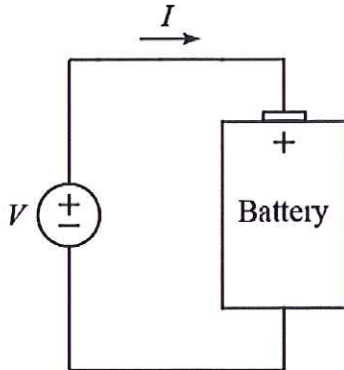


Ex:



$V$	$I$
12 V	1 A
10 V	0 A
8 V	-1 A


When voltage  $V$  is applied to the above battery, the currents shown in the table are measured.

- Find a Thevenin equivalent model of the battery.
- If a  $3\ \Omega$  resistor is connected across the battery (instead of  $V$ ), how much power is dissipated in the  $3\ \Omega$  resistor?

sol'n: a)  $V_{Th} = V$  across battery when nothing is connected to the battery, i.e., when no current is flowing

From the table, we see that no current flows when  $V = 10V$ . But  $V$  is the voltage across the battery. So  $V_{Th} = V = 10V$ .

$$V_{Th} = 10V$$

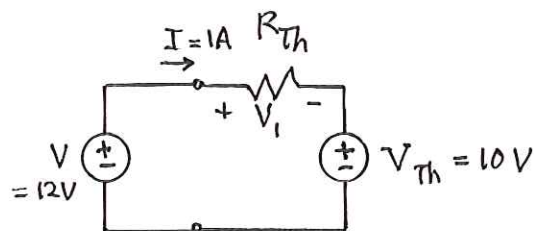

The above diagram shows the circuit model when  $V = 12V$  (and  $I = 1A$  according to the table).

Using a voltage loop, we can determine the voltage drop across  $R_{Th}$ , and then we can use Ohm's law to find the value of  $R_{Th}$  from  $I$  and  $V_1$ . Starting in the lower left corner of the circuit, we have the following v-loop eq'n:

$$+V - V_1 - V_{Th} = 0V$$

or

$$12V - V_1 - 10V = 0V$$

or


$$2V - V_1 = 0V$$

or


$$V_1 = 2V$$

So we can now compute  $R_{Th}$ :
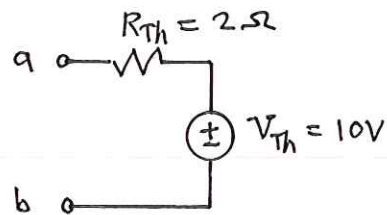
$$R_{Th} = \frac{2V}{I} = \frac{2V}{1A} = 2\Omega$$



b)

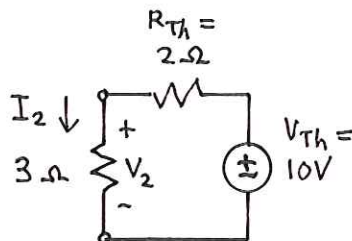

We have a voltage divider circuit.

$$V_2 = V_{Th} \frac{3\Omega}{2\Omega + 3\Omega} = 10V \left( \frac{3}{5} \right) = 6V$$

We can compute  $I_2$  from Ohm's law:

$$I_2 = \frac{V_2}{3\Omega} = \frac{6V}{3\Omega} = 2A$$

Our power is  $P = I_2 V_2 = 2A \cdot 6V = 12W$ .

Note: we could also say  $P = \frac{V_2^2}{3\Omega} = \frac{(6V)^2}{3\Omega} = 12W$ .