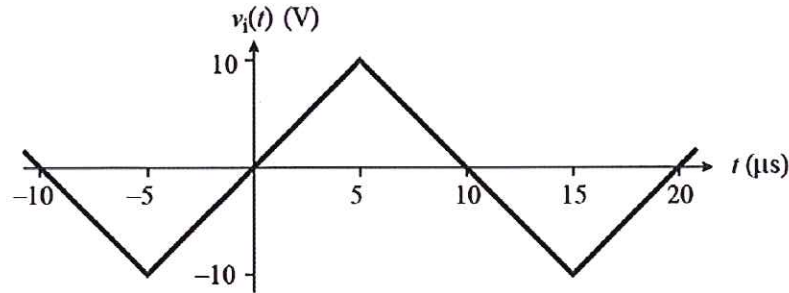





Ex:

A function generator outputs the following signal,  $v_i(t)$ .




Design op-amp circuits to output each of the following waveforms when  $v_i(t)$  is the input.

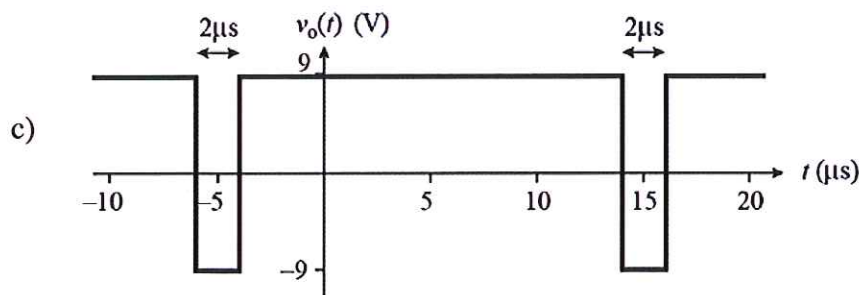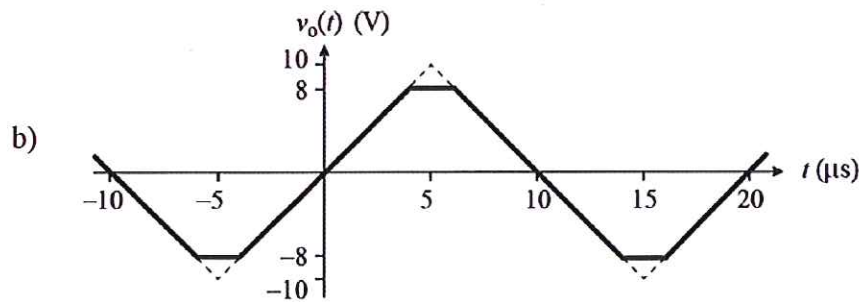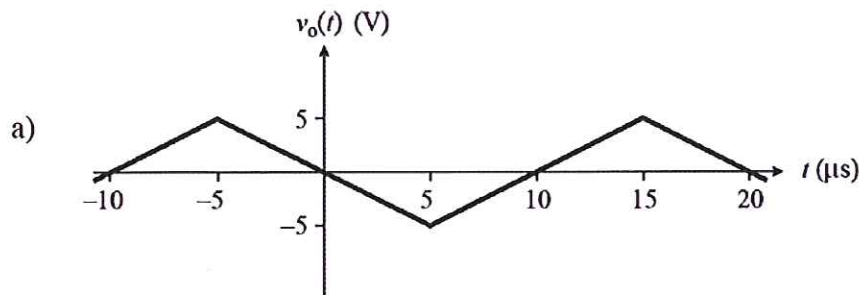You may use either one or two op-amps in each case.



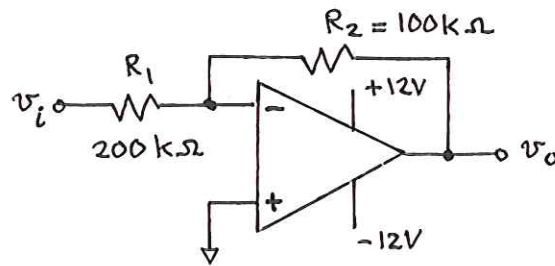
sol'n: a) We need an inverting amplifier with a gain of 0.5. We have  $v_o = -v_i R_2/R_1$ . So  $R_2/R_1 = 1/2$ .




We use  $R_1$ 's  $> 10\text{ k}\Omega$  and  $R_2$ 's  $< 1\text{ M}\Omega$ , and we use supply voltages of at least 6V and less than or equal to  $\pm 15\text{ V}$ , which is a typical maximum supply voltage.

b) We need a non-inverting amplifier with a gain of one. We use supply voltages of  $8+1\text{ V} = 9\text{ V}$  and  $-8-1\text{ V} = -9\text{ V}$  to get clipping at  $\pm 8\text{ V}$ .

For a gain of one, we use a buffer.

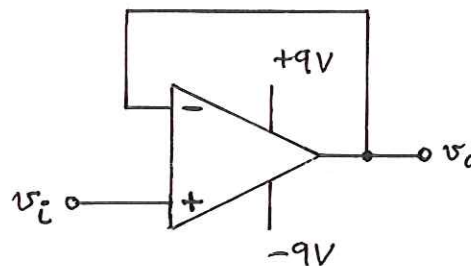

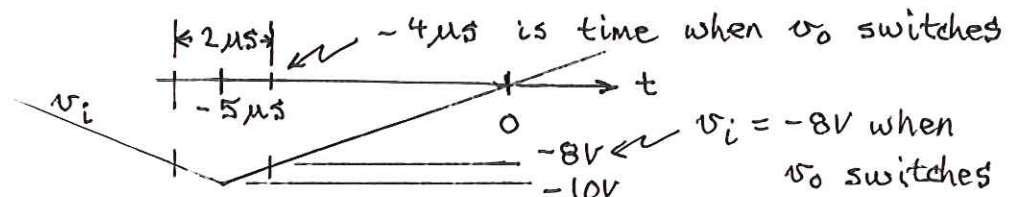c) To get a PWM wave, we use a comparator. We use supply voltages  $\pm 10\text{ V}$  to get  $\pm 9\text{ V}$  output. We now determine the input voltage where  $v_o$  switches.



So we need a reference voltage going into the comparator of  $-8V$ . To avoid using an additional  $v$ -source, we use a  $v$ -divider for the  $-8V$  reference.

$$v_{\text{ref}} = -10V \cdot \frac{R_1}{R_1 + R_2} = -8V$$

One solution is  $120k\Omega$  and  $30k\Omega$ . The key is to have a ratio of four to one.

Finally,  $v_o$  is high when  $v_i > -8V$ . So we want  $v_i$  to go into the  $+$  input of the comparator.

