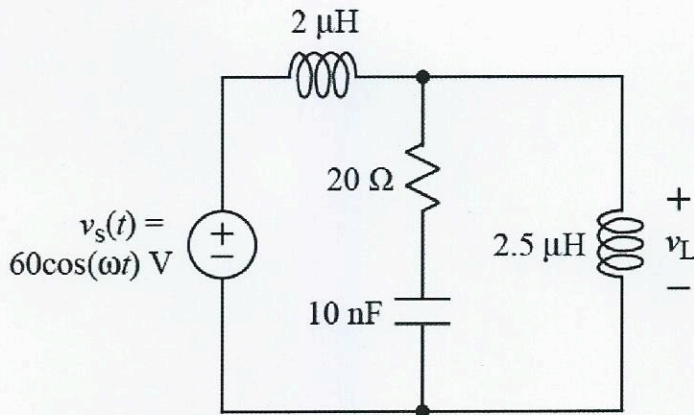


Ex:



$$\omega = 10 \text{ Mr/s}$$

- Draw a frequency-domain model for the above circuit.
- Find the value of phasor voltage V_L across the $2.5 \mu\text{H}$ inductor.
- Find a numerical expression for the value of $v_L(t)$.

sol'n: a) We first calculate impedance values.

$$j\omega L_1 = j10\text{M} 2\mu \Omega = j20 \Omega$$


$$\frac{1}{j\omega C} = \frac{1}{j10\text{M}10\text{n}} \Omega = -j10 \Omega$$

$$j\omega L_2 = j10\text{M} 2.5\mu \Omega = j25 \Omega$$

Next, we determine the phasor for the voltage source.

$$V_s = 60 e^{j0^\circ} \text{ V}$$

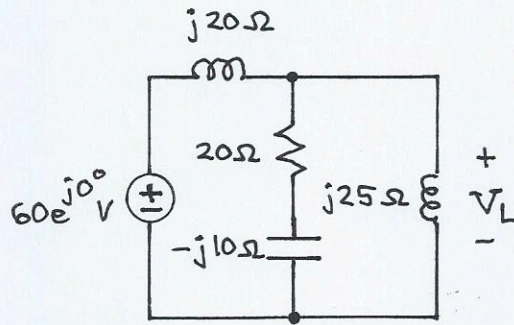We draw the frequency-domain circuit using phasors and impedances.



b) We have voltage divider consisting of

$$z_1 = j20\Omega \text{ and } z_2 = (20 - j10) \parallel j25\Omega$$

Note that V_L is also the voltage across z_2 .

We now find z_2 .

$$z_2 = (20 - j10) \parallel j25\Omega = 5\Omega \cdot (4 - j2) \parallel j5$$

or

$$z_2 = 5\Omega \frac{(4 - j2)j5}{4 - j2 + j5} = 5\Omega \frac{10 + j20}{4 + j3}$$

or

$$z_2 = 25\Omega \frac{2 + j4}{4 + j3} = 25\Omega \frac{2 + j4}{4 + j3} \cdot \frac{4 - j3}{4 - j3}$$

or

$$z_2 = 25\Omega \frac{(2 + j4)(4 - j3)}{4^2 + 3^2} = \frac{25\Omega}{25} (8 + 12 - j6 + j16)$$

or

$$z_2 = 20 + j10\Omega$$

Now for the voltage divider.

$$V_L = 60e^{j0^\circ} V \frac{z_2}{z_1 + z_2} = 60e^{j0^\circ} V \frac{20 + j10}{20 + j10 + j20}$$

or

$$V_L = 60e^{j0^\circ} V \frac{20 + j10}{20 + j30}$$

Polar form is convenient for our calculation.

$$20 + j10 = 10(2 + j) = 10\sqrt{2^2 + 1^2} e^{j \tan^{-1} \frac{1}{2}}$$

$$" = 10\sqrt{5} e^{j 26.6^\circ}$$

$$20 + j30 = 10(2 + j3) = 10\sqrt{2^2 + 3^2} e^{j \tan^{-1} \frac{3}{2}}$$

$$" = 10\sqrt{13} e^{j 56.3^\circ}$$

Using these results, we complete the calculation of V_L .

$$V_L = 60 e^{j0^\circ} V \frac{10\sqrt{5} e^{j 26.6^\circ}}{10\sqrt{13} e^{j 56.3^\circ}}$$

$$V_L = 60 \frac{\sqrt{5}}{\sqrt{13}} e^{j(26.6^\circ - 56.3^\circ)} V = 37.2 e^{-j 29.7^\circ} V$$

$$V_L = 37.2 e^{-j 29.7^\circ} V$$

c) Converting back to the time domain involves re-introducing the $\cos(\omega t)$ term.

$$v_L(t) = 37.2 \cos(10 \text{ Mr/s} \cdot t - 29.7^\circ) V$$