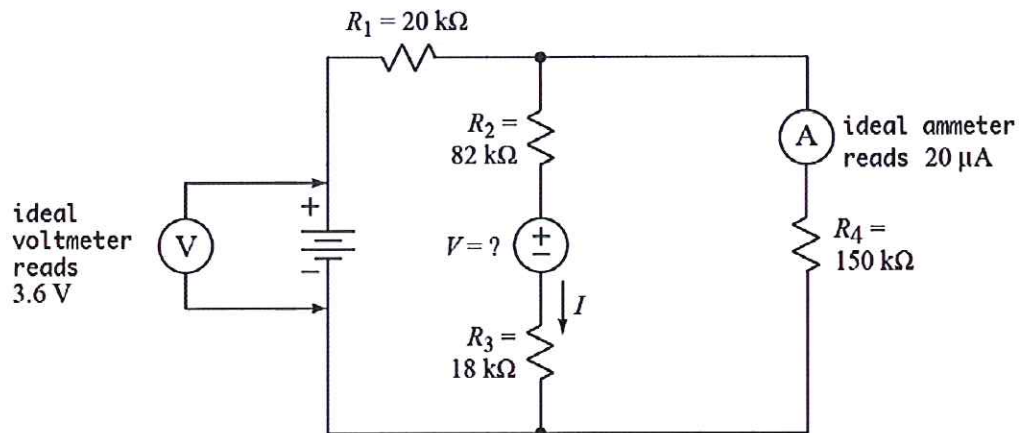



Ex:



Find the values of the following quantities in the above circuit:

- I
- V (the value of the voltage source in the center branch)
- P_{R1} (the power dissipated by R_1)

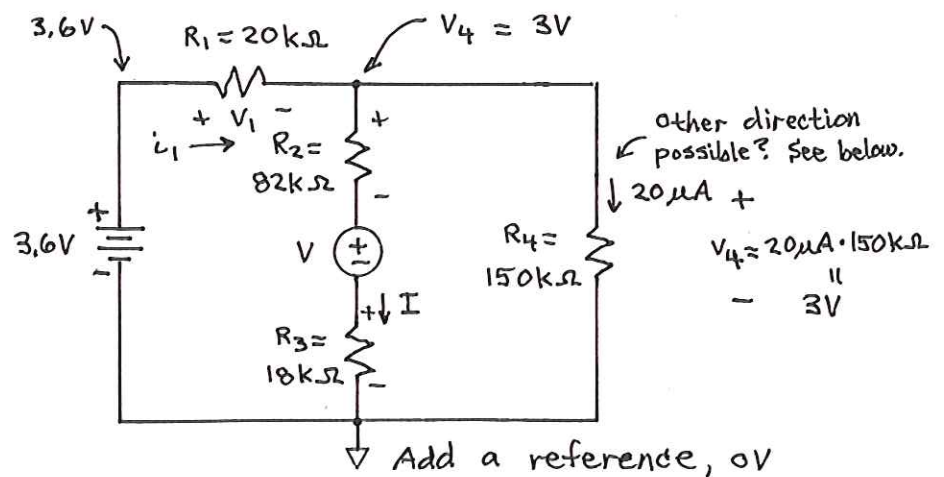sol'n: a) The first step is to redraw the circuit showing the measured values in their usual form.



Using Ohm's law gives a value of 3V across R_4 . Adding a reference at the bottom, means

the voltage at the top center node is $V_4 = 3V$. The voltage at the top left node is $3.6V$. The voltage drop across R_1 is the difference between the top left node and the top center node.

$$V_1 = 3.6V - 3V = 0.6V$$

Ohm's law for R_1 gives the total current flowing in the right side of the circuit.

$$i_1 = \frac{V_1}{R_1} = \frac{0.6V}{20k\Omega} = \frac{3}{100} \text{ mA} = 30\mu\text{A}$$

Using Kirchhoff's current summation law at the top center node yields an equation for current I .

$$i_1 = I + I_{R4}$$

or

$$30\mu\text{A} = I + 20\mu\text{A}$$

or

$$\boxed{I = 10\mu\text{A}}$$

Could the current in R_4 be $-20\mu\text{A}$?

Repeating the above calculations with $v_4' = -3V$, the values for V_1 , i_1 , and I change, although the logic behind the equations remains unchanged. (Primes designate the new values.)

$$V_1' = 3.6V - (-3V) = 6.6V$$

$$i_1' = \frac{V_1'}{R_1} = \frac{6.6V}{20k\Omega} = 330\mu\text{A}$$

$$I' = i_1' - i_{R4}' = 330\mu\text{A} - (-20\mu\text{A}) = \boxed{350\mu\text{A} = I'}$$

b) Voltage V is determined by the total voltage drop across the center branch minus the voltage drops across the resistors. The voltage drops across the resistors is found by using I and Ohm's law.

$$\text{case I: } i_{R4} = +20 \mu\text{A}, \quad I = 10 \mu\text{A}$$

$$V_{R2} = I R_2 = 10 \mu\text{A} \cdot 82 \text{k}\Omega = 820 \text{mV}$$

$$V_{R3} = I R_3 = 10 \mu\text{A} \cdot 18 \text{k}\Omega = 180 \text{mV}$$

$$V = V_4 - (V_{R2} + V_{R3}) = 3\text{V} - 1\text{V} = \boxed{2\text{V} = V}$$

$$\text{case II: } i'_{R4} = -20 \mu\text{A}, \quad I' = 330 \mu\text{A}$$

$$V'_{R2} = I' R_2 = 330 \mu\text{A} \cdot 82 \text{k}\Omega = 27.06 \text{V}$$

$$V'_{R3} = I' R_3 = 330 \mu\text{A} \cdot 18 \text{k}\Omega = 5.94 \text{V}$$

$$V' = V_4' - (V'_{R2} + V'_{R3}) = -3\text{V} - 33\text{V} = \boxed{-36\text{V} = V'}$$

c) Power is the product of current and voltage.

$$P_{R1} = i_1 V_1 = 30 \mu\text{A} (0.6\text{V}) = \boxed{18 \text{mW} = P_{R1}}$$

$$P'_{R1} = i'_1 V'_1 = 330 \mu\text{A} (6.6\text{V}) = \boxed{2.178 \text{W} = P'_{R1}}$$

One interesting observation is that R_1 would have to be a high-power resistor if the latter power is correct.