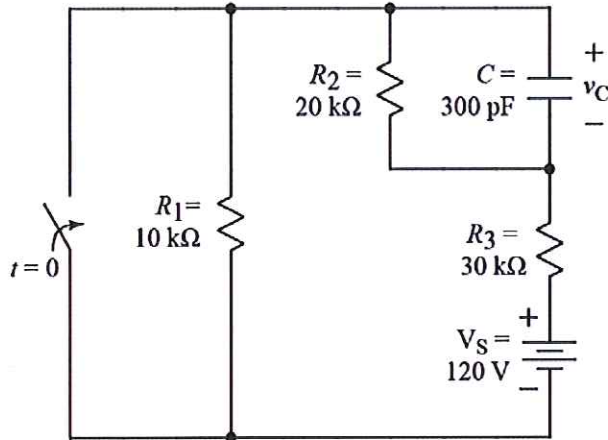


Ex:




The switch has been open for a long time and is closed at  $t = 0$ .

Write the full numerical expression for  $v_C(t)$  for  $t > 0$ .

sol'n: Time  $t=0^-$  yields the initial value of  $v_C$ .  
The circuit has reached equilibrium, and the  $C$  acts like an open circuit because it has ceased charging.

$t=0^-$  model:

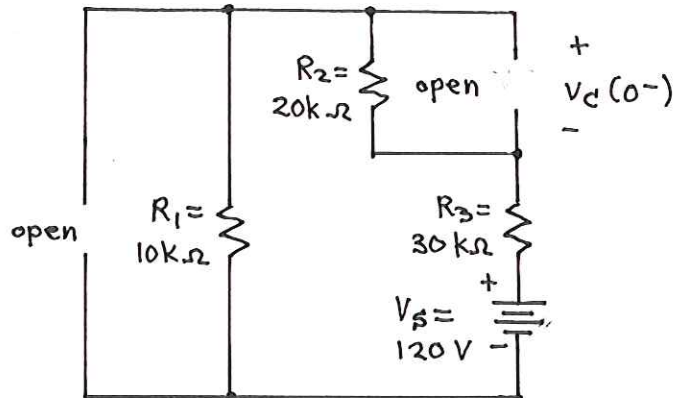

$v_C$  is the same as the voltage across  $R_2$ .

A voltage divider formula gives the voltage across  $R_2$ .

$$v_c = v_{R_2} = -120V \frac{R_2}{R_1 + R_2 + R_3}$$


$$" = -120V \frac{20k\Omega}{10k\Omega + 20k\Omega + 30k\Omega}$$

$$" = -120V \frac{20k}{60k}$$

$$v_c(0^-) = -40V$$

Time  $t \rightarrow \infty$  yields the final value of  $v_c$ . Again, the circuit reaches equilibrium and  $C$  acts like an open circuit.

The switch is closed, bypassing  $R_1$

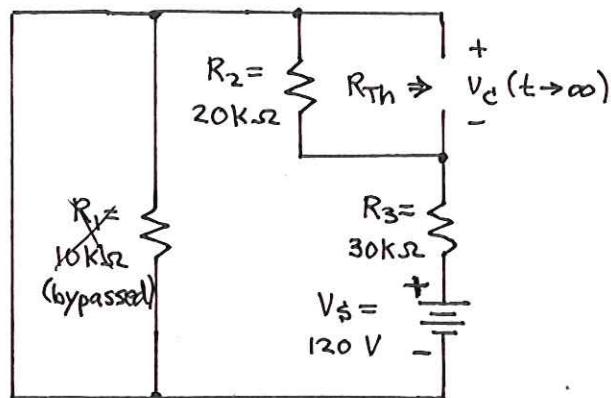


The voltage divider formula for  $v_c$  now excludes  $R_1$ .

$$v_c(t \rightarrow \infty) = -120V \cdot \frac{20k\Omega}{20k\Omega + 30k\Omega} = -48V$$

The time constant is  $\tau = R_{Th}C$ .

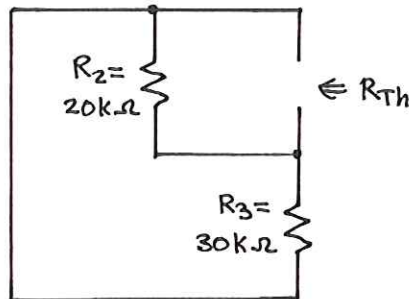$R_{Th}$  is the resistance seen looking into the terminals where  $C$  is connected, with  $V_S$  set to zero and the switch closed.



$$R_{Th} = R_2 \parallel R_3 = 20k\Omega \parallel 30k\Omega$$

or

$$= 10k\Omega \cdot 2 \parallel 3 = 10k\Omega \cdot \frac{2(3)}{2+3} = 12k\Omega$$

$$\tau = R_{Th} C = 12k\Omega (300pF) = 3.6\mu s$$

The values found above are placed in the general form of solution for RC problems:

$$v_c(t \geq 0) = v_c(t \rightarrow \infty) + [v_c(0^-) - v_c(t \rightarrow \infty)] e^{-t/\tau}$$

or

$$v_c(t \geq 0) = -48V + [-40V - (-48V)] e^{-t/3.6\mu s}$$

or

$$v_c(t \geq 0) = -48 + 8 e^{-t/3.6\mu s} \quad V$$