
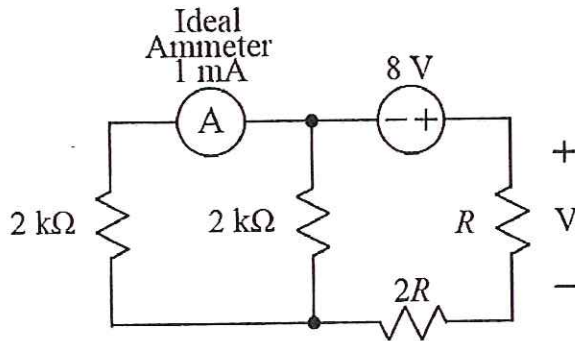


1. (20 points)

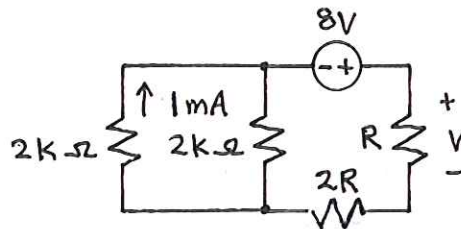

- Find V .
- Find R .

sol'n: a) The ideal ammeter has no V -drop, so we may redraw the circuit as follows:




The current in the $2k\Omega$ must be flowing up since the $8V$ source will push current out the $+$ side.

The two $2k\Omega$ resistors in parallel will have the same V -drop, so $1mA$ flows up thru the $2k\Omega$ resistor in the middle, too. (Same R 's, same V -drops, so same current.)

The voltage drop across each $2k\Omega$ resistor will be $V = IR = 1mA \cdot 2k\Omega = 2V$.

At the bottom node, the current flowing into the node from the right must be $2mA$ because $1mA + 1mA$ flows out of the node thru the $2k\Omega$ R 's.

Our new picture:

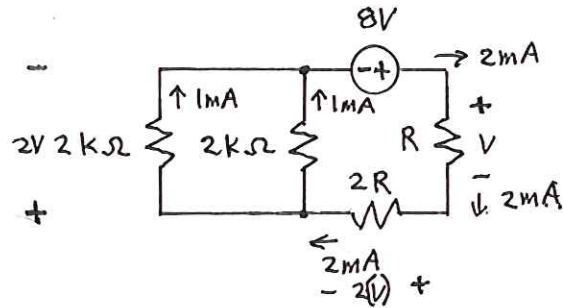

We must have $2 \cdot (V)$ across $2R$ since we have V across R , and the same current flows in R and $2R$.

From a V -loop around the outside we have

$$-2V + 8V - V - 2(V) = 0V$$

or

$$6V - 3(V) = 0V$$

or

$$V = 2V$$

- b) From the above calculation, we have $6V$ across $2R + R = 3R$. Using the V -divider formula, we have $2V$ across R as the answer for part (a). We also have $2mA$ thru R so we can use Ohm's law to find R .

$$R = \frac{2V}{2mA} = 1k\Omega$$